

4. References

Voltage or Current References

Circuit that yields a precise DC voltage or current independent of external influences is called a voltage reference or a current reference.

The primary external influences are:

- Power supply variations
- Temperature variations

Sensitivity and Fractional Temp. Coefficient

Used to characterize the dependence of a reference on power supply and temperature.

- A. The Sensitivity of V_{ref} to changes in power supply V_{DD} is given by,

$$S_{V_{DD}}^{V_{ref}} = \frac{V_{DD}}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial V_{DD}} \quad (1)$$

$$\text{Or, } \frac{\partial V_{ref}}{V_{ref}} = S_{V_{DD}}^{V_{ref}} \cdot \frac{\partial V_{DD}}{V_{DD}} \quad (2)$$

Sensitivity

Sensitivity may vary from 0.0 to 1.0.

Sensitivities less than 0.01 are practical values for a monolithic voltage reference.

The above formulation is valid for current references by simply replacing V_{ref} by I_{ref} .

Fractional Temp. Coefficient

- B. The Sensitivity of V_{ref} to changes in temperature T is given by, $S_T^{V_{ref}}$.

$$S_T^{V_{ref}} = \frac{T}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial T}$$

Got just by replacing V_{DD} by T in eqn (1)

$$\text{Or, } \frac{\partial V_{ref}}{V_{ref}} = S_T^{V_{ref}} \cdot \frac{\partial T}{T}$$

Fractional Temp. Coefficient

Fractional Temp. Coefficient, $TC_F(V_{ref})$:

This is another popular concept used to measure the degree of temperature dependence of reference.

$$TC_F(V_{ref}) = 1/V_{ref} (\partial V_{ref} / \partial T) = 1/T (S_T^{V_{ref}})$$

Units of TC_F - parts per million/ $^{\circ}\text{C}$ or ppm/ $^{\circ}\text{C}$.

Example:

Sensitivity, $S_T^{V_{ref}} = 0.01$ at room temperature,
 $\Rightarrow TC_F(V_{ref}) = 1/T (S_T^{V_{ref}})$
 $= (1/300) \times 0.01 \times 1,000,000$
 $= \underline{33.3 \text{ ppm}/^\circ\text{C}}$

References with TC_F of less than $50 \text{ ppm}/^\circ\text{C}$ are considered to be stable w.r.t. temperature.

Simple Voltage References


In CMOS IC design, we can derive reference voltages from the power supplies using resistors and MOSFETs.

1. Resistor – Only Voltage Reference
2. Resistor – MOSFET Voltage Reference
3. MOSFET – Only Voltage Reference

1. Resistor – Only Voltage Reference

This voltage divider, formed with 2 resistors, provide a DC voltage between V_{DD} and ground depending on values of R_1 and R_2 .

Here, $V_{ref} = \frac{R_2}{(R_1 + R_2)} V_{DD}$

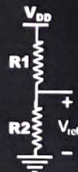**Advantages:**

- Simple
- Temperature Insensitive
- Process Insensitive – changes in the sheet resistance have no effect on the voltage division.

Disadvantages:

- To reduce the power dissipation, the resistors must be made large. But large resistors require a large die area.
- The sensitivity of V_{ref} w.r.t. V_{DD} is found to be,


$$S_{V_{DD}}^{V_{ref}} = \frac{V_{DD}}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial V_{DD}} = 1$$

2. Resistor – MOSFET Voltage Reference

Since gate and drain terminals are shorted, M_1 always remains in saturation.

Here, $V_{DS} = V_{GS} = V_{ref}$
 $I_D = (V_{DD} - V_{ref})/R = \frac{1}{2} \beta_1 (V_{GS} - V_{th})^2$

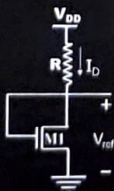Or, $V_{ref} = V_{th} + \sqrt{\frac{2I_D}{\beta_1}} = V_{th} + \sqrt{\frac{2(V_{DD} - V_{ref})}{R\beta_1}}$



$$S_{V_{DD}}^{V_{ref}} = \frac{V_{DD}}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial V_{DD}} = \frac{1}{V_{th} \sqrt{\frac{2R\beta_1}{V_{DD}} + 2}}$$

$$TC_F(V_{ref}) = \frac{1}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial T}$$

$$TC_F(V_{ref}) = \frac{1}{V_{ref}} \left[\frac{\partial V_{th}}{\partial T} - \frac{1}{2} \sqrt{\frac{2V_{DD}}{R\beta_1}} \left(\frac{1}{R} \frac{\partial R}{\partial T} - \frac{1.5}{T} \right) \right]$$

\downarrow
 $V_{th} \cdot TC_{V_{th}}$

3. MOSFET – Only Voltage Reference


This generates a reference voltage equal to the voltage on the gates of the MOSFETs w.r.t. ground.

$$\frac{1}{2}\beta_1(V_{ref}-V_{SS}-V_{th})^2 = \frac{1}{2}\beta_2(V_{DD}-V_{ref}-V_{th})^2$$

Or the reference voltage is given by,

$$V_{ref} = \frac{V_{DD} - V_{th} + \sqrt{\frac{\beta_1}{\beta_2}} (V_{SS} + V_{th})}{\sqrt{\frac{\beta_1}{\beta_2}} + 1}$$
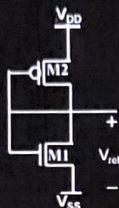
$$\frac{\beta_1}{\beta_2} = \left[\frac{(V_{DD} - V_{ref} - V_{th})^2}{(V_{ref} - V_{SS} - V_{th})^2} \right]$$



Sensitivity of V_{ref} w.r.t. V_{DD} is given by,

$$S_{V_{DD}}^{V_{ref}} = \frac{V_{DD}}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial V_{DD}} = \frac{V_{DD}}{V_{DD} - V_{th} + \sqrt{\frac{\beta_1}{\beta_2}} (V_{SS} + V_{th})}$$

Assuming the temperature dependence of the ratio of the transconductance parameters, β_1/β_2 , is negligible, the $TC_F(V_{ref})$ is given by,

$$TC_F(V_{ref}) = \frac{1}{V_{ref}} \cdot \frac{\partial V_{ref}}{\partial T}$$

$$TC_F(V_{ref}) = \frac{1}{V_{ref}} \cdot \frac{1}{\sqrt{\frac{\beta_1}{\beta_2}} + 1} \left[\frac{\partial(-V_{th})}{\partial T} + \sqrt{\frac{\beta_1}{\beta_2}} \frac{\partial V_{th}}{\partial T} \right]$$

To achieve $TC_F(V_{ref}) = 0$ requires,

$$TC_F(V_{ref}) = \frac{1}{V_{ref}} \cdot \frac{1}{\sqrt{\frac{\beta_1}{\beta_2}} + 1} \left[\frac{\partial(-V_{th})}{\partial T} + \sqrt{\frac{\beta_1}{\beta_2}} \frac{\partial V_{th}}{\partial T} \right] = 0$$

$$\text{i.e., } \frac{\partial(-V_{th})}{\partial T} = -\sqrt{\frac{\beta_1}{\beta_2}} \frac{\partial V_{th}}{\partial T} \Rightarrow 2.7\text{mV}/^\circ\text{C} = \sqrt{\frac{\beta_1}{\beta_2}} (2.4\text{mV}/^\circ\text{C})$$

$$\text{i.e., } \beta_1/\beta_2 = 1.125$$

Zero temperature coefficient, to a first order can be met by satisfying this equation. However, this ratio is most often set by the desired V_{ref} . So for a particular single value of V_{ref} , the reference becomes temperature insensitive.

Design Example:

Design a 3V MOSFET-Only voltage reference. Determine the temperature coeff. of the reference. Data given: $V_{DD}=+5\text{V}$, $V_{SS}=0\text{V}$, $V_{th}=0.8\text{V}$, $V_{tp}=0.9\text{V}$, $L_1=L_2=5\mu\text{m}$, $K_n=50\mu\text{A/V}^2$, $K_p=17\mu\text{A/V}^2$.

$$\frac{\beta_1}{\beta_2} = \left[\frac{(5 - 3 - 0.9)}{(3 - 0 - 0.8)} \right]^2 = 0.25$$

Setting $L_1=L_2= W_1 = 5\mu\text{m}$,

$$\frac{\beta_1}{\beta_2} = \frac{K_n W_1 L_2}{K_p W_2 L_1} = \frac{50\mu\text{A/V}^2 \cdot 5\mu\text{m} \cdot 5\mu\text{m}}{17\mu\text{A/V}^2 \cdot W_2 \cdot 5\mu\text{m}} = 0.25$$

Solving gives, $W_2 = 60\mu\text{m}$.

The temp. coeff. is given by,

$$TC_F(V_{ref}) = \frac{1}{V_{ref}} \cdot \frac{1}{\sqrt{\frac{\beta_1}{\beta_2}} + 1} \left[\frac{\partial(-V_{th})}{\partial T} + \sqrt{\frac{\beta_1}{\beta_2}} \frac{\partial V_{th}}{\partial T} \right]$$

$$\text{But, } \frac{\partial V_{th}}{\partial T} = V_{th} \cdot TCV_{th} = (0.8\text{V})(-0.003/^\circ\text{C}) = -2.4\text{mV}/^\circ\text{C}$$

$$-\frac{\partial V_{tp}}{\partial T} = -V_{tp} \cdot TCV_{tp} = -(0.9\text{V})(-0.003/^\circ\text{C}) = 2.7\text{mV}/^\circ\text{C}$$

$$TC_F(V_{ref}) = \frac{1}{3} \cdot \frac{1}{\sqrt{\frac{50 \times 5}{17 \times 60}} + 1} \left[0.0027 + \sqrt{\frac{50 \times 5}{17 \times 60}} (-0.0024) \right] = 337\text{ppm}/^\circ\text{C}$$

Current Source Self-Biasing Circuits

The drawback of the 3 references discussed so far are that, they are very sensitive to power supply and temperature.

Here, we discuss 3 methods of biasing which reduce the effects of power supply variations and possibly temp.

1. Threshold Voltage Referenced Self-Biasing
2. Diode Referenced Self-Biasing
3. Thermal Voltage Referenced Self-Biasing

1. Threshold Voltage Referenced Self-Biasing


MOSFETs M3 & M4 force the same current to flow through M1 & M2.

$$IR = V_{GS1} = V_{TN} + \sqrt{\frac{2I}{\beta_1}}$$

If β_1 is very large, then, I is given by,

$$I \approx V_{TN}/R$$

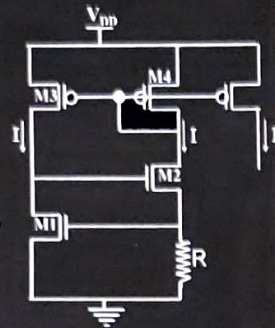i.e., current is independent of the power supply voltage (neglecting channel length modulation and body effect).




$$I = \frac{1}{2}\beta_1(V_{GS1} - V_{TN})^2$$

$$\text{Or, } V_{GS1} = V_{TN} + \sqrt{\frac{2I}{\beta_1}}$$


Note:

- Here we assumed the output resistance of the MOSFET were infinite. But by cascoding M3 and M4 helps to make the bias circuit behave more ideal.
- The accuracy of I is limited by the threshold voltage accuracy, which may vary by 20%, and the $n+$ resistivity, which may vary by 20% as well.
- $TC_F(I)$ depends on $TC_F(V_{TN})$ and $TC_F(R)$.
But $TC_F(V_{TN}) = -3000 \text{ ppm}/^\circ\text{C}$ and $TC_F(R) = +2000 \text{ ppm}/^\circ\text{C}$.
So, the reference current, I has a large negative temperature coefficient.

Startup Circuit

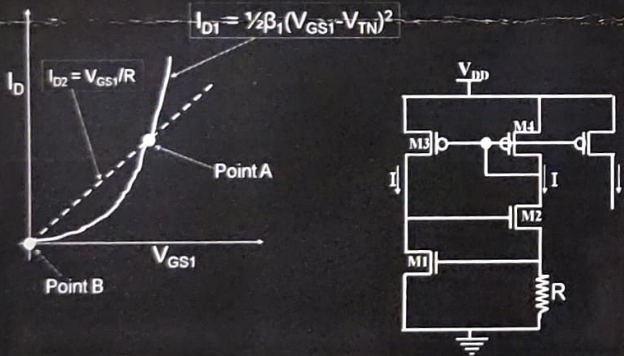


Startup Circuit

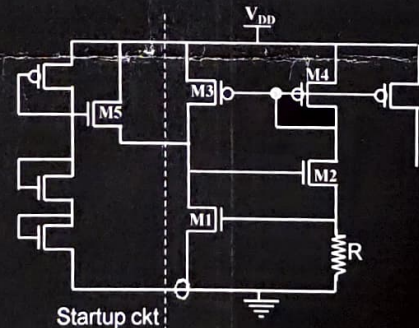

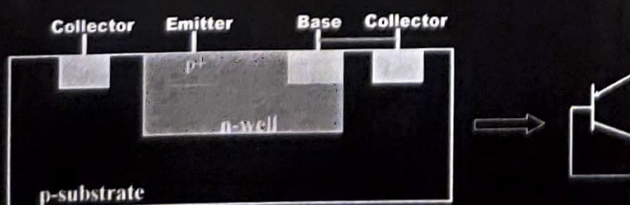2. Diode Referenced Self-Biasing

The parasitic PNP transistor, available in the n-well process, in conjunction with the CMOS transistors, is used to generate the reference current or voltage.




A Base-Collector connected transistor is equivalent to a Diode.



The no. '1' indicates the minimum sized emitter. The current through a forward-biased Diode is given by,

$$I_d = I_s e^{V_d/V_T}, \text{ Where } V_T \text{ is the thermal voltage} = kT/q$$

I_s is the saturation current

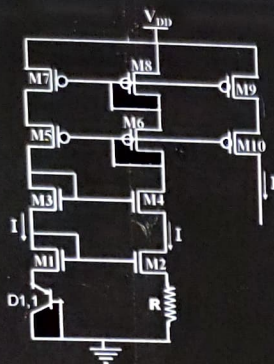

Diode Referenced Self-Biasing Circuit

Here the cascode mirrors made with M1 through M8 force the same current, I , to flow through D1 and R

$$I = V_d/R = I_s e^{V_d/\eta V_T}$$

$$\text{Or, } V_d = \eta V_T \ln(I/I_s)$$

Solving for the resistor gives,

$$R = \frac{\eta V_T}{I} \ln(I/I_s)$$

The main benefit of this circuit over the threshold referenced self-biasing circuit is the better matching, from wafer to wafer and on the same die, of the diode voltage over the threshold voltage.

Sensitivity and $TC_F(I_{ref})$:

$$I_{ref} = V_d/R$$

This shows that the reference is insensitive to power supply variations.

$$TC_F(I_{ref}) = \frac{1}{I_{ref}} \frac{\partial I_{ref}}{\partial T} = \frac{1}{I_{ref}} \frac{\partial}{\partial T} \left(\frac{V_d}{R} \right)$$

$$= \frac{1}{I_{ref}} \left[\frac{R \frac{\partial V_d}{\partial T} - V_d \frac{\partial R}{\partial T}}{R^2} \right]$$

$$TC_F(I_{ref}) = \frac{1}{V_d} \frac{\partial V_d}{\partial T} - \frac{1}{R} \frac{\partial R}{\partial T} = TC_F(V_d) - TC_F(R)$$


$$TC_F(I_{ref}) = TC_F(V_d) - TC_F(R)$$

Drawback: Temperature dependence.

The temp. coeff. of the diode $\approx -3,300 \text{ ppm}/^\circ\text{C}$ and R has $+2000 \text{ ppm}/^\circ\text{C}$. This causes the biasing circuit to have a large negative temperature coefficient.

Therefore, this reference is also called as CTAT (Complimentary To Absolute Temperature).

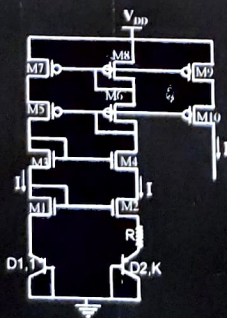3. Thermal Voltage Referenced Self-Biasing



M1 through M8 forces the same current through D1 and D2.

$$V_{d1} = IR + V_{d2} \quad \text{--- (1)}$$

$$I_{d1} = I_s e^{V_{d1}/\eta V_T} \rightarrow V_{d1} = \eta V_T \ln \frac{I}{I_s}$$

$$I_{d2} = K I_s e^{V_{d2}/\eta V_T} \rightarrow V_{d2} = \eta V_T \ln \frac{I}{K I_s}$$

From eqn. (1), solving for the resistor, R, gives,

$$R = (V_{d1} - V_{d2})/I = \frac{\eta V_T}{I} \ln(K)$$

$$\text{Or, } I = \frac{\eta V_T \ln(K)}{R} = \frac{\eta k}{qR} \ln(K) \cdot T \quad \left| \quad V_T = kT/q \right.$$

$$\text{Or, } I = \frac{\eta V_T \ln(K)}{R} = \frac{\eta k}{qR} \ln(K) \cdot T$$

Here, the current is proportional to the absolute temperature (PTAT).

$$TC_F(I_{ref}) = \frac{1}{I_{ref}} \frac{\partial I_{ref}}{\partial T} = \frac{1}{I_{ref}} \frac{\partial}{\partial T} \left(\frac{\eta V_T \ln(K)}{R} \right)$$

$$TC_F(I_{ref}) = \frac{1}{V_T} \frac{\partial V_T}{\partial T} - \frac{1}{R} \frac{\partial R}{\partial T} = \underline{\underline{TC_F(V_T) - TC_F(R)}}$$

$$TC_F(I_{ref}) = \underline{\underline{TC_F(V_T) - TC_F(R)}}$$

Advantages:

Since both V_T and R exhibit positive temperature coeff., it gives better temperature characteristics than the diode or threshold voltage references.


$TC_F(V_T) \approx +3,300 \text{ ppm}/^\circ\text{C}$, and $TC_F(R) = +2000 \text{ ppm}/^\circ\text{C}$
Hence, $TC_F(I_{ref}) \approx 1,300 \text{ ppm}/^\circ\text{C}$

Drawbacks:

Mismatches in the gate-source voltages of M1 and M2 can result in large variations in I_{ref} .

Bandgap Voltage References

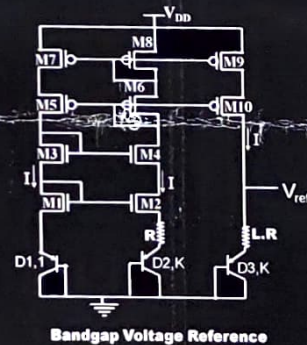Bandgap voltage references combine the **positive TC** of the thermal voltage with the **negative TC** of the diode forward voltage in a circuit to achieve a voltage reference with a **zero TC**.



Diode D3 is the same size as D2, while the resistor in series with D3 is L times larger than the resistor in series with D2.

The current I in the figure is given by,

$$I = \frac{\eta V_T \ln(K)}{R}$$

The reference output voltage w.r.t. ground is given by,

$$V_{ref} = I \cdot L \cdot R + V_{d3}$$

$$\text{Or, } V_{ref} = (L \cdot \eta \ln(K) V_T + V_{d3}) = (L \cdot \eta \ln(K) V_T + \eta V_T \ln \frac{1}{K I_s})$$

The TC of the bandgap reference is zero when,

$$\frac{\partial V_{ref}}{\partial T} = L \cdot \eta \ln(K) \frac{\partial V_T}{\partial T} + \frac{\partial V_{d3}}{\partial T} = 0$$

$$\frac{\partial V_{ref}}{\partial T} = L \cdot \eta \ln(K) \frac{\partial V_T}{\partial T} + \frac{\partial V_{d3}}{\partial T} = 0$$

$0.085 \text{ mV}/^\circ\text{C} \quad -2 \text{ mV}/^\circ\text{C}$

This is true when,


$$L \cdot \eta \ln(K) = 2/0.085 = 23.5$$

For $\eta=1$ and $K=8$ the factor $L = 11.3 \approx 12$ for a zero TC.

The value of V_{ref} [for $\eta=1, K=8, L=12, V_T=26 \text{ mV}, I=10 \mu\text{A}, I_s=10^{-15} \text{ A}, T=300^\circ\text{K}$] will be,

$$V_{ref} = (L \cdot \eta \ln(K) V_T + \eta V_T \ln \frac{1}{K I_s}) = 1.25 \text{ V}$$

Beta Multiplier Referenced Self-Biasing

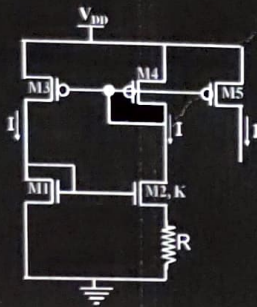

Width of M2 is made 'K' times larger than width of M1, so that,

$$\beta_2 = K \beta_1 \text{ assuming } L_1 = L_2 \text{ and } W_2 = K W_1$$

and therefore,

$$V_{GS1} = V_{GS2} + IR \quad (1)$$

But,

$$V_{GS1} = V_{TN} + \sqrt{\frac{2I}{\beta_1}}$$

Neglecting body effect,

$$V_{GS2} = V_{TN} + \sqrt{\frac{2I}{K\beta_1}}$$

$$I = \frac{1}{2} \beta (V_{GS} - V_{TN})^2$$

$$\text{Or, } V_{GS} = V_{TN} + \sqrt{\frac{2I}{\beta}}$$

Solving for I,

$$I = \frac{2}{R^2 \beta_1} \left[1 - \sqrt{\frac{1}{K}} \right]^2 \quad (2)$$


This is the basic design equation for this reference. K is always greater than 1.

Temperature coeff. of the current reference is,

$$TC_F(I_{ref}) = \frac{1}{I} \frac{\partial I}{\partial T} = -2 \frac{1}{R} \frac{\partial R}{\partial T} - \frac{1}{\beta_1} \frac{\partial \beta_1}{\partial T}$$

$$= -4000 \text{ ppm/}^\circ\text{C} + \frac{1.5}{T}$$

Biasing β multiplier reference

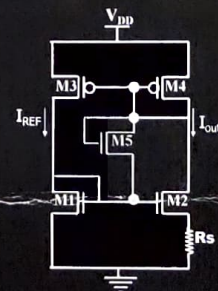


Example:

Using the β multiplier current reference, design a $10\mu\text{A}$ current source. Estimate the TC of the reference at 300°K and assume $V_{DD}=5\text{V}$, $V_{SS}=0\text{V}$.

If we set $L_1 = L_2 = W_1 = 5\mu\text{m}$ and $K=4$ then using eqn. (1) and solving for R,

$$R^2 = \frac{2}{10\mu\text{A} \cdot 50\mu\text{A/V}^2} \cdot \frac{1}{4} \Rightarrow R = 31.6\text{K}\Omega$$
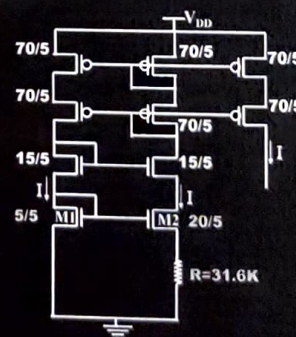
$$TC_F(I_{ref}) = -4000 \text{ ppm/}^\circ\text{C} + \frac{1.5}{300} \times 1,000,000 = 1000 \text{ ppm/}^\circ\text{C}$$




A Voltage Reference

If the reference is designed correctly, we can make the TC of V_{GS1} equal to zero. We define our reference voltage as,

$$V_{ref} = V_{GS1}$$

Substituting eqn. (2) in (1),
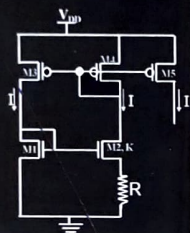
$$V_{ref} = V_{GS1} = \frac{2}{R\beta_1} \left(1 - \frac{1}{\sqrt{K}} \right) + V_{THN}$$



The change in V_{ref} with temperature is

$$\frac{dV_{ref}}{dT} = \frac{dV_{THN}}{dT} - \frac{2}{R\beta_1} \left(1 - \frac{1}{\sqrt{K}} \right) \left[\frac{1}{R} \frac{\partial R}{\partial T} + \frac{1}{\beta_1} \frac{\partial \beta_1}{\partial T} \right]$$

or

$$\frac{dV_{ref}}{dT} = -2.4 \text{ mV}/^\circ\text{C} - \frac{2}{R\beta_1} \left[1 - \frac{1}{\sqrt{K}} \right] \left[-2,000 \text{ ppm}/^\circ\text{C} + \frac{1.5}{T} \right]$$

At 300 °K Eq. (21.46) is equal to zero when

$$\frac{2}{R\beta_1} \left[1 - \frac{1}{\sqrt{K}} \right] = \frac{2,400}{3,000} = 0.8$$

Furthermore, if $K = 4$ we require that

$$R = \frac{1}{0.8 \cdot \beta_1}$$

and

$$V_{ref} = 0.8 + V_{THN} = 1.63 \text{ V}$$

- There will be an error in the reference voltage associated with the change in the threshold voltage due to process variations and body effect as well as changes in R , β , and T .
- Using p-channel MOSFETs in their own well eliminates errors due to the body effect.
- The threshold voltage can vary by as much as 20 percent (this is part of the reason why the body effect is neglected so often in our hand calculations).
- Thus, precision voltages are more difficult to achieve than the bandgap reference of the last section. Often, voltage references are adjusted on die by laser trimming via metal options a resistor value.

The following example illustrates the design and temperature performance of a zero TC voltage reference using the β multiplier self-biased reference.

Design a zero TC voltage β multiplier reference at 300°K with $V_{SS}=0$ V and $V_{DD}=5$ V. Simulate the design for changing V_{DD} and temperature.

- We will use the general cascode schematic shown earlier with V_{DD} swept in the simulations and $V_{SS}=0$.

The resistor for this design is,

$$R = \frac{1}{0.8 \beta_1} = \frac{1}{0.8 \times 50} = 25 \text{ K}\Omega$$