
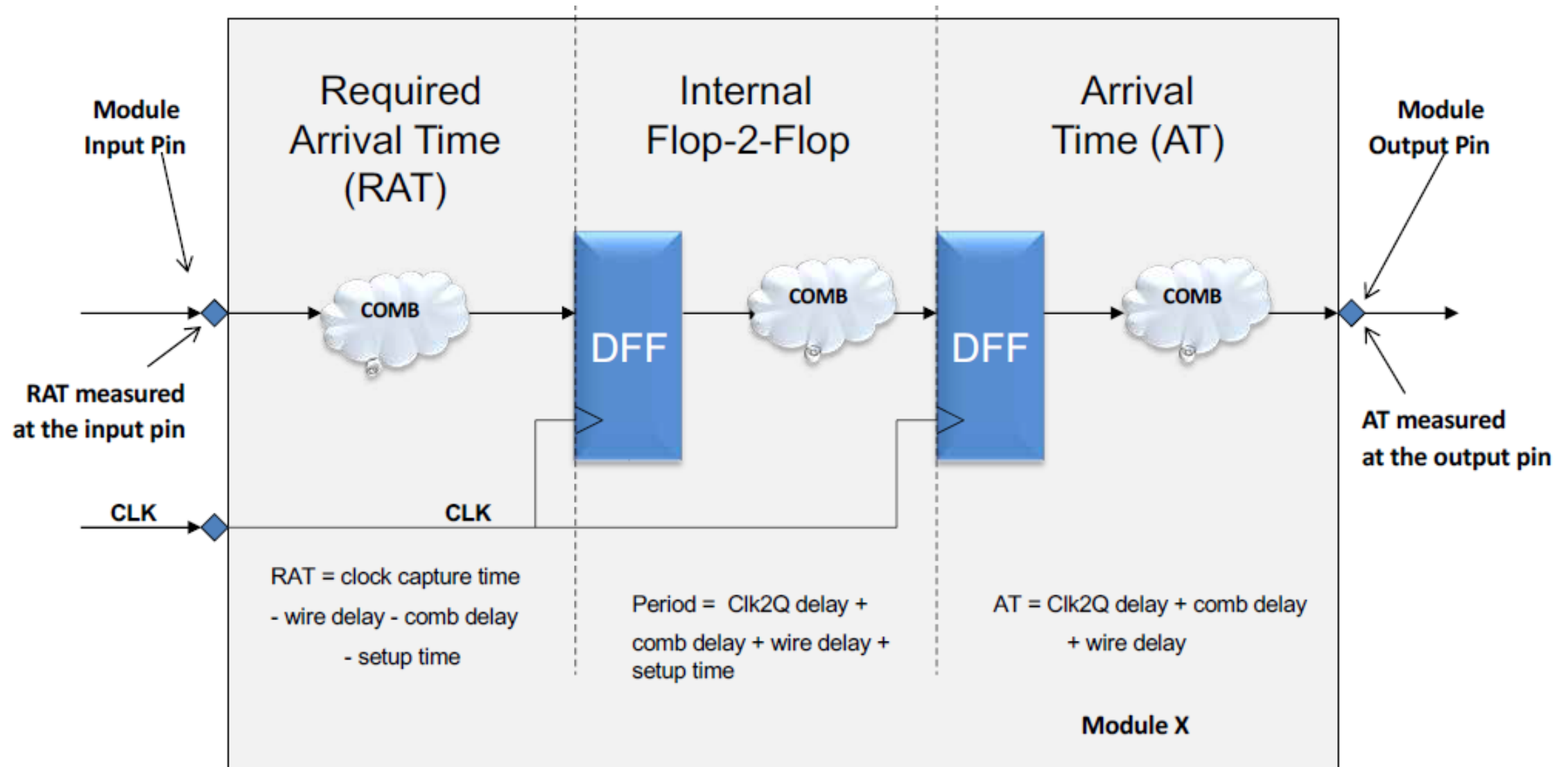


ASIC Timing

Basics of Timing




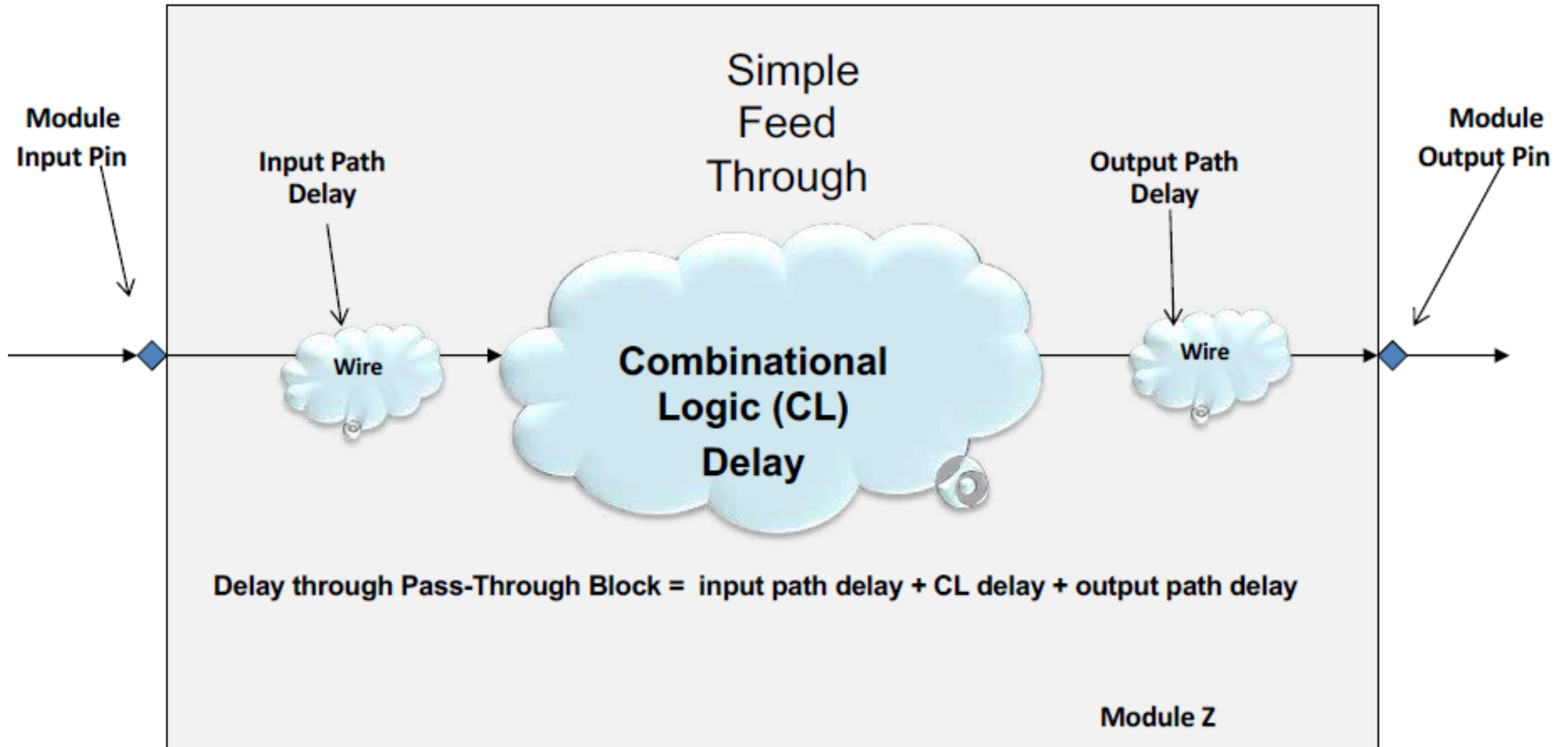


Basics of Timing: Pin-2-Pin (Pass-through)




Simple path representation

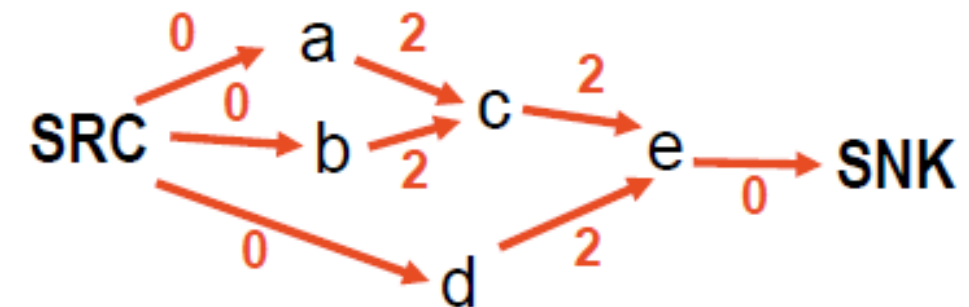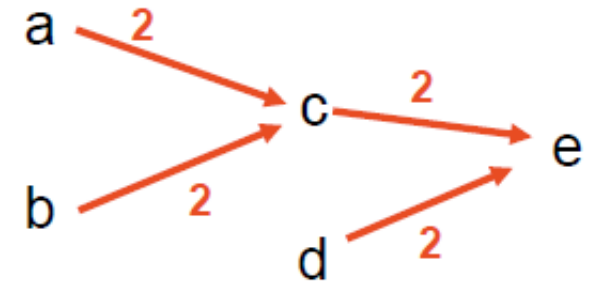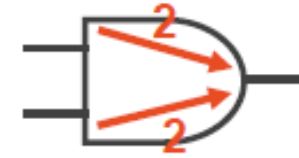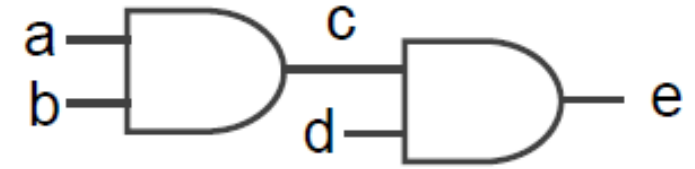- **Consider a circuit**
- Timing model of AND gate
- **Build a graph:**
 - Wires are Vertices - 1 per gate output and 1 for each PI and PO
 - Gates are Edges - input pin to output pin, 1 edge per input with a delay for each edge
 - **Add Source/Sink Nodes:**
 - 0-weight edge to each PI and from each PO.
- All paths start and end at a single node
- **Add interconnect delay – if available**



Node Oriented Timing Analysis

- Enumerate every path, number of paths get exponentially bigger
- Instead, use node-oriented timing analysis
 - For each node, find the worst delay to the node along any path
 - Define two important values:
 - Arrival Time at a node (AT): the longest path from the source to the node
 - Required Arrival Time at node (RAT): the latest time the signal is allowed to leave the node to make it to the sink in time
- **Slack at node n is defined as:**
- $\text{Slack}(n) = \text{RAT}(n) - \text{AT}(n)$

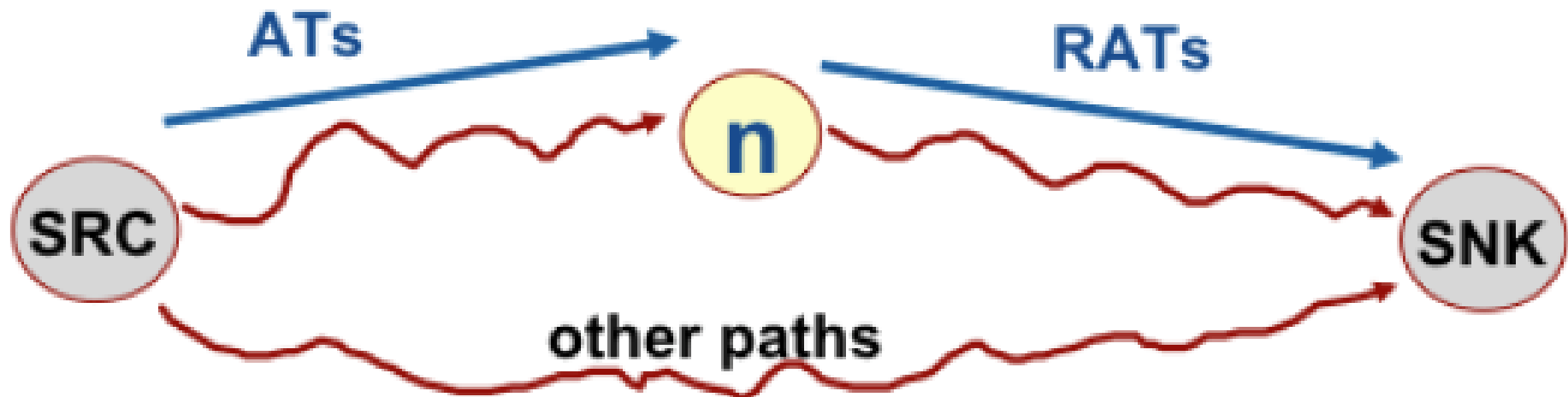


Compute ATs and RATs


- Recursively
- **Arrival Time** at a node is just the maximum of the ATs at the predecessor nodes plus the delay from that node
- **Required Arrival Time** to a node is just the minimum of the RATs at the successor nodes minus the delay to that node

$$AT(n) = \begin{cases} 0 & n = \text{SRC} \\ \max_{p \in \text{pred}(n)} [AT(p) + \Delta(p, n)] & n \neq \text{SRC} \end{cases}$$

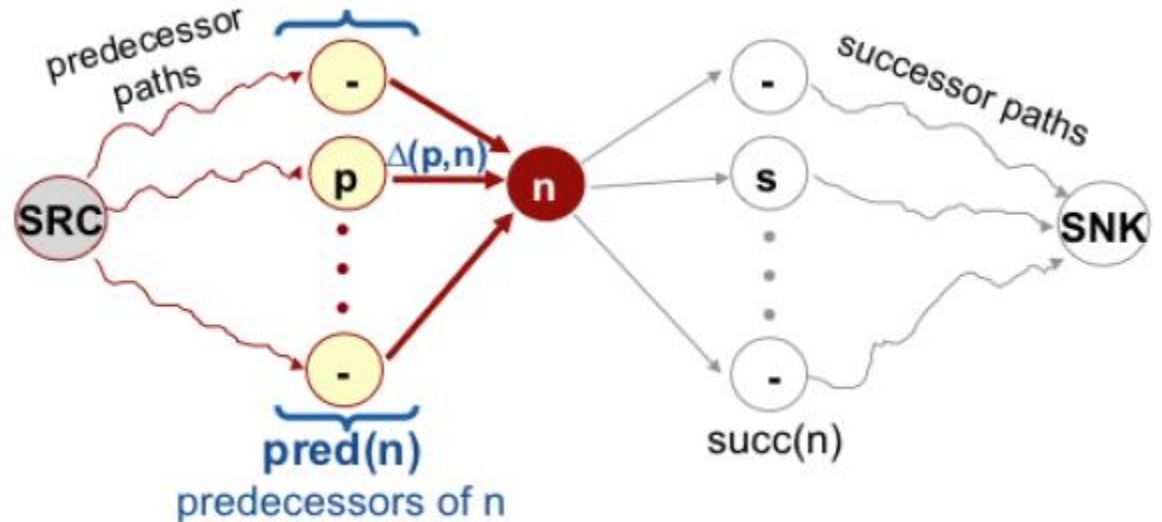
$$RAT(n) = \begin{cases} T & n = \text{SNK} \\ \max_{s \in \text{succ}(n)} [RAT(s) + \Delta(n, s)] & n \neq \text{SNK} \end{cases}$$




AT, RAT, and Slack

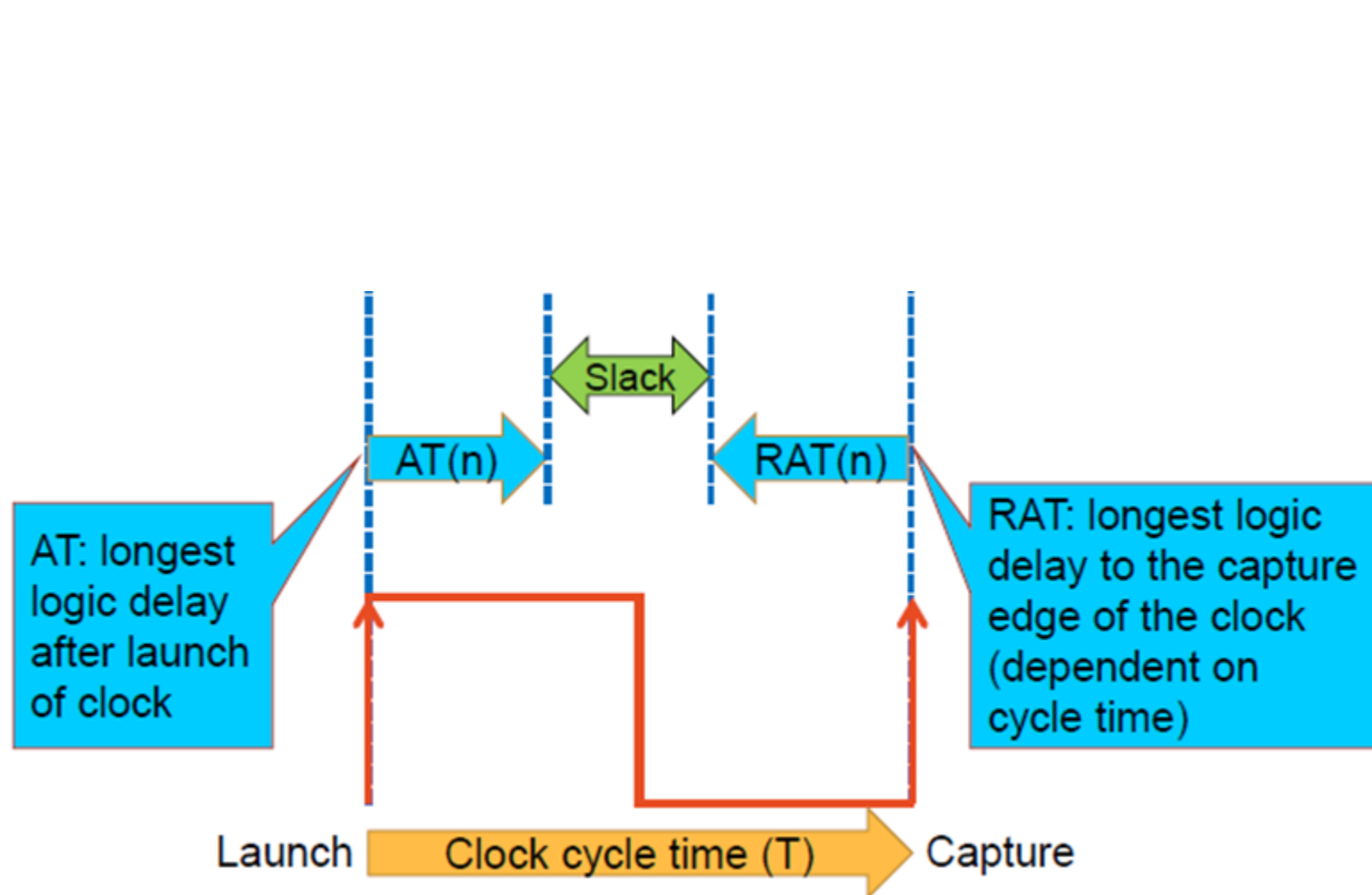

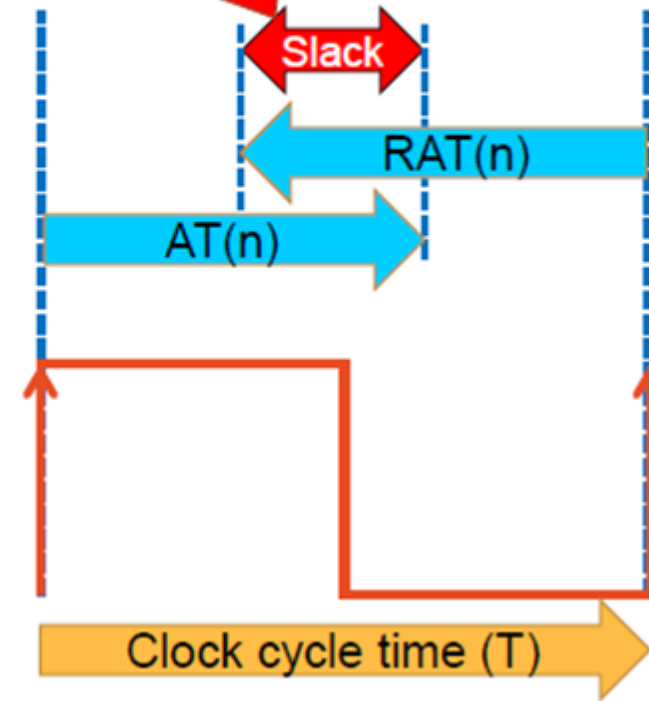If the signal arrives too late, we get *negative slack*, which means there is a timing violation.





Example

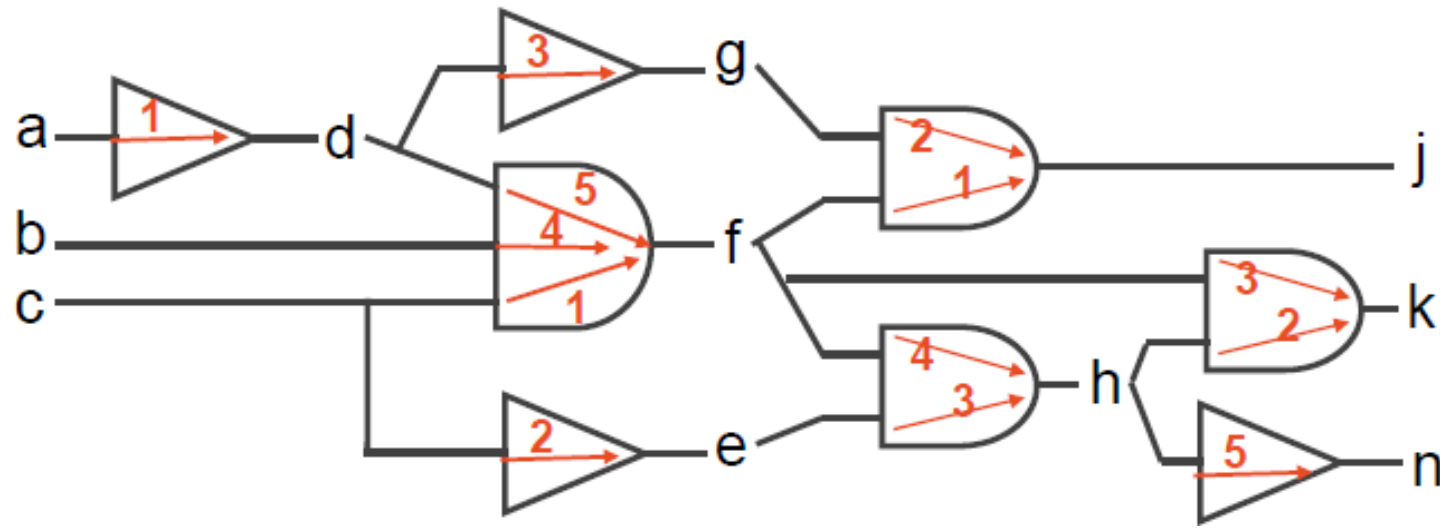

- Does it meet a cycle time of $T=12$?
- **Fill in the RAT, AT, and SLACK of each node**
 - Find out whether timing is met
 - Figure out what the worst path is

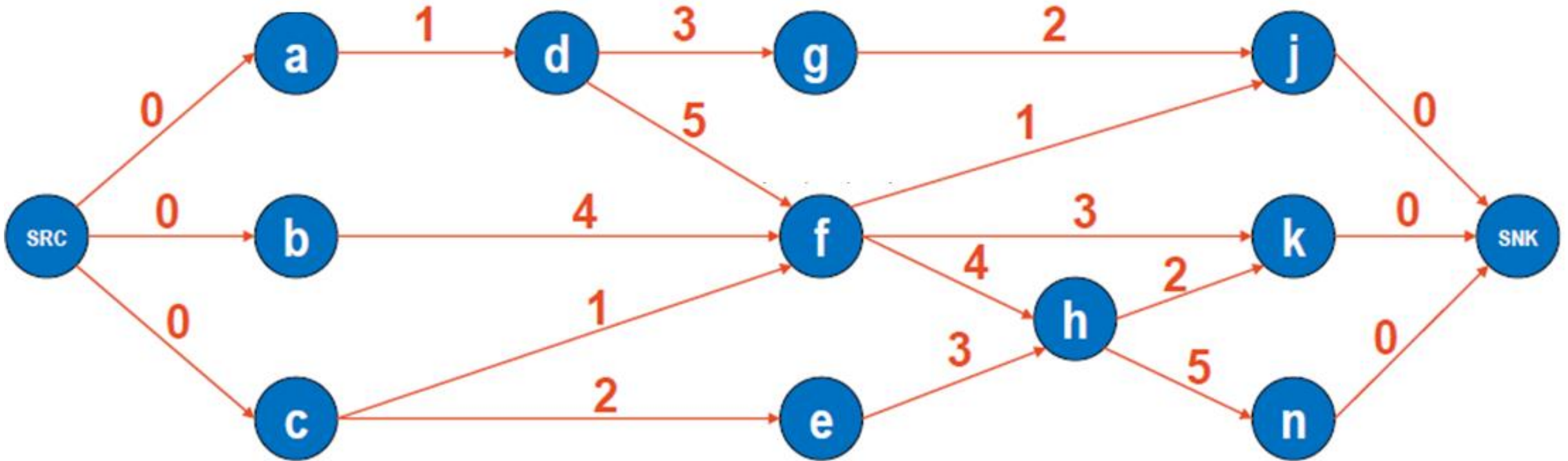
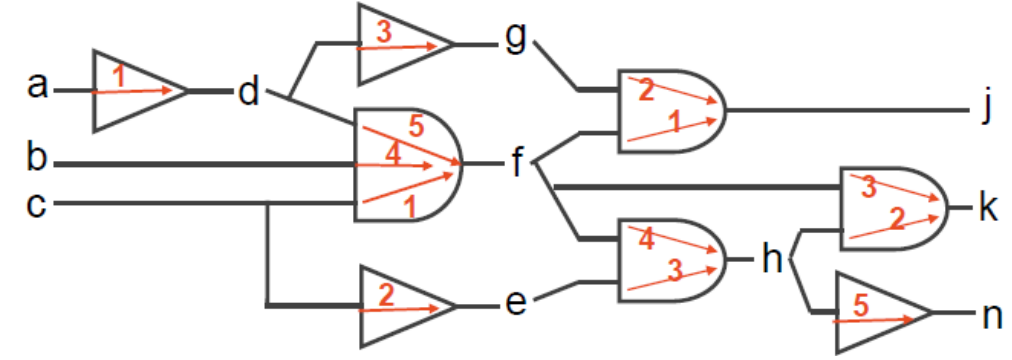
Example

- Start by representing it as a directed acyclic graph (DAG)
- Compute ATs from SRC to SNK



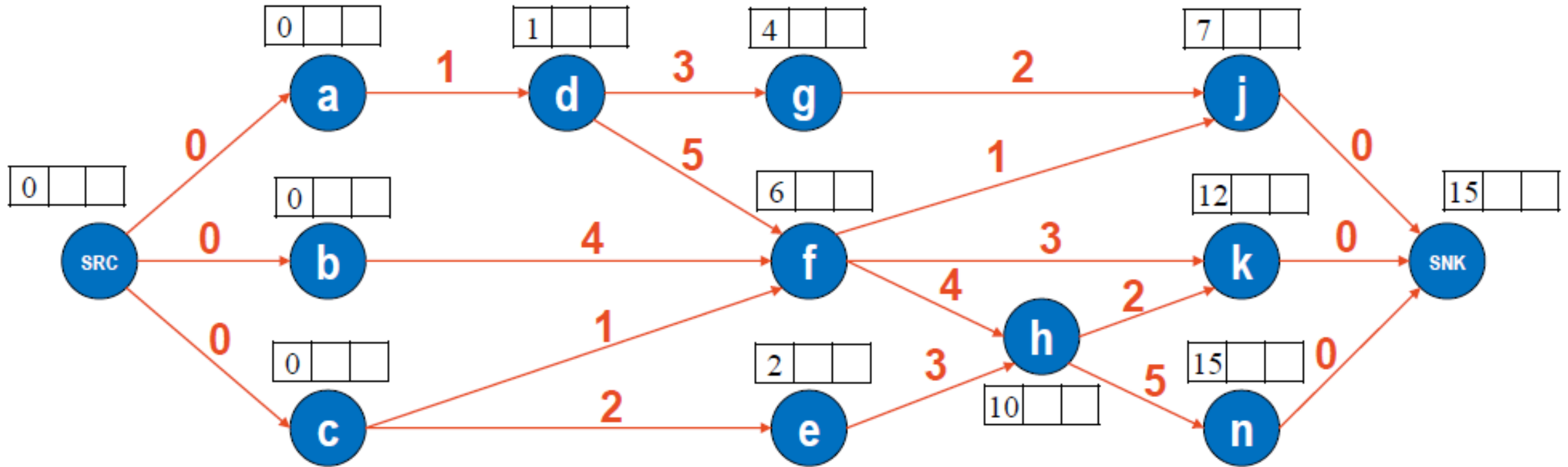
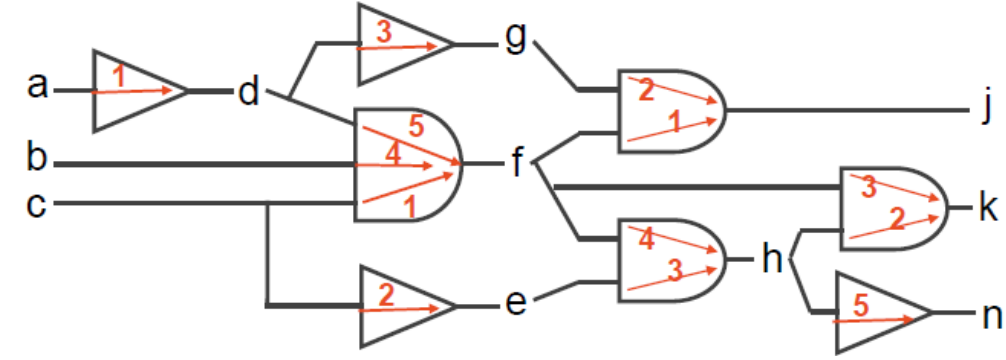
Example

- Start by representing it as a directed acyclic graph (DAG)
- Compute ATs from SRC to SNK



Example

- Add RAT to SNK from SRC

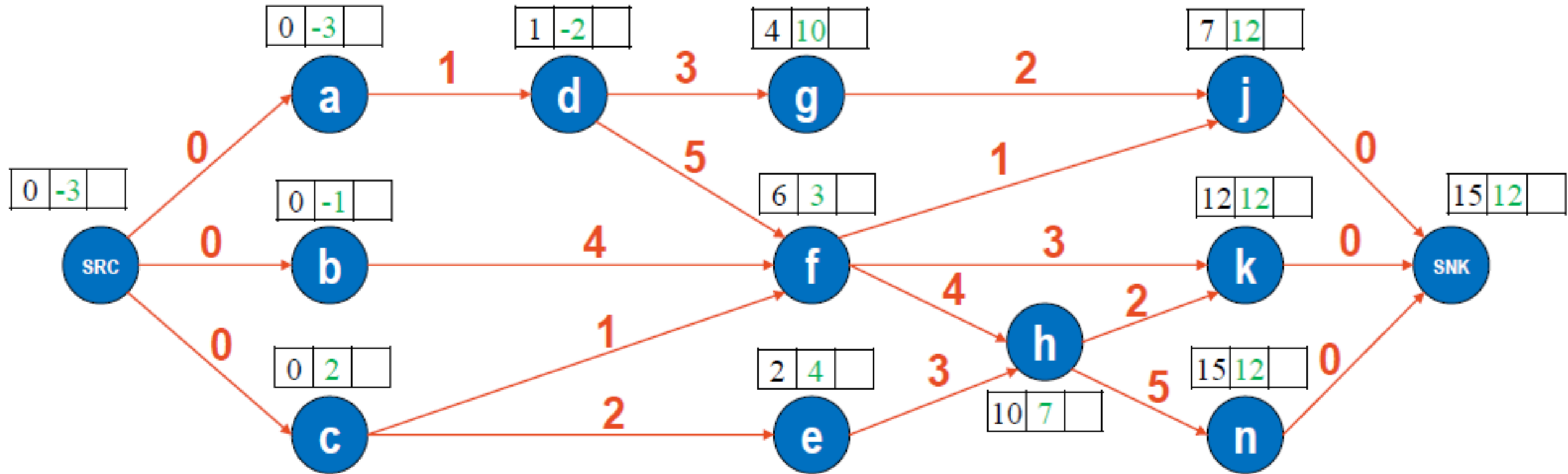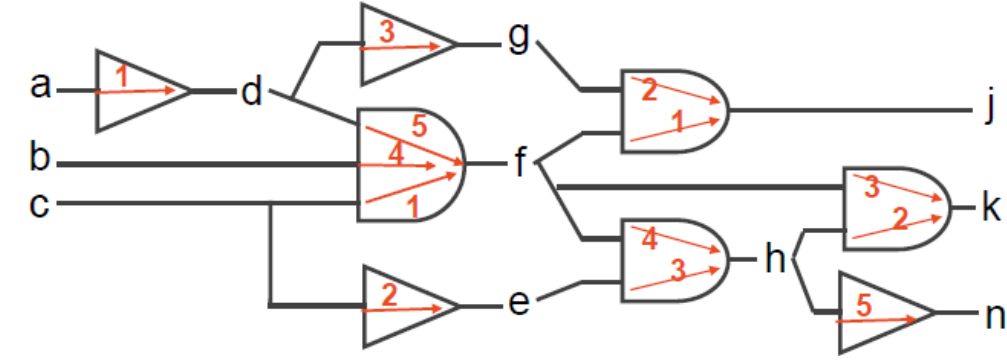

Example

- Calculate the slack - find the critical path

