



Design for Testability (DFT)



A collection of computer hardware components. At the top, there is a CRT monitor, a tower unit with a CD-ROM drive, two external speakers, a keyboard, and a mouse. Below these, there is a laptop computer. A blue arrow points from the text 'Computer Hardware' to the laptop.



DFT

- ▶ A fault is **testable** if there exists a well-specified procedure
 - ▶ (e.g., test pattern generation, evaluation, and application) to expose it, and the procedure is implementable with a reasonable cost using current technologies.
- ▶ DFT techniques improve the controllability and observability of internal nodes, so that embedded functions can be tested.
 - 1) **Controllability**, which is a measure of the difficulty of setting internal circuit nodes to 0 or 1 by assigning values to primary inputs (PIs), and
 - 2) **Observability**, which is a measure of the difficulty of propagating a node's value to a primary output (PO)
- ▶ For sequential circuits, **predictability**, which represents the ability to obtain known output values in response to given input stimuli.



Definition

- ▶ *Design for testability* (DFT) refers to those design techniques that make the task of subsequent testing easier.
- ▶ DFT methods for digital circuits:
 - ▶ Ad-hoc methods
 - ▶ Structured methods:
 - ▶ *Scan*
 - ▶ *Partial Scan*
 - ▶ *Built-in self-test* (BIST)
 - ▶ *Boundary scan*
- ▶ DFT method for mixed-signal circuits:
 - ▶ Analog test bus



Ad-Hoc DFT Methods


- ▶ Good design practices learnt through experience are used as guidelines:
 - ▶ Avoid asynchronous (unclocked) feedback.
 - ▶ Make flip-flops initializable.
 - ▶ Avoid redundant gates. Avoid large fanin gates.
 - ▶ Provide test control for difficult-to-control signals.
 - ▶ Avoid gated clocks.
 - ▶ Design reviews conducted by experts or design auditing tools.
 - ▶ Disadvantages of ad-hoc DFT methods:
 - ▶ Experts and tools not always available.
 - ▶ Test generation is often manual with no guarantee of high fault coverage.
 - ▶ Design iterations may be necessary.
-




Ad-Hoc DFT Methods

▶ Test points

 - ▶ Employ test points to increase control and observability
 - ▶ CP – Control point
 - ▶ OP – Observable point



(a)

 


(b)

Employing test points (a) Original circuit (b) Using edge pins to achieve controllability and observability


Ad-Hoc DFT Methods

▶ Test points

 - ▶ Employ test points to increase control and observability
 - ▶ CP – Control point
 - ▶ OP – Observable point



(c)

 

(d)

(c) Using a CP for 0-injection and an OP for observability


(d) Using a 0/1 injection circuit



Ad-Hoc DFT Methods

▶ Test points

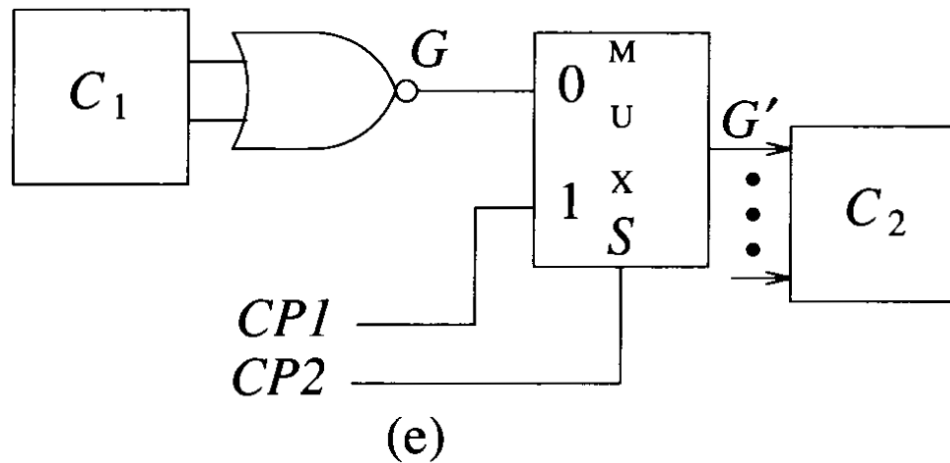- ▶ Employ test points to increase control and observability
 - ▶ CP – Control point
 - ▶ OP – Observable point




(e) Using a MUX for 0/1 injection

Ad-Hoc DFT Methods


Fault redundancy:

Error control circuitry:

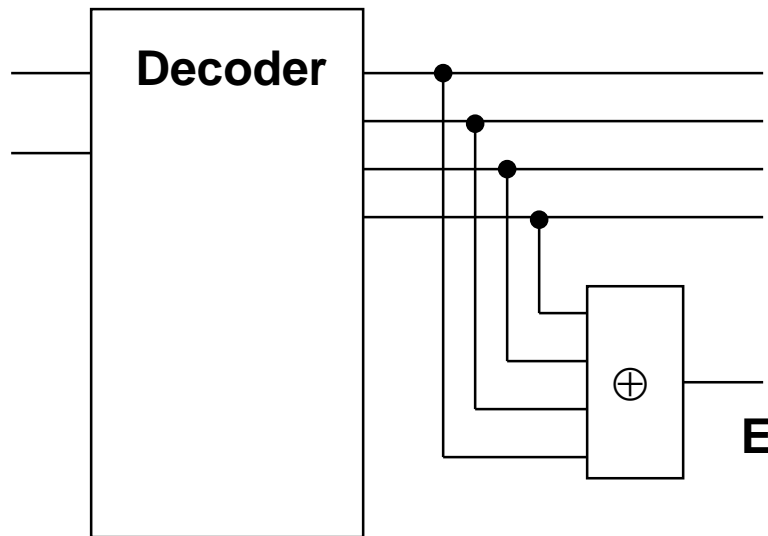

$E = 1$ if decoder is fault-free
Fault $\equiv 1$ not testable

Testable error control circuitry:

 


$T \equiv 0$ - normal working mode
 $T = 1$ - testing mode

Ad-Hoc DFT Methods


Multiplexing monitor points:

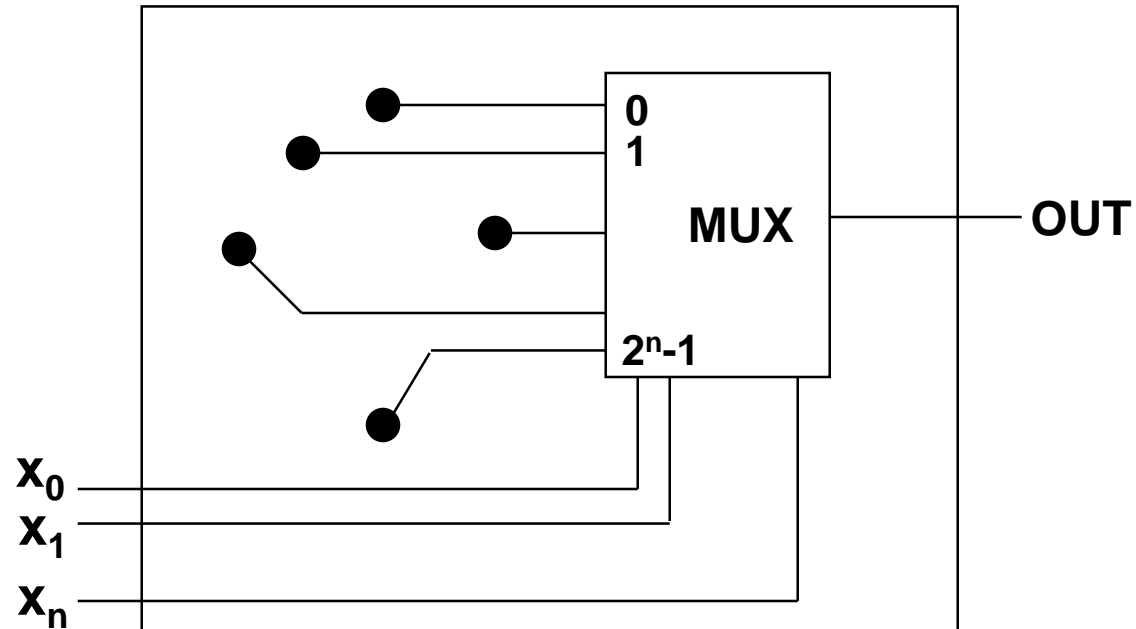- To reduce the number of output pins for observing monitor points, multiplexer can be used:
- 2^n observation points are replaced by a single output and n inputs to address a selected observation point
- Disadvantage:
- only one observation point can be observed at a time



Ad-Hoc DFT Methods

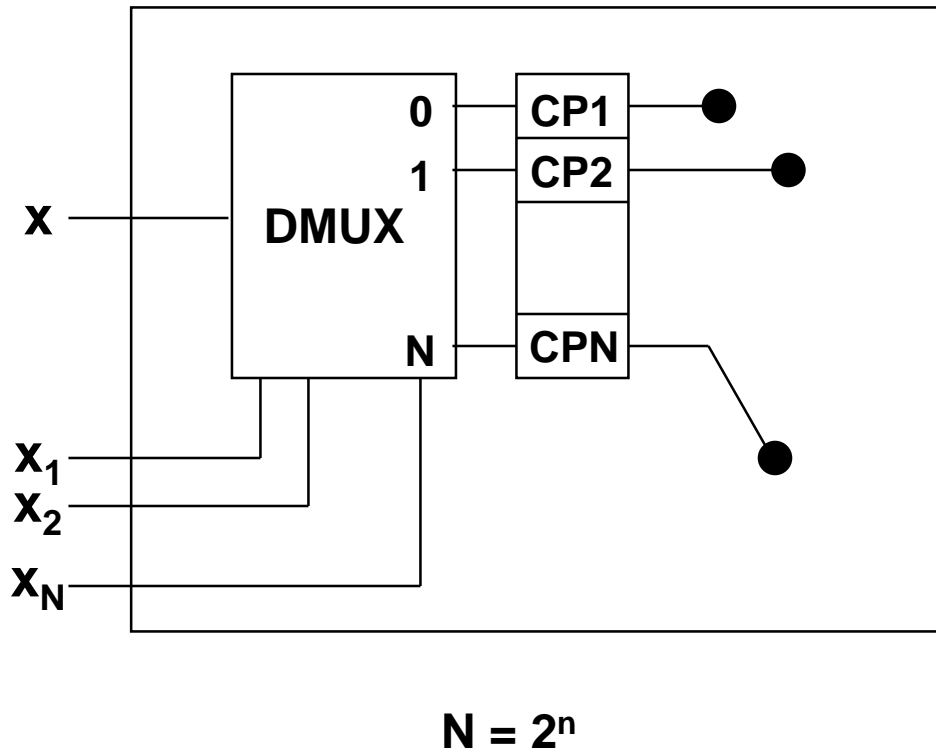De-multiplexer for implementing control points:



- To reduce the number of input pins for controlling test-points, de-multiplexer and a latch register can be used.

Scan Design

- ▶ Scan design is implemented to provide controllability and observability of internal state variables for testing a circuit.
- ▶ It is also effective for circuit partitioning.
- ▶ A scan design with full controllability and observability turns the sequential test problem into a combinational one.




Scan Design Requirements

- ▶ Circuit is designed using pre-specified design rules.
- ▶ Test structure (hardware) is added to the verified design:
 - ▶ Add a *test control* (TC) primary input.
 - ▶ Add flip-flops called as *scan flip-flops* (SFF) and connect to form one or more shift registers in the test mode.
 - ▶ Make input/output of each scan shift register controllable/observable from PI/PO.




Adding Scan Structure

 - ▶ Convert each flip-flop to a scan register
 - ▶ Only costs one extra multiplexer
- ▶ Normal mode: flip-flops behave as usual
- ▶ Scan mode: flip-flops behave as shift register



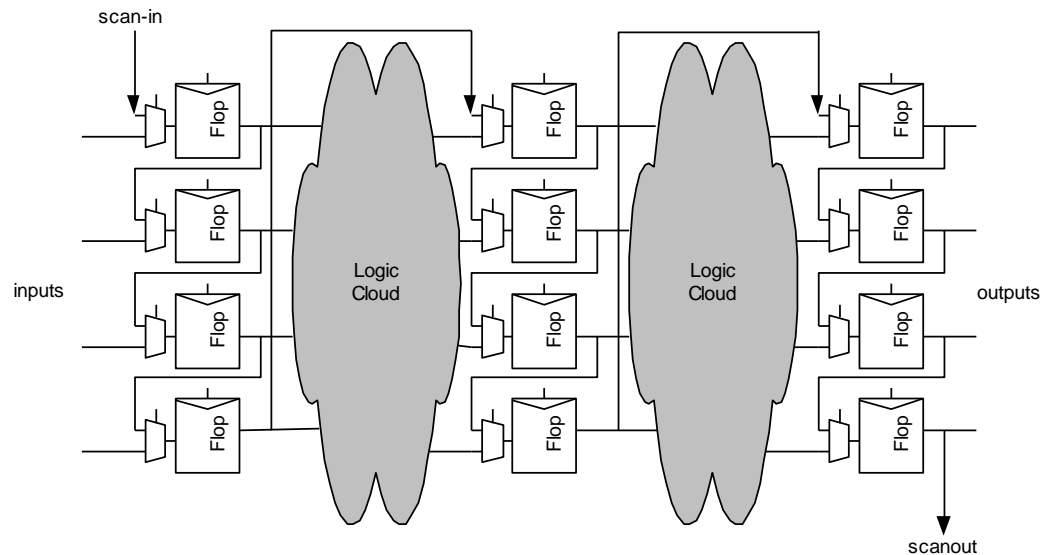- ▶ Contents of flops can be scanned out and new values scanned in




Scan Design Rules

- ▶ Use only clocked D-type of flip-flops for all state variables.
- ▶ At least one PI pin must be available for test; more pins, if available, can be used.
- ▶ All clocks must be controlled from PIs.
- ▶ Clocks must not feed data inputs of flip-flops.



Adding Scan Structure

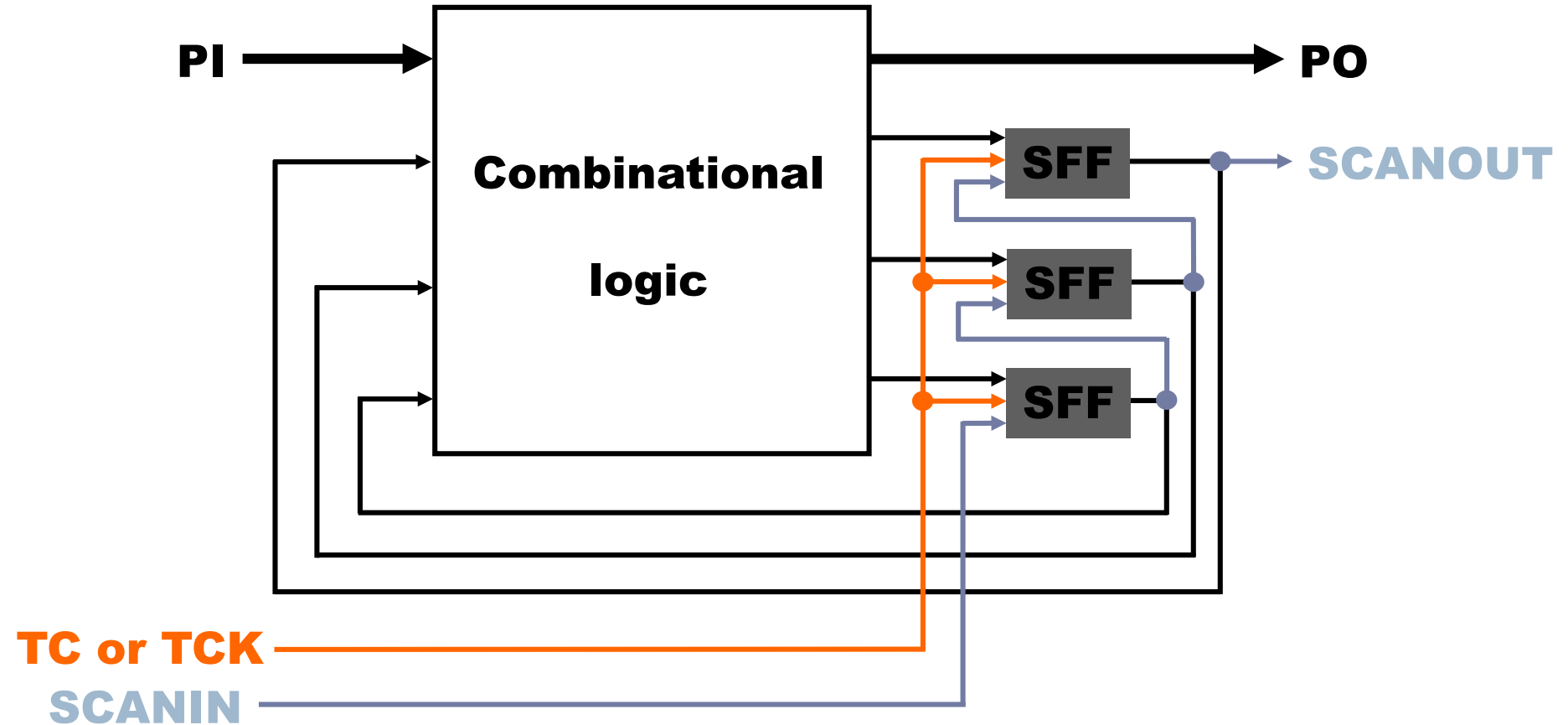

► **Built-In Self-Testing**

Pattern Generation and Response Compaction



BIST Motivation

- ▶ **Useful for field test and diagnosis**
- ▶ **Hardware BIST benefits:**
 - Lower system test effort
 - Improved system maintenance and repair
 - Improved component repair
 - Better diagnosis



Costly Test Problems Alleviated by BIST

- ▶ Increasing chip logic-to-pin ratio – harder observability
- ▶ Increasingly dense devices and faster clocks
- ▶ Increasing test generation and application times
- ▶ Increasing size of test vectors stored in ATE
- ▶ Expensive ATE needed for 1 GHz clocking chips
- ▶ Hard testability insertion – designers unfamiliar with gate-level logic, since they design at behavioral level
- ▶ *In-circuit testing* no longer technically feasible
- ▶ Shortage of test engineers
- ▶ Circuit testing cannot be easily partitioned



Economics – BIST Costs

- Chip area overhead for:
 - ▶ Test controller
 - ▶ Hardware pattern generator
 - ▶ Hardware response compacter
- Pin overhead -- At least 1 pin needed to activate BIST operation
- Performance overhead – extra path delays due to BIST
- *Yield loss* – due to increased chip area or more chips in system because of BIST
- Reliability reduction – due to increased area
- Increased BIST hardware complexity – happens when BIST hardware is made testable



BIST Benefits

► **Faults tested:**


- **Single combinational / sequential stuck-at faults**
- **Delay faults**
- **Single stuck-at faults in BIST hardware**

► **BIST benefits**

- **Reduced testing and maintenance cost**
- **Lower test generation cost**
- **Reduced storage / maintenance of test patterns**
- **Simpler and less expensive ATE**
- **Can test many units in parallel**
- **Shorter test application times**
- **Can test at functional system speed**



BIST – Forms of Testing

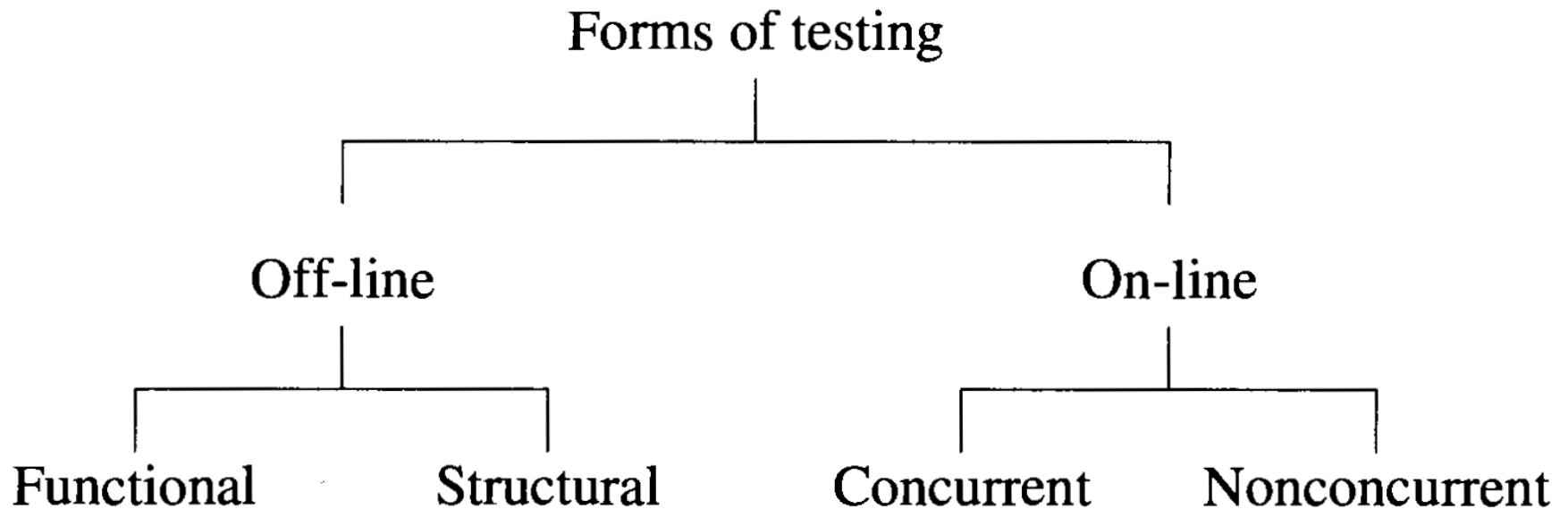


Definitions

- ▶ **BILBO** – Built-in logic block observer, extra hardware added to flip-flops so they can be reconfigured as an LFSR pattern generator or response compacter, a scan chain, or as flip-flops
 - ▶ **Concurrent testing** – Testing process that detects faults during normal system operation
 - ▶ **CUT** – Circuit-under-test
 - ▶ **Exhaustive testing** – Apply all possible 2^n patterns to a circuit with n inputs
 - ▶ **LFSR** – Linear feedback shift register, hardware that generates pseudo-random pattern sequence
 - ▶ **Signature** – Any statistical circuit property distinguishing between bad and good circuits
-



BIST Process

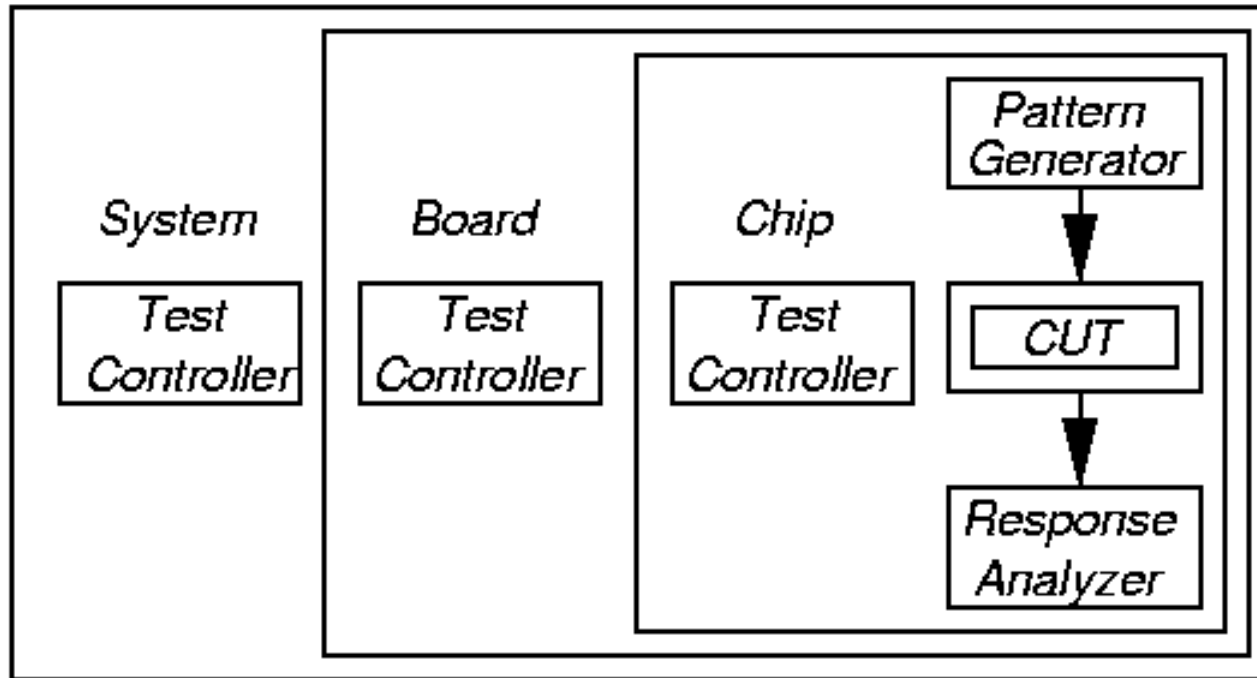

- ▶ **Test controller** – Hardware that activates self-test simultaneously on all PCBs

Pattern Generation


- ▶ **Store in ROM – too expensive**
- ▶ ***Exhaustive***
- ▶ ***Pseudo-exhaustive***
- ▶ ***Pseudo-random (LFSR) – Preferred method***



Stored patterns

- ▶ An automatic test pattern generation (ATPG) and fault simulation technique is used to generate the test patterns.
- ▶ A good test pattern set is stored in a ROM on the chip.
- ▶ When BIST is activated, test patterns are applied to the CUT and the responses are compared with the corresponding stored patterns.
- ▶ Although stored-pattern BIST can provide excellent fault coverage, it has limited applicability due to its high area overhead.

Exhaustive Pattern Generation

 


- ▶ Exhaustive pattern BIST eliminates the test generation process and has very high fault coverage.
- ▶ To test an n-input block of combinational logic, it applies all possible 2^n -input patterns to the block.
- ▶ Impractical for $n > 20$

Pseudo-Exhaustive Method

- Partition large circuit into *fanin cones*
 - Backtrace from each PO to PIs influencing it
 - Test fanin cones in parallel



Pseudo-Exhaustive Pattern Generation

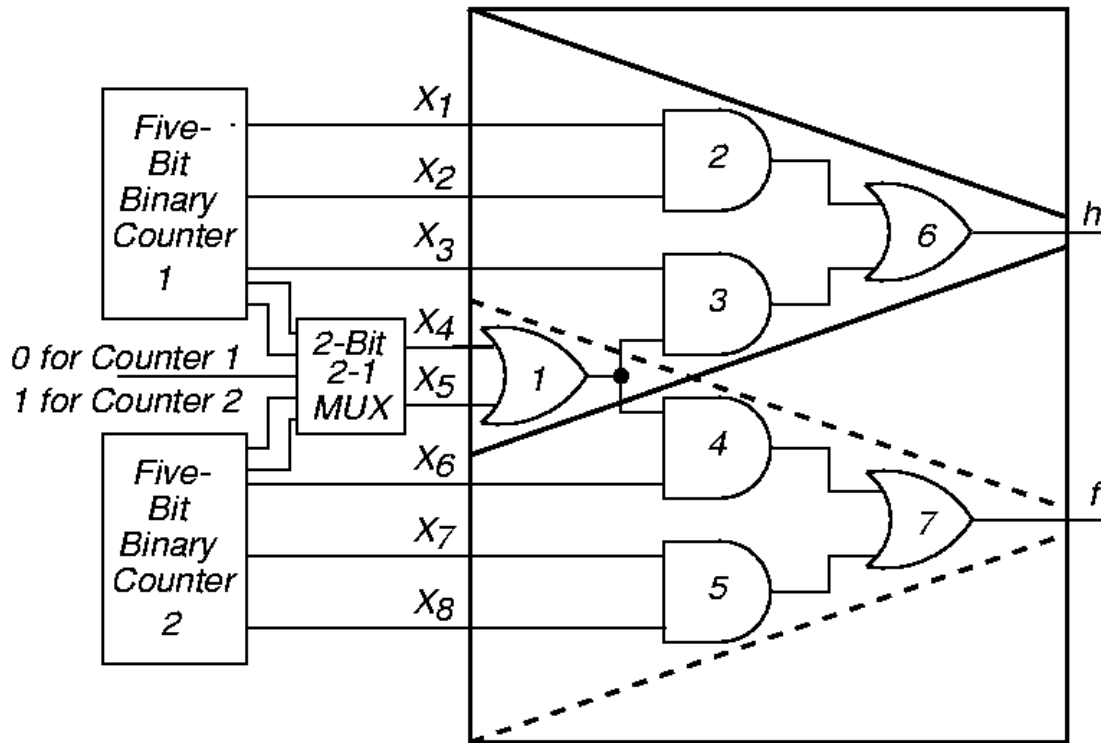

Reduced # of tests
from
 $2^8 = 256$ to $2^5 \times 2 = 64$


The total circuit is divided into two cones based on the cones of influence

Pseudo-Random Pattern Generation

- ▶ A string of 0's and 1's is called a pseudo-random binary sequence when the bits appear to be random in the local sense, but they are in some way repeatable.
- ▶ The linear feedback shift register (LFSR) pattern generator is most commonly used for pseudo-random pattern generation




Pseudo-Random Pattern Generation

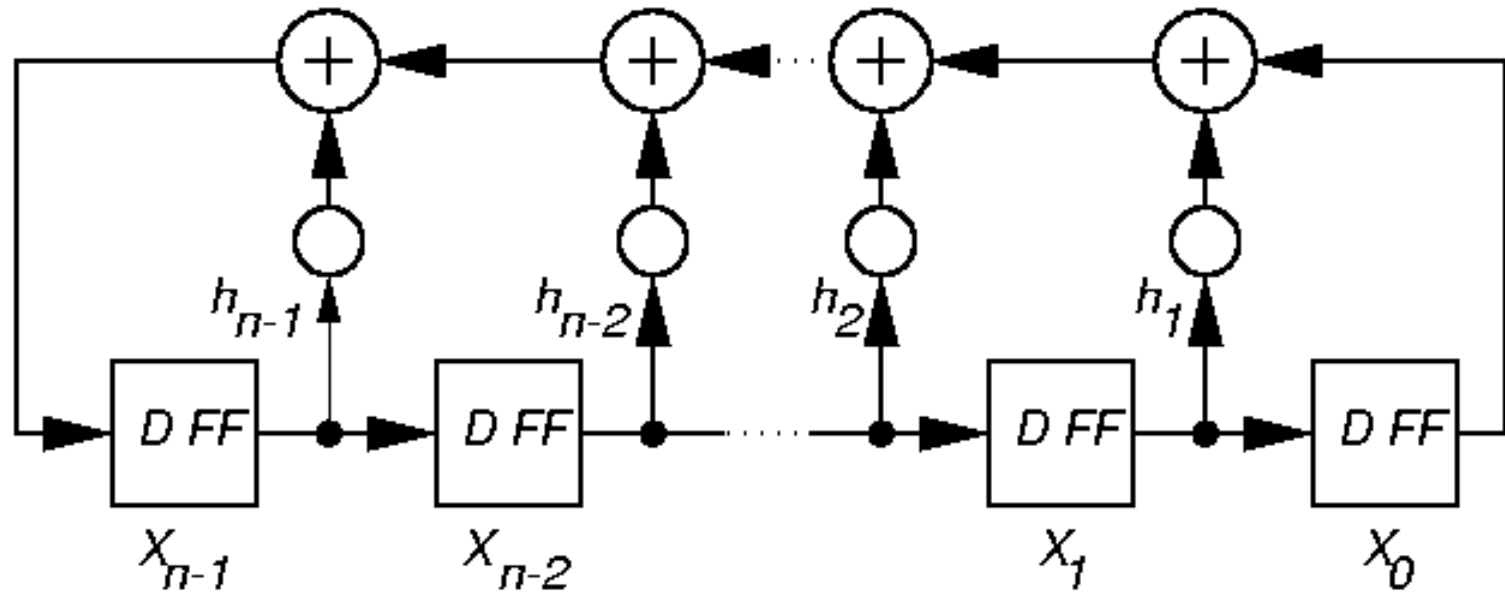

- ▶ standard, external exclusive-OR linear feedback shift register
- ▶ There are n flip-flops (X_{n-1}, \dots, X_0) and this is called n-stage LFSR
- ▶ This is known as a maximal length LFSR

LFSR Example

 

- These patterns have no obvious order, and they have certain randomness properties.
- Such a LFSR known as pseudo random pattern generator.

Modified LFSR with 0000 state

- If the all 0's test pattern is required, an n bit LFSR can be modified by adding an AND gate with n-1 inputs.
- When in state 0001, the next state is 0000; when in state 0000, the next state is 1000; otherwise the sequence is same.

