



# Fault Modeling



# Logical Fault Models

---

- ▶ Logical faults represents the effect of physical faults on the behavior of the modeled system
  - ▶ Faults that affects the logic function
  - ▶ Delay faults

# Logical Fault Models

---

- ▶ What do we gain by modeling physical faults as a logical faults?
- ▶ First
  - ▶ Fault analysis become logical
  - ▶ Complexity is greatly reduces
- ▶ Second
  - ▶ Some logical faults are technology independent, same faults model is applicable to many technologies.
  - ▶ Testing & diagnosis method developed for such faults remain valid despite changes in technology
- ▶ Third
  - ▶ Test derived for the logical faults can be used for physical faults, whose effect on circuit behavior is not completely known.

# Explicit & Implicit Faults

---

## ► Explicit fault

- A fault universe in which every fault is individually identified and hence the faults to be analyzed can be explicitly enumerated.

## ► Implicit fault

- A fault universe by collectively identifying the faults of interest – typically by defining their characteristic properties

# Structural & Functional Faults

---

- ▶ **Structural fault**

- ▶ In conjunction with structural model

- ▶ **Functional fault**

- ▶ In conjunction with functional model

# Frequent Testing Strategy

---

- ▶ Single fault assumption
- ▶ Many physical faults can affect an area containing several components
- ▶ Newly manufactured system prior to testing, multiple faults are likely to exist.
- ▶ Multiple fault - If the testing experiments does not detect the every single faults, then the circuit may contain one of the undetected faults at any time, and the occurrence of a second single faults between two testing experiments creates a multiple fault.


# Stuck at Faults

---


- ▶ Faults affecting interconnections are **short & open**
- ▶ Short
  - ▶ By connecting points not intended to be connected
- ▶ Open
  - ▶ Breaking between connections
- ▶ A short between ground or supply and a signal line can make the signal remain at a fixed logic value  $v$  ( $v \in 0,1$ ) and it is denoted by s-a-v
- ▶ A short between two signal lines usually creates a new logic function – **Bridging faults**

# Stuck faults caused by open

---

 

Single stuck faults

 

Multiple stuck faults



# Fault Detection


---

- ▶ Faults detection works by comparing the response of a known-good version of the circuit to that of the actual circuit, for a given stimulus set.
- ▶ A fault exists if there is any difference in the responses.
- ▶ One common fault detection approach is path sensitization.
- ▶ The path sensitization method, which is used by the tool to detect stuck-at faults, starts at the fault site and tries to construct a vector to propagate the fault effect to a primary output
 
# Fault Classes

---


- ▶ **Untestable (UT)**
- ▶ Untestable (UT) faults are faults for which no pattern can exist to detect them. Untestable faults cannot cause functional failures, so the tools exclude them when calculating test coverage.
- ▶ The following are the Untestable Faults.
  - ▶ **Un-used (UU)**
    - ▶ The unused fault class includes all faults on circuitry unconnected to any circuit observation point and faults on floating primary outputs.



---
 
## ► Tied (TI)


- The tied fault class includes faults on gates where the point of the fault is tied to a value identical to the fault stuck value.
- In below fig, node A is connected to GND and there assumed to be a s-a-0 fault at A.



---


- ▶ **Blocked (BL)**

 - ▶ The blocked fault class includes faults on circuitry for which tied logic blocks all paths to an observable point


 
# Redundant Fault

- ▶ The redundant fault class includes faults that test generator considers undetectable.
- ▶ After the test pattern generator exhausts all patterns, it performs a special analysis to verify that the fault is undetectable under any conditions.




Undetectable if Y is s-a-0
 
# Fault Modeling

---

- ▶ The effects of physical defects
- ▶ Most commonly used fault model: **Single stuck-at fault**



**A s-a-1 B s-a-1 C s-a-1 D s-a-1**

**A s-a-0 B s-a-0 C s-a-0 D s-a-0**

**E s-a-1 F s-a-1 G s-a-1**


**E s-a-0 F s-a-0 G s-a-0**

**14 faults**

# Fault Coverage (FC)

$$FC = \frac{\text{\# faults detected}}{\text{\# faults in fault list}}$$

**Example:**

 

**6 stuck-at faults**  
(  $a_0, a_1, b_0, b_1, c_0, c_1$  )

Test	faults detected	FC
$\{(0,0)\}$	$c_1$	16.67%
$\{(0,1)\}$	$a_1, c_1$	33.33%
$\{(1,1)\}$	$a_0, b_0, c_0$	50.00%
$\{(0,0), (1,1)\}$	$a_0, b_0, c_0, c_1$	66.67%
$\{(1,0), (0,1), (1,1)\}$	all	100.00%

# Fault Modeling

---

- ▶ Single stuck at faults
  - ▶ S @ 0
  - ▶ S @ 1
- ▶ Bridge fault
- ▶ Multiple stuck at faults




# Single stuck at fault

---

## Fault free expression

$$Z1 = x1.x2$$

$$Z2 = x2.x3$$

 

# Single stuck at fault - s@0

---

## Fault free expression


$$Z1 = x1.x2$$

$$Z2 = x2.x3$$

## Faulty expression

$$Z1 = 0$$

$$Z2 = x2.x3$$

 

# Single stuck at fault - s@1

---

## Fault free expression


$$Z1 = x1.x2$$

$$Z2 = x2.x3$$

## Faulty expression

$$Z1 = x2$$

$$Z2 = x2.x3$$

 

# Single stuck at fault - bridge fault

---

## Fault free expression


$$Z1 = x1.x2$$

$$Z2 = x2.x3$$

## Faulty expression


$$Z1 = (x1+x2).x2 = x2$$

$$Z2 = x2.x3$$

 

# Fault Simulation Terminologies


---

 

a:SA0 propagates




a:SA0 is blocked

 

a:SA0 is not activated
 
# Fault Detection

- ▶ For a single output circuit, a test  $t$  that detects a fault  $f$  makes  $Z(t) = 0$  and  $Z_f(t) = 1$  or vice-versa.
- ▶ Thus set of all tests that detect  $f$  is given by the solutions of the equation
  - ▶  $Z(x) \text{ XOR } Z_f(x) = 1$



$$Z = (x_2 + x_3)x_1 + \bar{x}_1 x_4$$

Let  $f$  be  $x_4$  s-a-0.


$$Z_f = (x_2 + x_3)x_1$$

$$\bar{x}_1 x_4 = 1.$$

**Thus any test in which  $x_1 = 0$  and  $x_4 = 1$  is a test for  $f$ .  
any of the four tests (0001, 0011, 0101, 0111) that detect  $f$ .**
 
# Fault Equivalence

- ▶ **Fault equivalence:** Two faults  $f1$  and  $f2$  are equivalent if all tests that detect  $f1$  also detect  $f2$ .
- ▶ If faults  $f1$  and  $f2$  are equivalent then the corresponding faulty functions are identical.



- AND bridging fault of  $x, y$  is functionally equivalent to  $z$  s-a-0








# Fault Collapsing

---

- ▶ With any  $n$  input gate we have  $2(n+1)$  stuck at faults
  - ▶ For a 2 input nand gate all the input s-a-0 is equivalent to output s-a-1.
- ▶ This type of reduction of set of faults to be analyzed based on the equivalence relations is called equivalence fault collapsing




# Equivalence Rules

       


- Need to consider only  $n+2$  stuck at faults.

# Equivalence Example

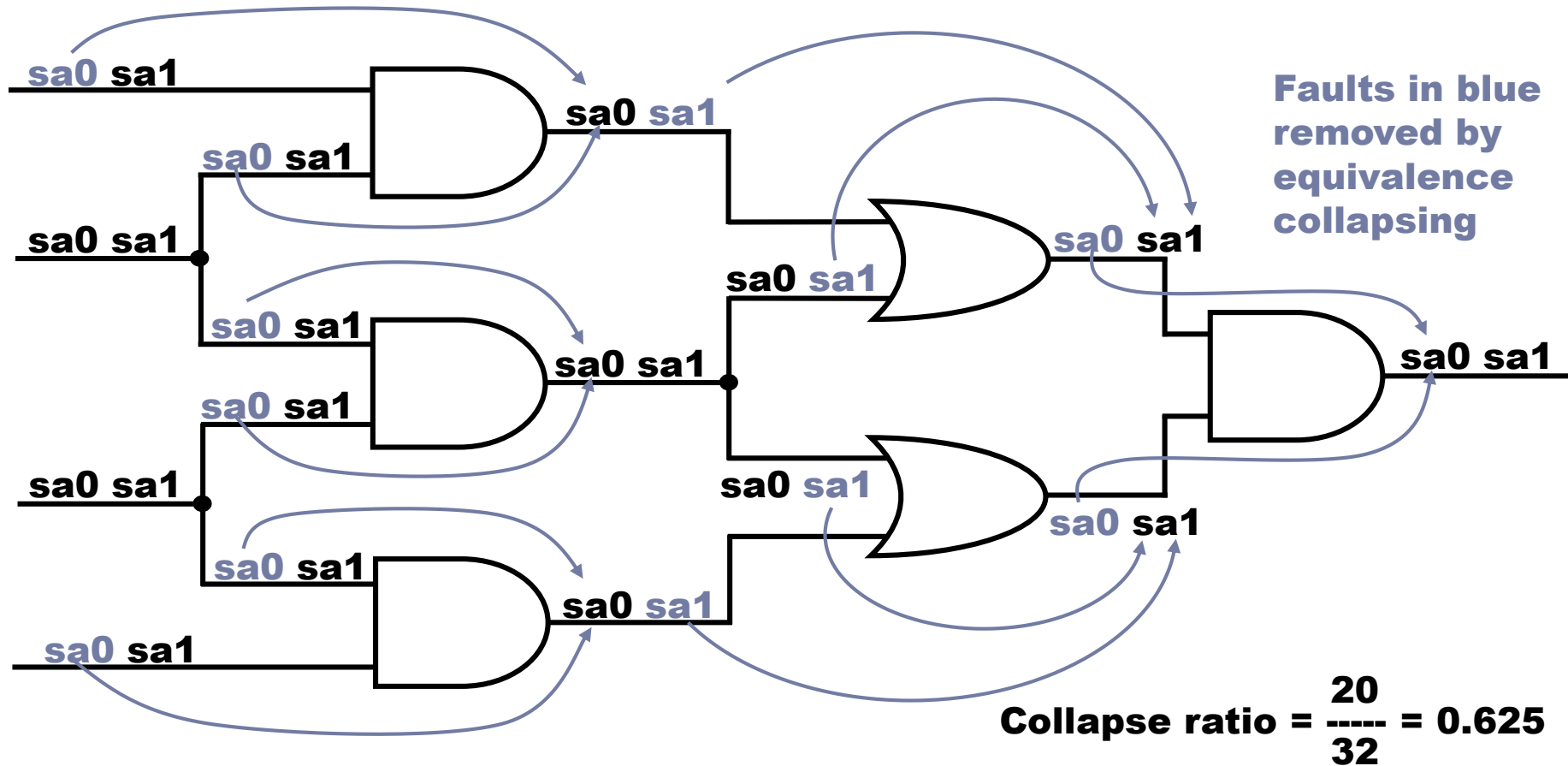
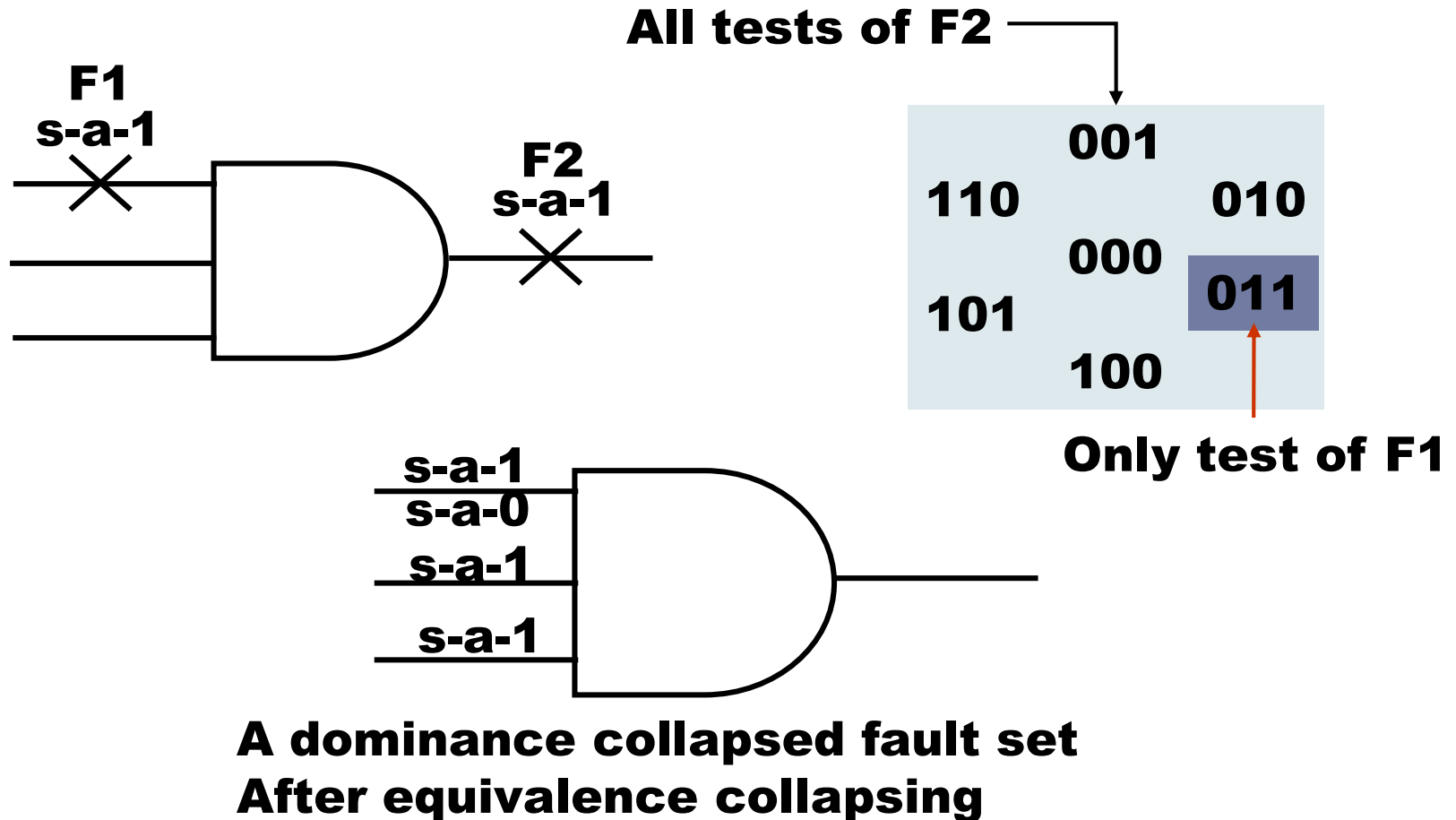
# Dominance Example

In a tree circuit (without fanouts) PI faults form a dominance collapsed fault set.




# Fault Dominance

---

- ▶ If all tests of fault F2 detects another fault F1, then F1 dominates F2.
- ▶ **Dominance fault collapsing:** If fault F2 dominated by F1, then F2 is removed from the fault list.
- ▶ When dominance fault collapsing is used, it is sufficient to consider only the input faults of Boolean gates
- ▶ If two faults dominate each other then they are equivalent.

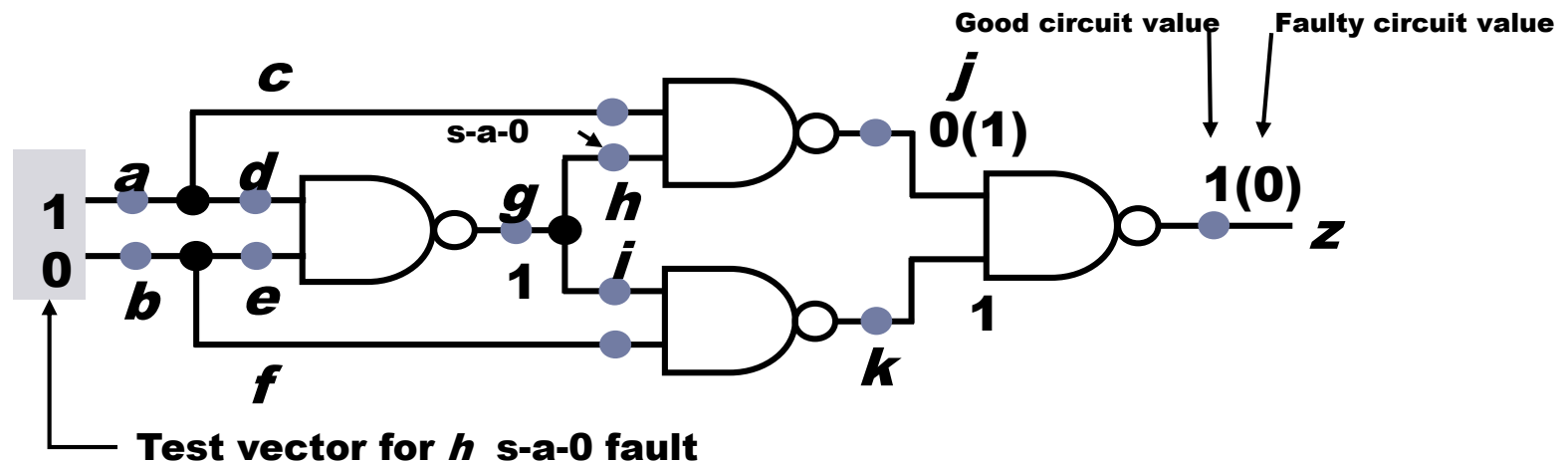
# Single Stuck-at Fault Model

- ▶ Three properties define a single stuck-at fault
  - ▶ Only one line is faulty
  - ▶ The faulty line is permanently set to 0 or 1
  - ▶ The fault can be at an input or output of a gate
- ▶ Example: XOR circuit has 12 fault sites (●) and 24 single stuck-at faults



 
# Checkpoints

- ▶ Primary inputs and fanout branches of a combinational circuit are called **checkpoints**.
- ▶ **Checkpoint theorem:** A test set that detects all single (multiple) stuck-at faults on all checkpoints of a combinational circuit, also detects all single (multiple) stuck-at faults in that circuit.




**Total fault sites = 16**

**Checkpoints (●) = 10**

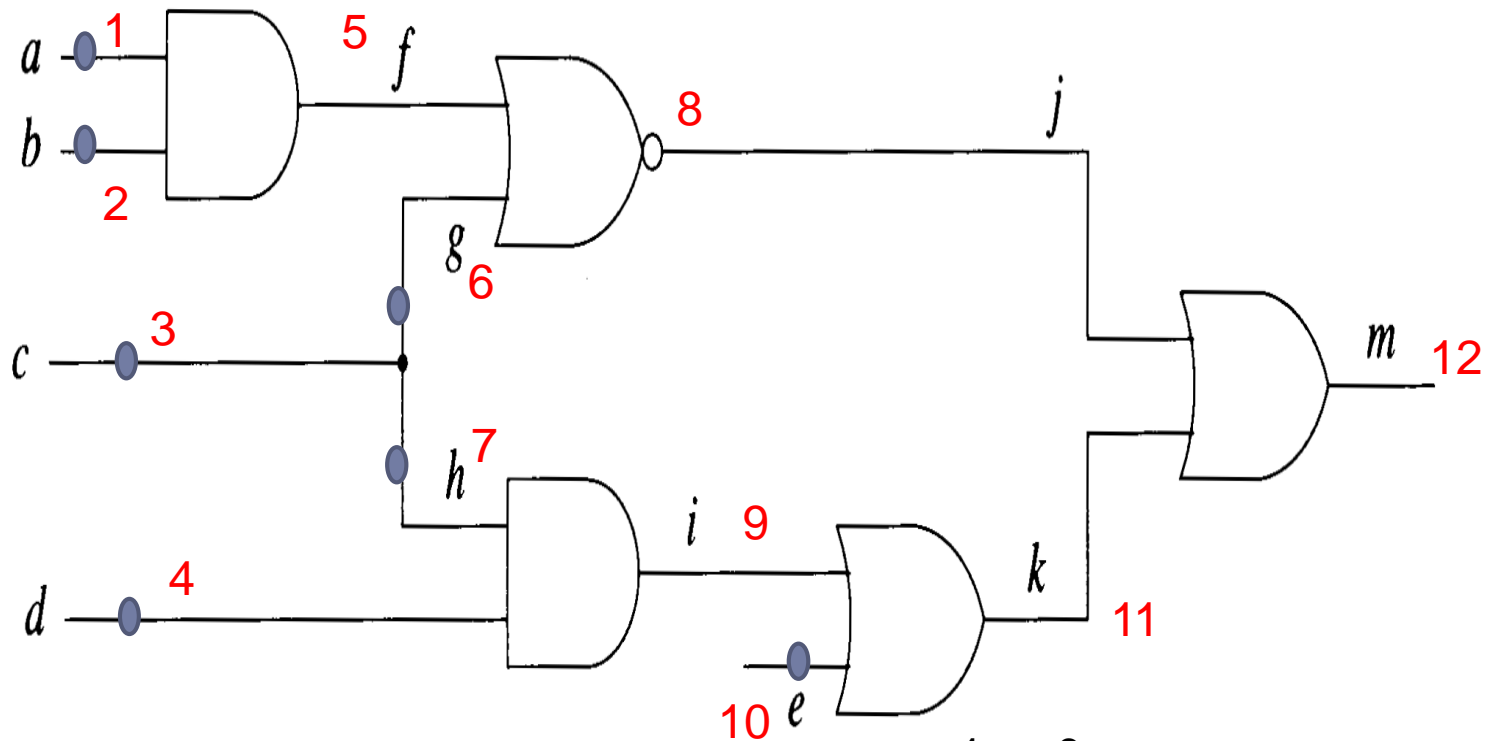

- 12 fault sites – 24 stuck at faults
- 7 Checkpoints

- |       |        |
|-------|--------|
| 1. a0 | 9. e0  |
| 2. a1 | 10. e1 |
| 3. b0 | 11. g0 |
| 4. b1 | 12. g1 |
| 5. c0 | 13. h0 |
| 6. c1 | 14. h1 |
| 7. d0 |        |
| 8. d1 |        |

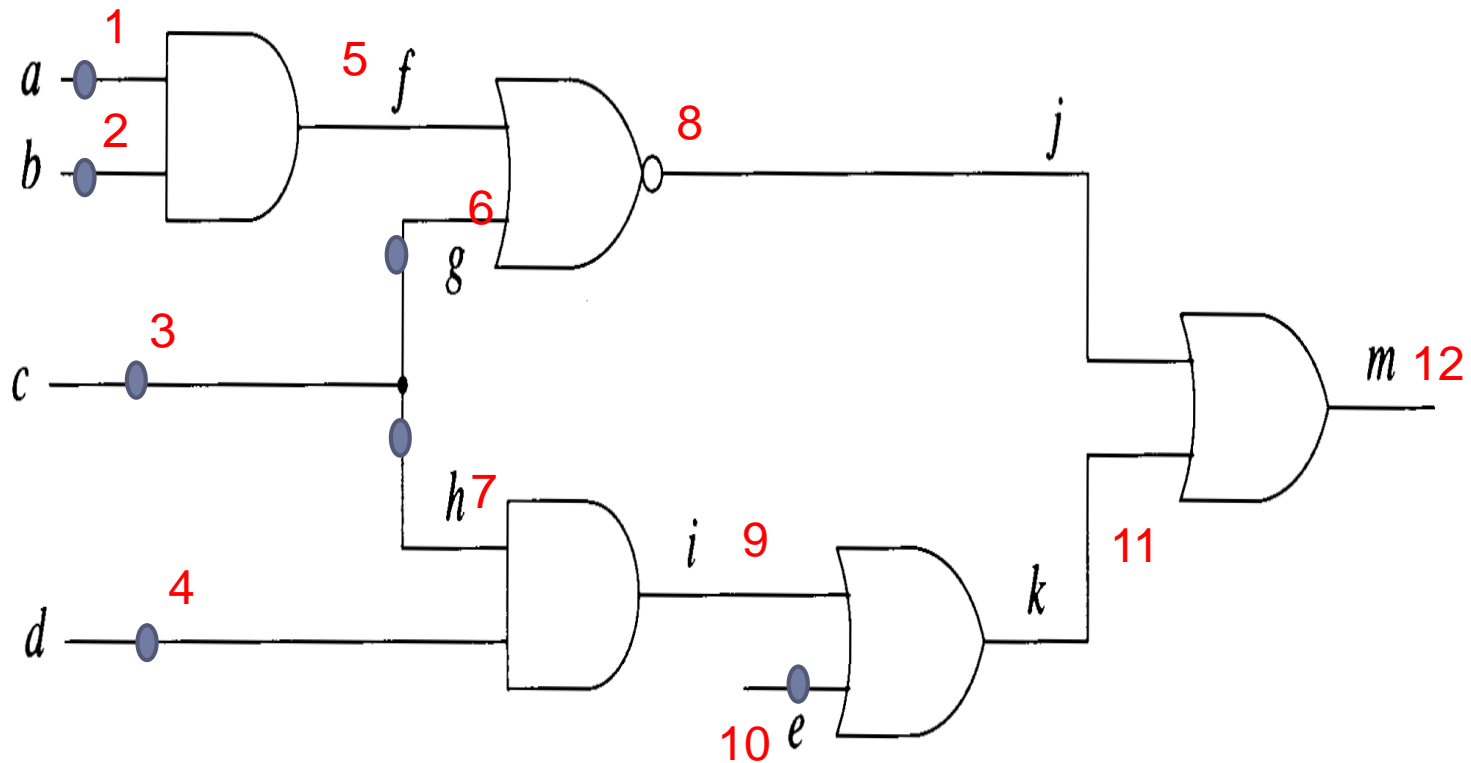

- Input  $a$  s-a-0 and  $b$  s-a-0 are equivalent – remove  $b$  s-a-0
- Input  $d$  s-a-0 equivalent to  $h$  s-a-0, remove it
- $g$  s-a-1 equivalent to  $f$  s-a-1, which dominates  $a$  s-a-1, so remove it
- $e$  s-a-1 equivalent to  $i$  s-a-1, which dominates  $h$  s-a-1, so remove it
- *Number of faults reduced from 24 to 10*



# Assignment

---

- ▶ Current (or IDDQ) and Very Low-level Voltage (VLV) test