

Datapath Functional Units

Contents

- Comparator
- Funnel Shifter
- Multi Input Adder
- Multiplier
- Divider

Introduction


- Data path
 - Consists of functional units where all computations are carried out
 - Ex: Registers, multiplexers, bus, adders, multipliers, counter
- Control path
 - Consists of FSM and provide control signals to the data path in proper sequence
 - With the help of control signals various operations are carried out by the data path
 - Also takes inputs from the data path regarding status information

Introduction

- Illustrate data and control path
 - $P = Q + R$
 - $S = P - R$


Multiplication by repeated addition

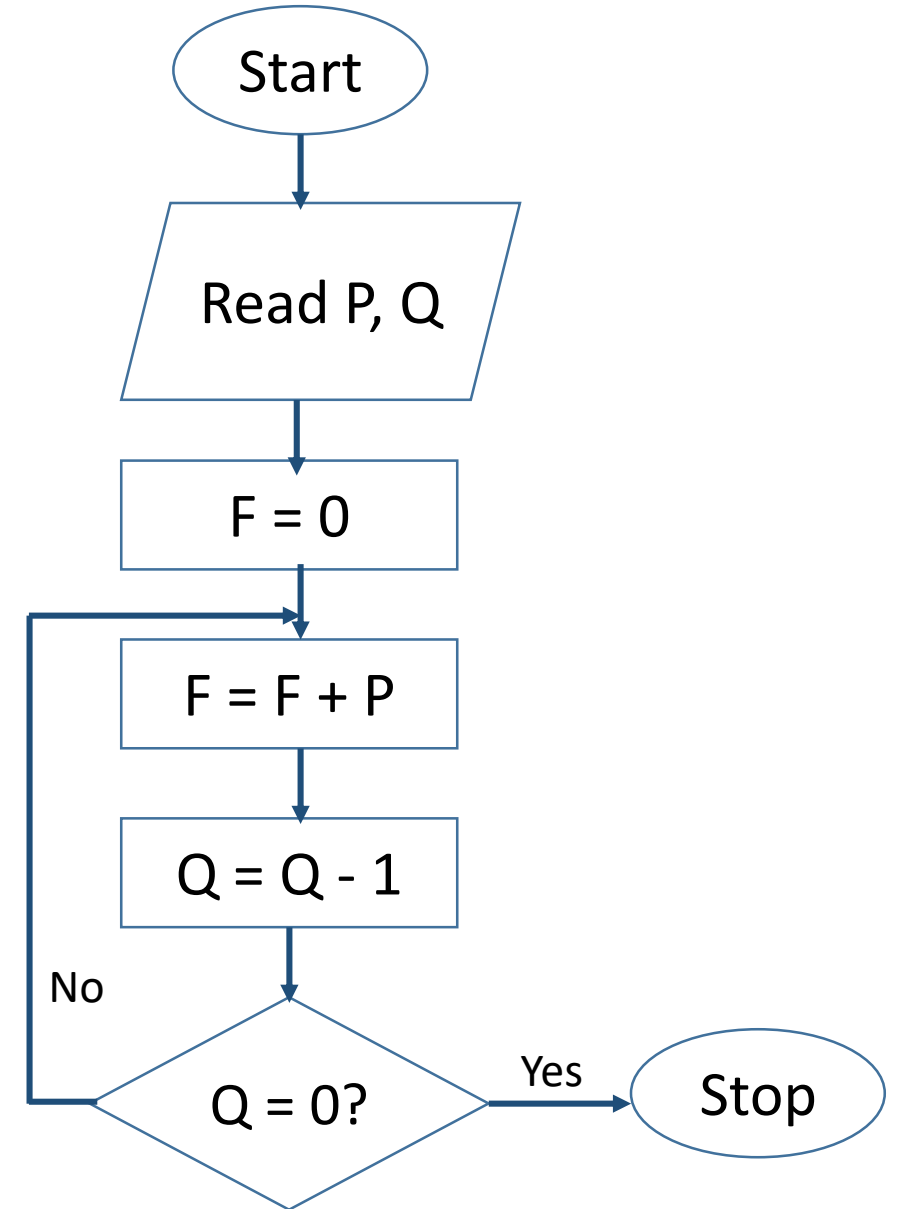- Illustrate $P * Q$ by repeated addition
- Assumption, Q is not zero
- Identify the functional blocks
- Design the FSM to implement the algorithm with the help of data path




Multiplication by repeated addition

- Data Path

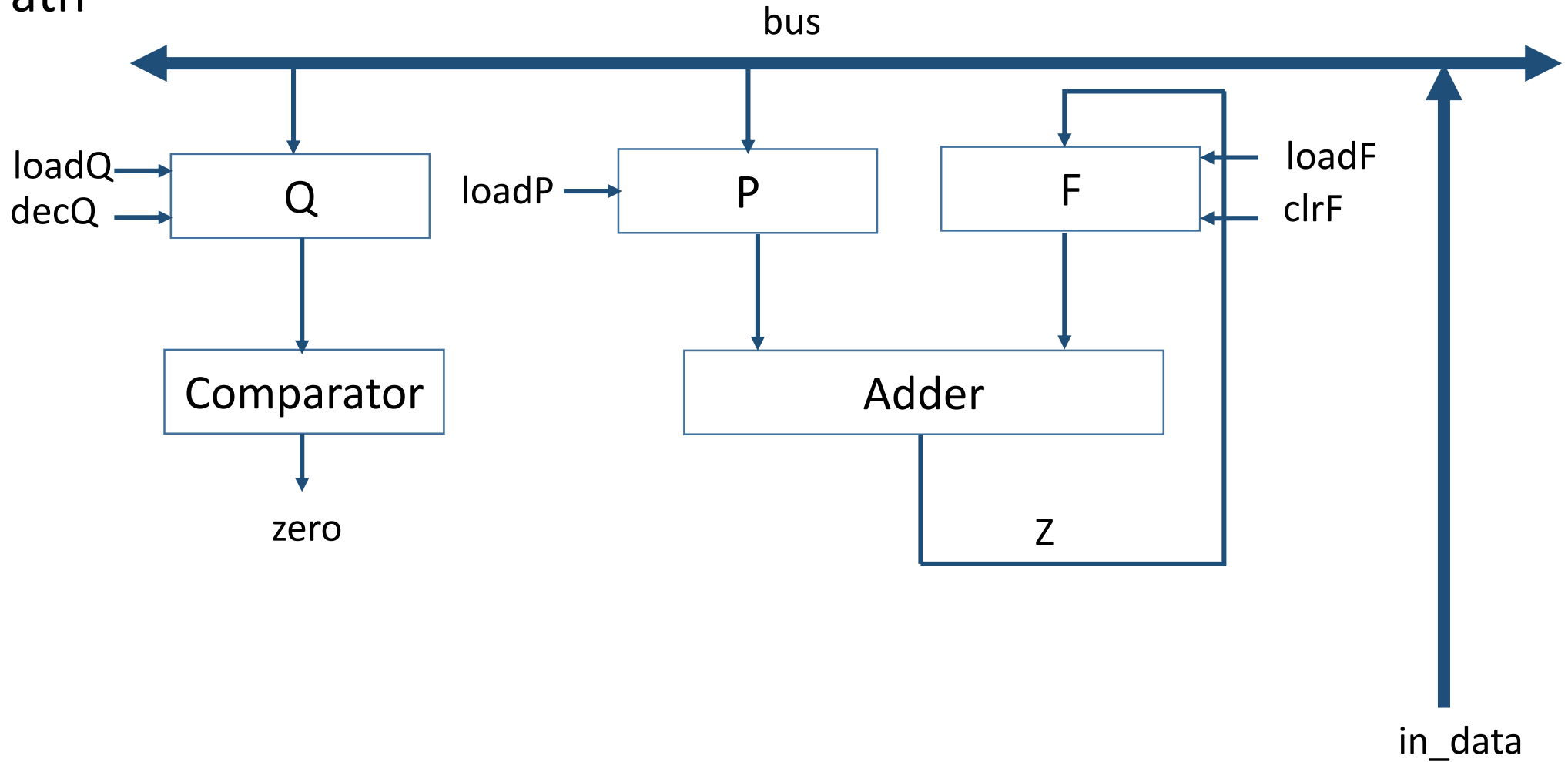



Multiplication by repeated addition

- Block Diagram

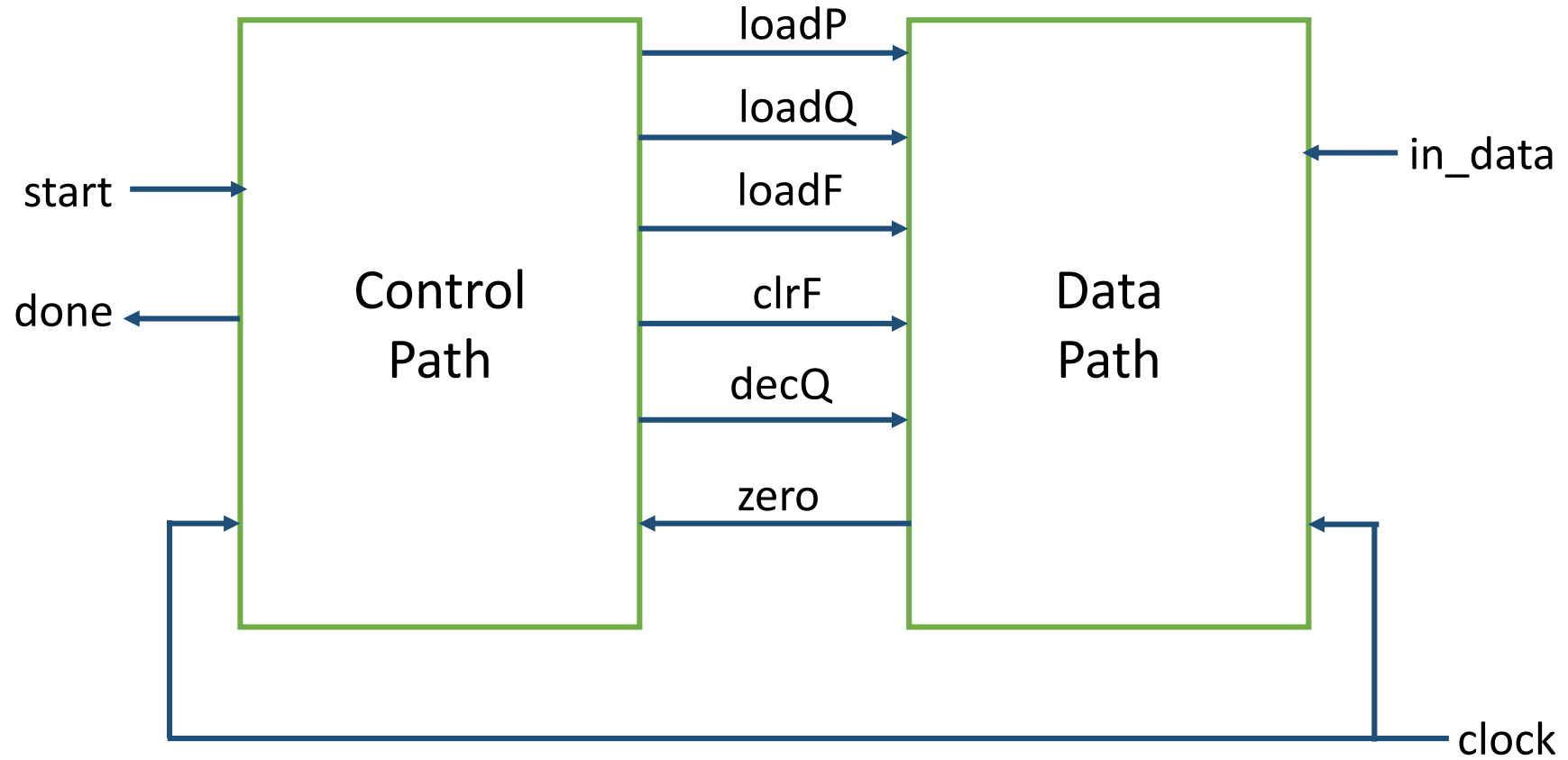

Multiplication by repeated addition

- Control Path

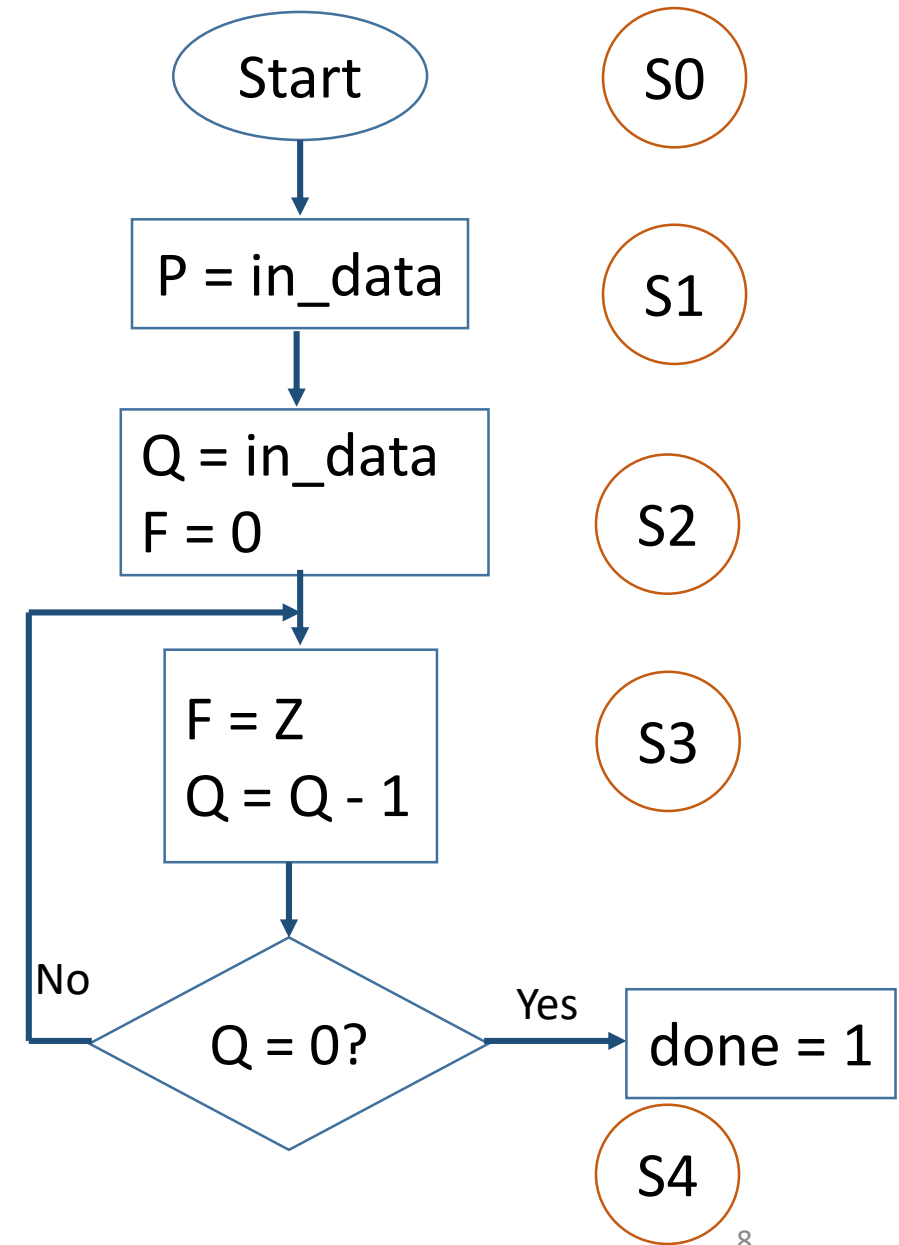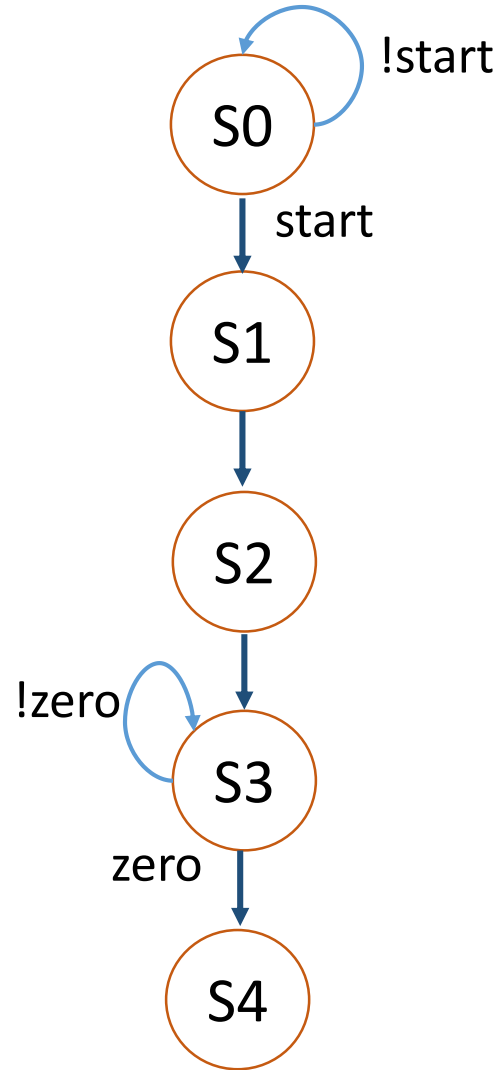

Multiplication by repeated addition

- Write HDLs and simulate

