

Datapath Functional Units

Contents

- Comparator
- Funnel Shifter
- Multi Input Adder
- Multiplier
- Divider

Introduction


- Data path
 - Consists of functional units where all computations are carried out
 - Ex: Registers, multiplexers, bus, adders, multipliers, counter
- Control path
 - Consists of FSM and provide control signals to the data path in proper sequence
 - With the help of control signals various operations are carried out by the data path
 - Also takes inputs from the data path regarding status information

Introduction

- Illustrate data and control path
 - $P = Q + R$
 - $S = P - R$


Multiplication by repeated addition

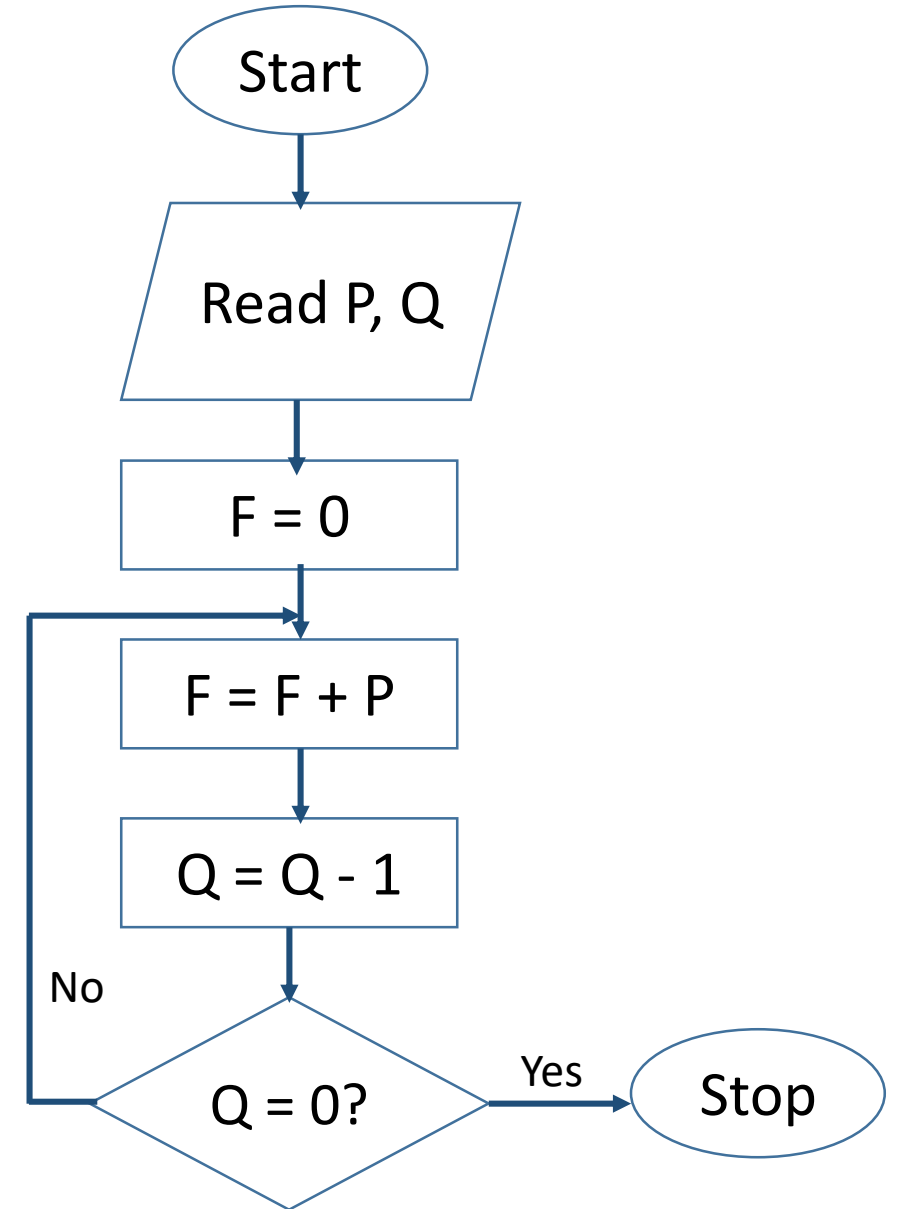- Illustrate $P * Q$ by repeated addition
- Assumption, Q is not zero
- Identify the functional blocks
- Design the FSM to implement the algorithm with the help of data path




Multiplication by repeated addition

- Data Path

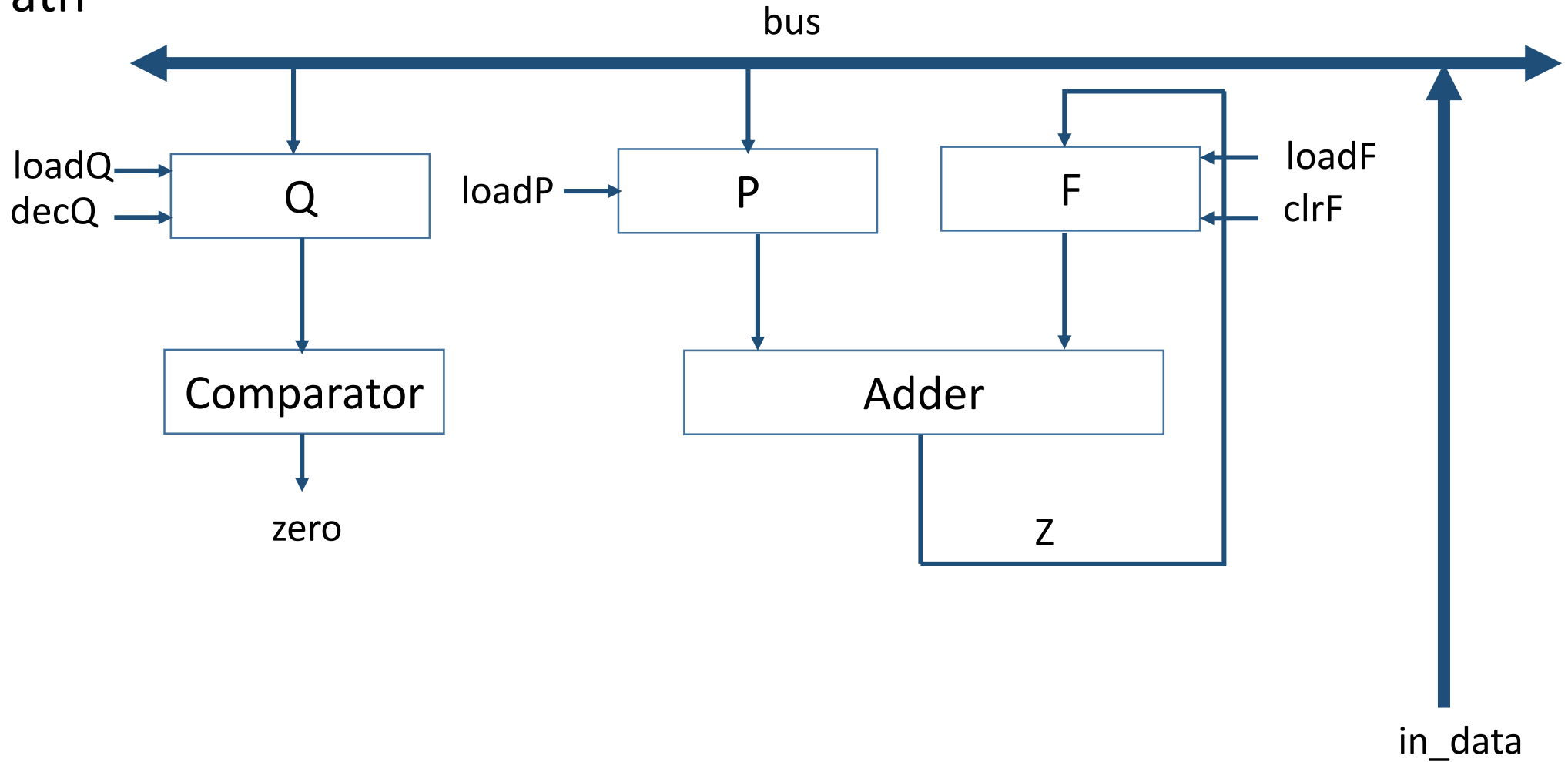



Multiplication by repeated addition

- Block Diagram

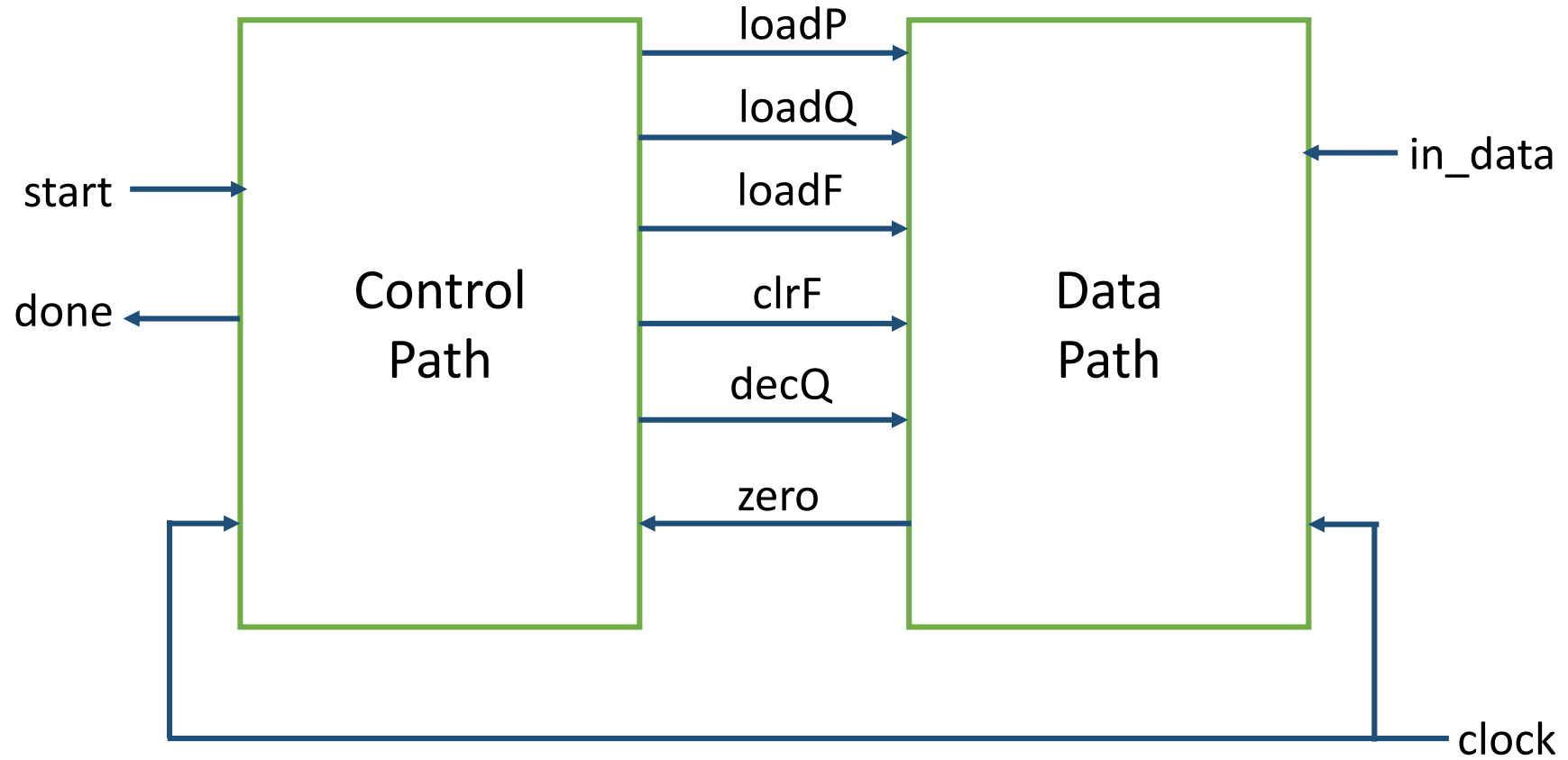


Multiplication by repeated addition

- Control Path

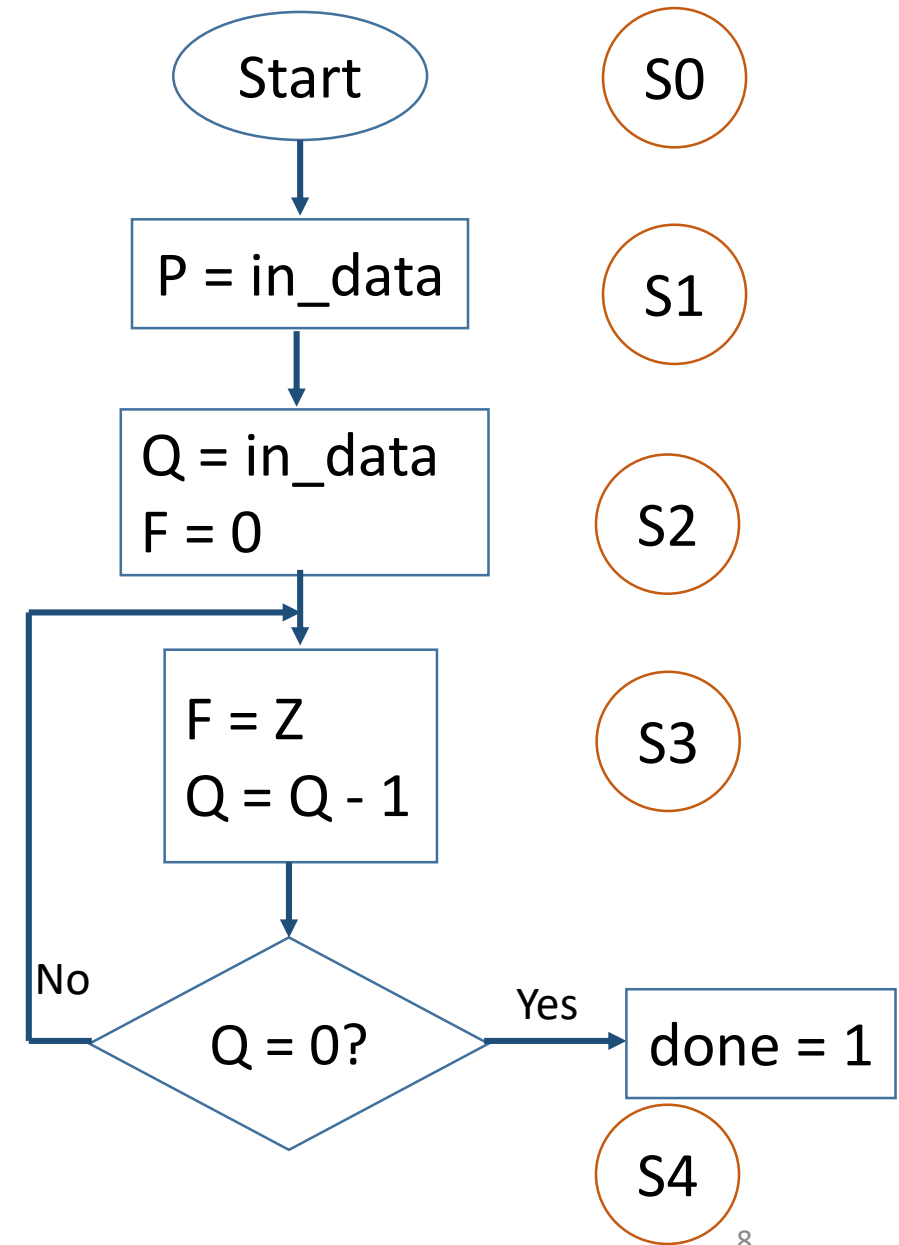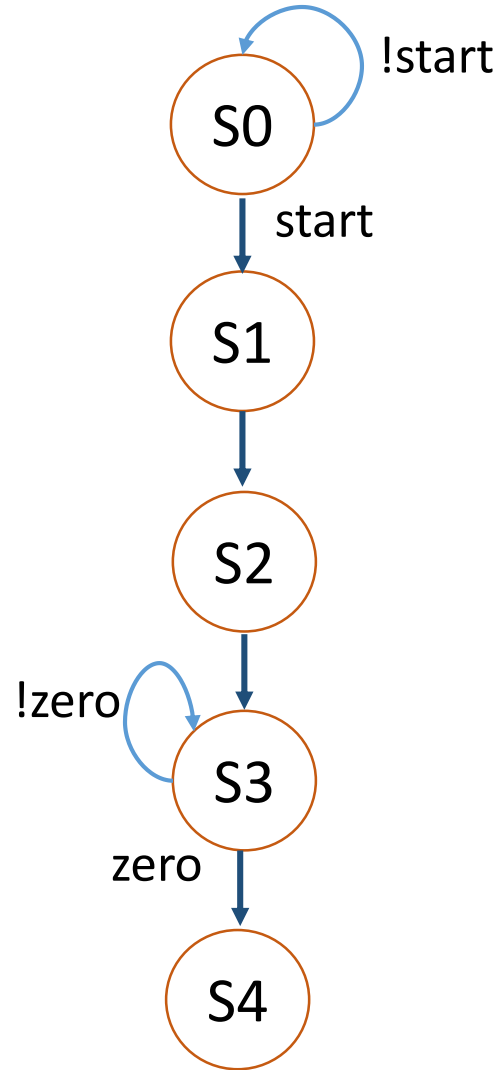

Multiplication by repeated addition

- Write HDLs and simulate



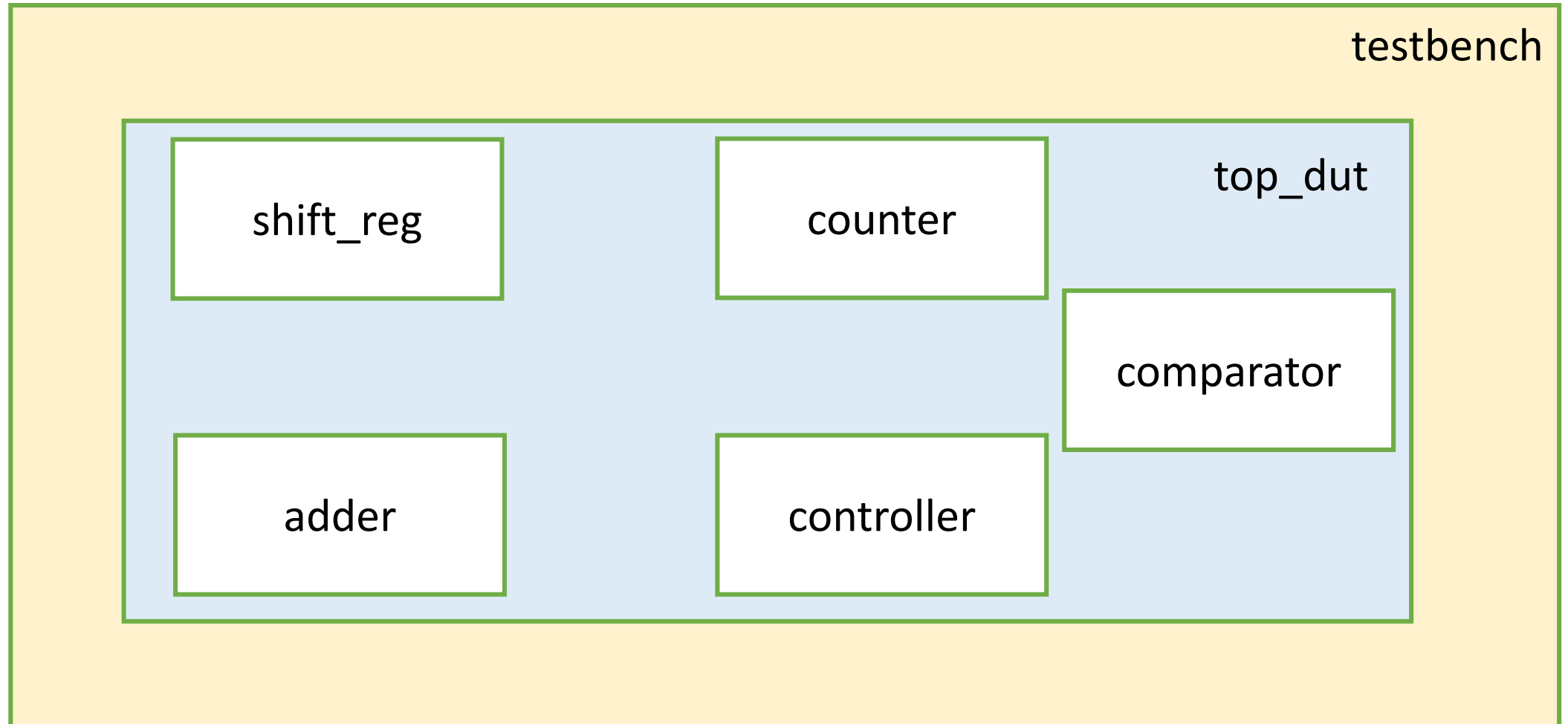


Comparators

- 0's detector: $A = 00\dots000$
- 1's detector: $A = 11\dots111$
- Equality comparator: $A = B$
- Magnitude comparator: $A < B$


1's & 0's Detectors

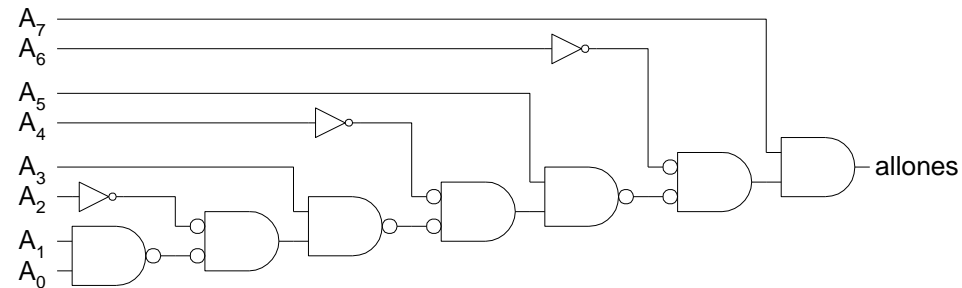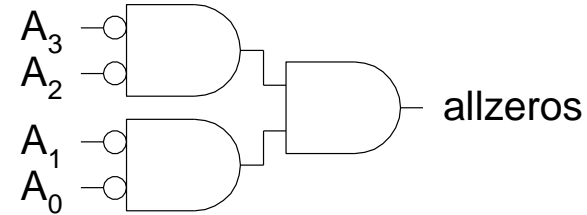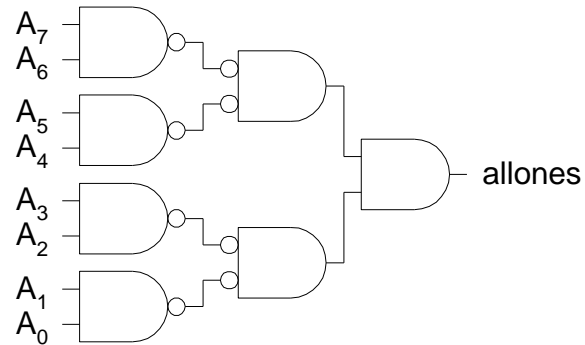- 1's detector: N-input AND gate
- 0's detector: NOTs + 1's detector (N-input NOR)




Equality Comparator

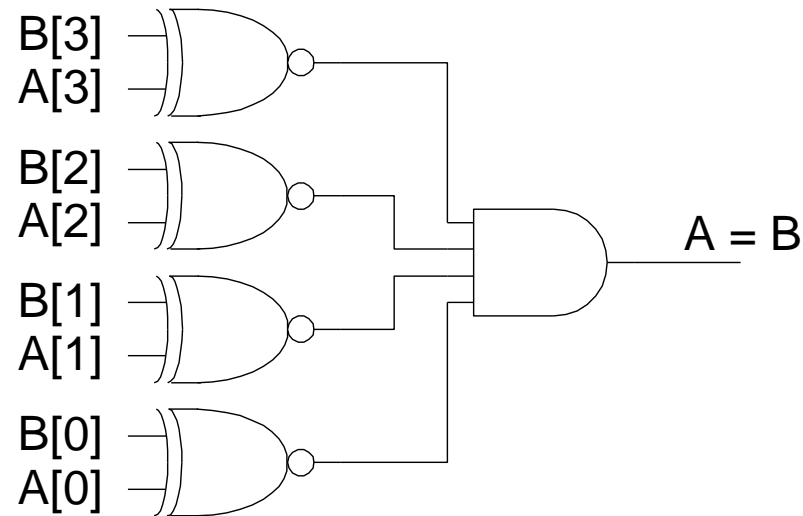- Check if each bit is equal (XNOR, an equality detector gate)
- 1's detect on bitwise equality



Magnitude Comparator

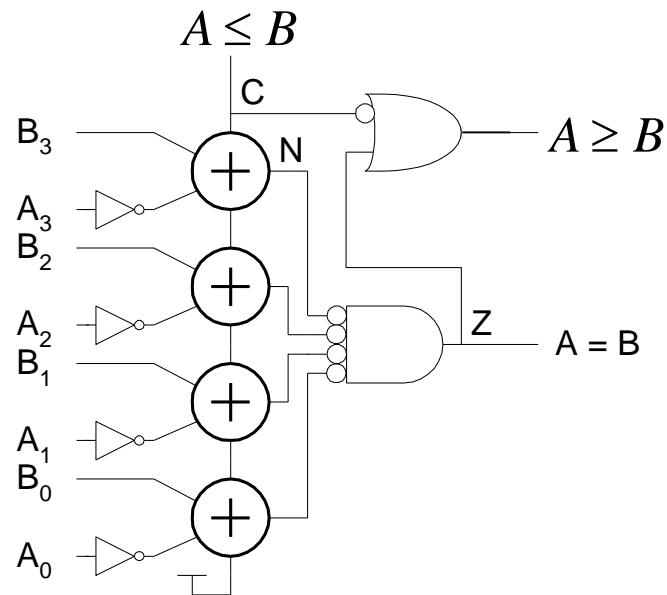- Compute $B-A$ and look at sign
- $B-A = B + \sim A + 1$
- For unsigned numbers, carry out is sign bit



Signed vs. Unsigned

- For signed numbers, comparison is harder
 - C: carry out
 - Z: zero (all bits of A-B are 0)
 - N: negative (MSB of result)
 - V: overflow (inputs had different signs, output sign \neq B)

Considering B - A


Relation	Unsigned Comparison	Signed Comparison
$A = B$	Z	Z
$A \neq B$	\bar{Z}	\bar{Z}
$A < B$	$C \cdot \bar{Z}$	$\bar{S} \cdot \bar{Z}$
$A > B$	C	S
$A \leq B$	C	\bar{S}
$A \geq B$	$\bar{C} + Z$	$S + Z$

Shifters

- Logical Shift:
 - Shifts number left or right and fills with 0's
 - $1011 \text{ LSR } 1 = 0101$ $1011 \text{ LSL } 1 = 0110$
- Arithmetic Shift:
 - Shifts number left or right. Rt shift sign extends
 - $1011 \text{ ASR } 1 = 1101$ $1011 \text{ ASL } 1 = 0110$
- Rotate:
 - Shifts number left or right and fills with lost bits
 - $1011 \text{ ROR } 1 = 1101$ $1011 \text{ ROL } 1 = 0111$

Funnel Shifter

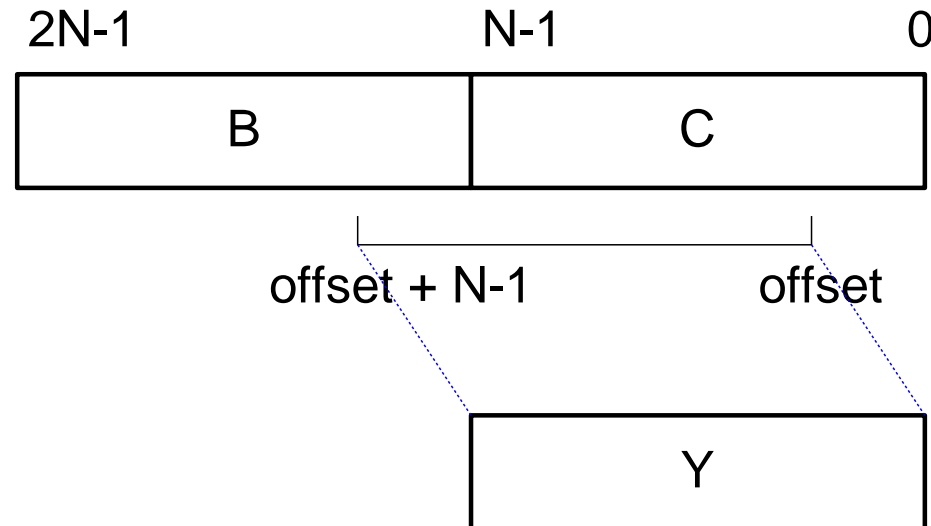- A funnel shifter creates a $2N - 1$ -bit input word Z from A then selects an N -bit field from this input word
- Selects N -bit field Y from $2N$ -bit input
 - Shift by k bits ($0 \leq k < N$)



Funnel Shifter Design

- Log N stages of 2-input muxes

