

Technology Mapping

Ref



Synthesis and Optimization of Digital Circuits by G.D.Micheli

Introduction

- Objective: To relate the circuit representation to that of the cell library and to find a cell interconnection
- Classified into two major groups: *heuristic* algorithms and *rule-based* approaches
- Two-level & Multi-level logic representations
- Covering
 - Portion of a logic network can be replaced by a library cell
 - Selecting adequate number of instances of library elements to cover the logic network while optimizing figure of merit, such as area and/or delay
- Cell *matches* a subnetwork when they are functionally equivalent
- A cell may match a subnetwork even if the number of inputs differs and some of these are shorted together or connected to a fixed voltage rail


Two-Level Logic

- During elaboration, primary inputs and outputs (ports) are defined and sequential elements (flip-flops, latches) are *inferred*
- **This results in a set of combinational logic clouds with:**
 - Input ports and register outputs are inputs to the logic
 - Output ports and register inputs are the outputs of the logic
 - The outputs can be described as Boolean functions of the inputs
 - The goal of Boolean minimization is to reduce the number of literals in the output functions
- **Many different data structures are used to represent the Boolean functions:**
 - Truth tables, cubes, Binary Decision Diagrams, equations, etc
 - A lot of the research was developed upon SOP or POS representation, which is better known as “Two-Level Logic”

  

Multi-Level Logic
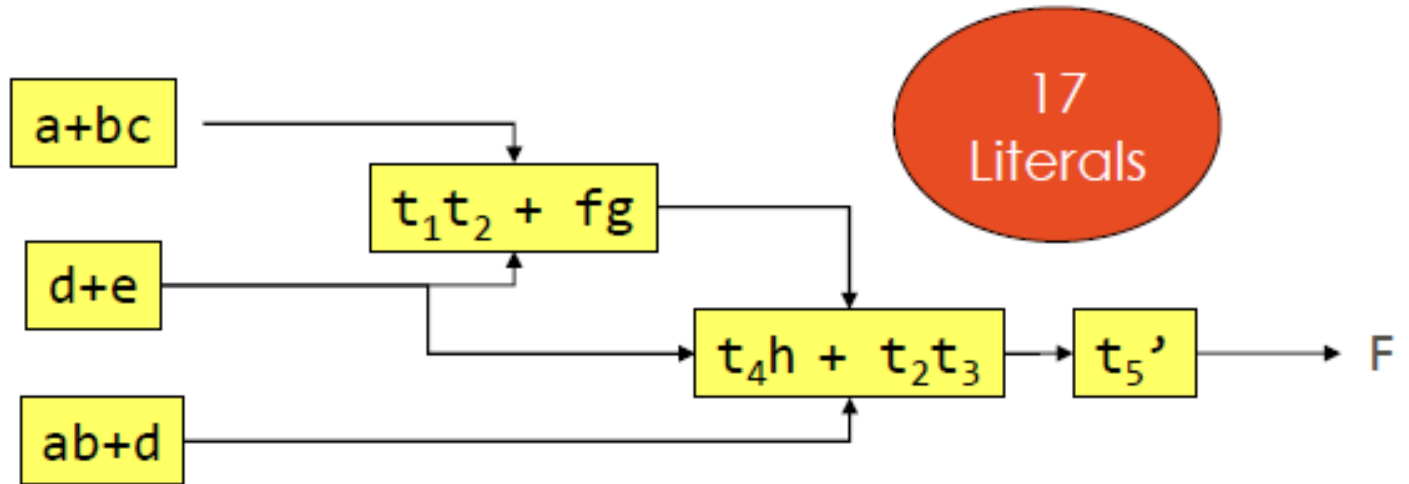
```
t1 = a + bc;  
t2 = d + e;  
t3 = ab + d;  
t4 = t1t2 + fg;  
t5 = t4h + t2t3;  
F = t5';
```




Minimize Multi-level Logic using various techniques to reduce number of variables

Binary Decision Diagrams (BDD)

- BDDs are DAGs that represent the truth table of a given function



$$f(x_1, x_2, x_3) = \sim x_1 \sim x_2 \sim x_3 + \sim x_1 \sim x_2 x_3 + \sim x_1 x_2 \sim x_3 + x_1 x_2 \sim x_3$$

x_1	x_2	x_3	$f(x_1, x_2, x_3)$
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1

 




Reduced Ordered BDD (ROBDD)

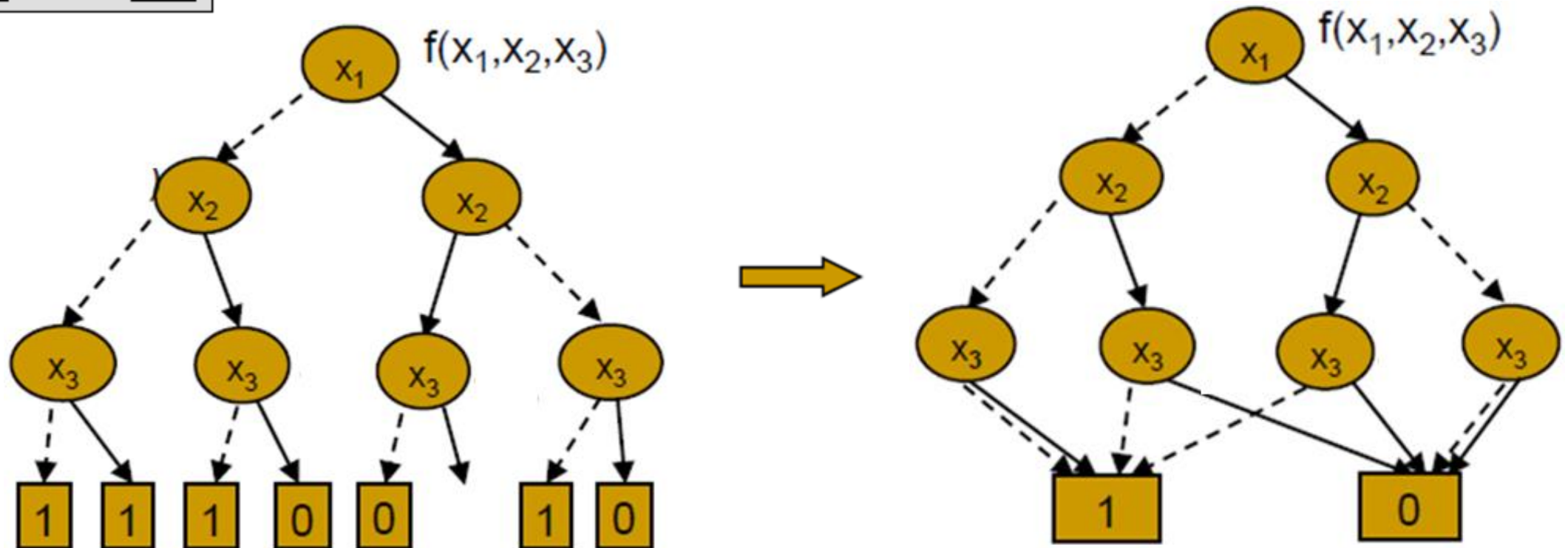 - BDDs can be very big
 - Use reduced representation
- **Reduction Rule 1: Merge equivalent leaves**






Reduced Ordered BDD (ROBDD)

   - Reduction Rule 2: Merge isomorphic nodes




Reduced Ordered BDD (ROBDD)

   - Reduction Rule 3: Eliminate Redundant Tests



Binary Decision Diagrams (BDD)

- The Shannon Expansion of a function relates the function to its *cofactors*
 - Given a Boolean function $f(x_1, x_2, \dots, x_i, \dots, x_n)$
 - Positive cofactor: $f_{i1} = f(x_1, x_2, \dots, 1, \dots, x_n)$
 - Negative cofactor: $f_{i0} = f(x_1, x_2, \dots, 0, \dots, x_n)$
- Shannon's expansion theory states that
 - $f = x_i' f_{i0} + x_i f_{i1}$
 - $f = (x_i + f_{i0})(x_i' + f_{i1})$
- This leads to the formation of a BDD:
- Example:
$$\begin{aligned} f &= ac + bc + a'b'c' \\ &= a'(b'c' + bc) + a(c + bc) \\ &= a'(b'c' + bc) + a(c) \end{aligned}$$

 

Reduced Ordered BDD (ROBDD)

- Assignment $f = ab + a'c + a'bd$
- **An Important Point:**
- The size of a BDD can vary drastically if the order in which the variables are expanded is changed.

Technology mapping

- **Technology mapping is the phase of logic synthesis when gates are selected from a technology library to implement the circuit**
- **Why technology mapping?**
- Straight implementation may not be good.
- For example, $F=abcdef$ as a 6-input AND gate causes a long delay
- Gates in the library are pre-designed, they are usually optimized in terms of area, delay, power, etc.
- Fastest gates along the critical path, area-efficient gates (combination) off the critical path.
- **Can apply a minimum cost tree-covering algorithm to solve this problem**

Technology Mapping Algorithm

- Using a recursive tree-covering algorithm, a logic network to a technology library can be mapped
- **Process requires three steps:**
 1. Map netlist and tech library to simple gates
 - Describe the netlist with only NAND2 and NOT gates
 - Describe SC library with NAND2 and NOT gates and associate a cost with each gate
 2. Tree-ifying the input netlist
 - Tree covering can only be applied to trees
 - Split tree at all places, where fanout > 1
 3. Minimum Cost Tree matching
 - For each node in your tree, recursively find the minimum cost target pattern at that node

1. Simple Gate Mapping

- Apply De Morgan laws to your Boolean function to make it a collection of NAND2 and NOT gates
- Consider

$t_1 = d + e;$
 $t_2 = b + h;$
 $t_3 = at_2 + c;$
 $t_4 = t_1t_3 + fgh;$
 $F = t_4';$

$$t_1 = d + e = \text{NAND}(\bar{d}, \bar{e})$$


$$t_2 = b + h = \text{NAND}(\bar{b}, \bar{h})$$

$$t_3 = at_2 + c = \overline{\overline{at_2} \cdot \bar{c}} = \text{NAND}(\text{NAND}(a, t_2), \bar{c})$$

$$t_4 = t_1t_3 + fgh = \text{NAND}(\overline{t_1t_3}, \overline{fgh})$$

$$fgh = \overline{\overline{f} \cdot \overline{h}} \cdot g = \overline{\overline{\overline{f} \cdot \overline{h}} \cdot \bar{g}} = \text{NAND}(\text{NAND}(\bar{f}, \bar{h}), \bar{g})$$

$$F = \bar{t_4}$$

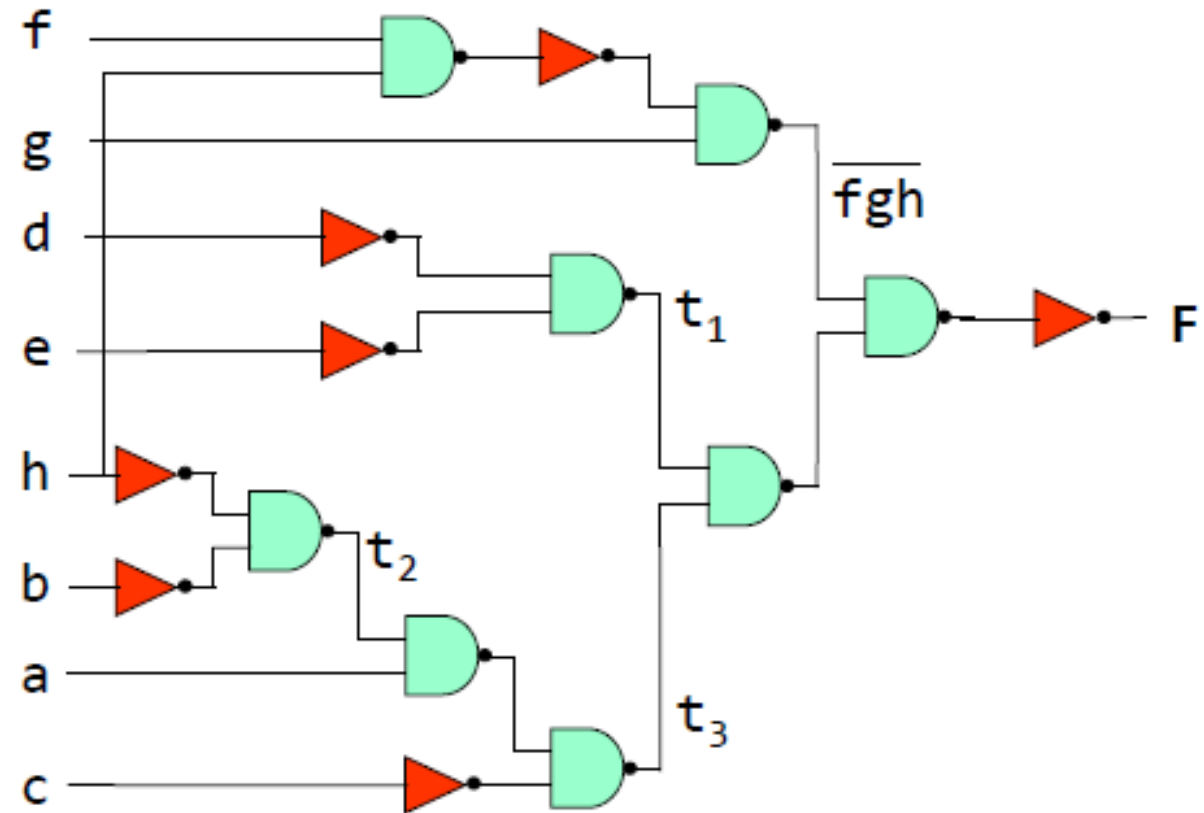


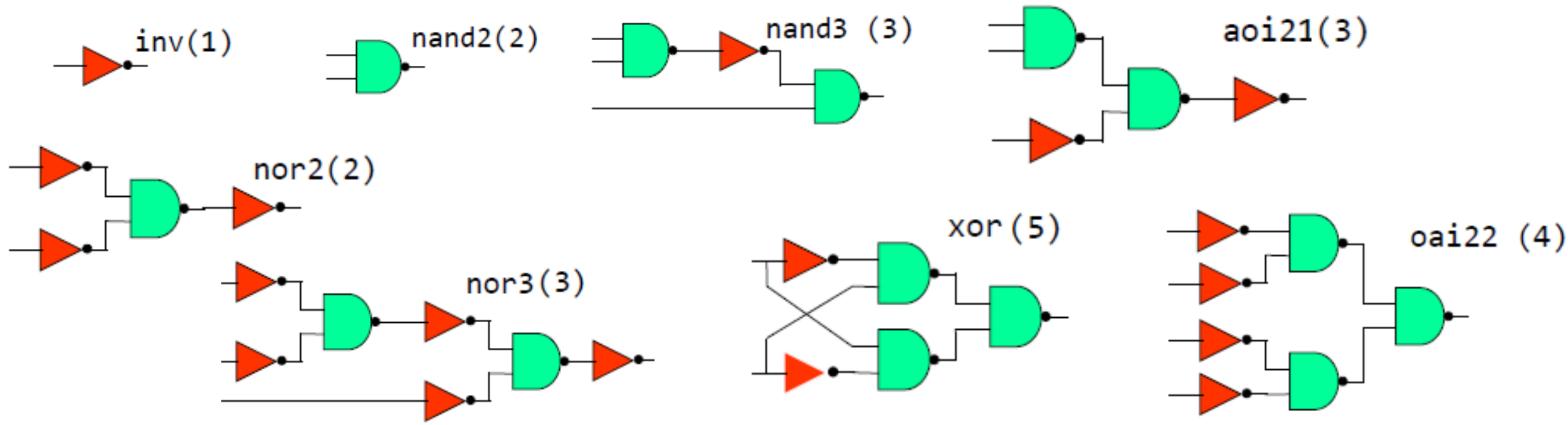1. Simple Gate Mapping

- Given a set of gates (standard cell library) with cost metrics (area/delay/power)




- We need to define the gates with the same NAND2/NOT set



 2. Tree-ifying

- *Break the tree at any node with fanout>1*



3. Minimum Tree Covering

- Now, we can apply a recursive algorithm to achieve a minimum cover
- Start at the output of the graph
- For each node, find all the matching target patterns.
- The cost of node i for using gate g is:

$$\text{cost}(i) = \min_k \left\{ \text{cost}(g_i) + \sum_k \text{cost}(k_i) \right\}$$

where k_i are the inputs to gate g

- For simplicity, redraw the graph with


- Every NOT is just an empty circle:






- Every NAND is just a full circle:



- Every input is just a box:

 

Minimum Tree Covering - Example

   

f: NOT $2 + \min(w) = 2 + 11 = 13$

AND2 $4 + \min(y) + \min(z) = 4 + 2 + 6 = 12$

AOI21 $6 + \min(x) = 6 + 3 = 9$

w: NAND2 $3 + \min(y) + \min(z) = 3 + 2 + 6 = 11$

y: NOT 2

z: NAND2 $3 + \min(x) = 3 + 3 = 6$

x: NAND2 3

Assignment

```
t1 = d + e;  
t2 = b + h;  
t3 = at2 + c;  
t4 = t1t3 + fgh;  
F = t4';
```

```
t1 = a + bc;  
t2 = d + e;  
t3 = ab + d;  
t4 = t1t2 + fg;  
t5 = t4h + t2t3;  
F = t5';
```