 



# **3. Current Mirrors**

# Current Mirrors

- **Current Mirrors / Sources / Sinks** are the important basic building blocks of analog design.
- An **ideal current source** is a two terminal element whose current is constant for any voltage across it and has infinite resistance.




**Symbol**

 


**V-I characteristics**
 
# Current Source / Sink

- Most Current Source applications require one of their terminals to be common with the most positive or the most negative D.C. voltage in the circuit.




**Current Sink**

 

**Current Source**
 
# Floating Current Source

- Neither terminal is connected to  $V_P$  nor  $V_N$ .



**Floating Current Source**

# Current Mirror


- No clear cut difference between current source and current mirror.
- A Current Mirror is also called as a  
**'Current Controlled Current Source'** (CCCS)

# Applications

- Used as biasing elements for amplifier stages.
- Used as load devices for amplifiers.
- More economical than resistors in terms of the die area required to fabricate.
- In some D/A converters, array of current sources are used to produce an analog o/p proportional to the digital i/p.
- Can be used for analog signal processing.
 
# Simple Current Source


- A simple MOSFET in saturation acts as a simple current source.



$$I_{out} = \frac{1}{2} \mu_n C_{ox} (W/L) \left[ \left( \frac{R_2}{R_1 + R_2} V_{DD} - V_t \right)^2 \right]$$
 
# Design of Basic Current Source

- Design is based on “copying” current from an available golden reference.



- A relatively complex circuit – sometimes requiring external adjustments, is used to generate a stable reference current,  $I_{REF}$ , which is then copied to many current sources.




# How to Generate Copies

For a MOSFET,  $I_D = I_{REF} = f(V_{GS})$ ;

Then,  $V_{GS} = f^{-1}(I_{REF})$

If this voltage is applied to gate-source of another MOSFET,
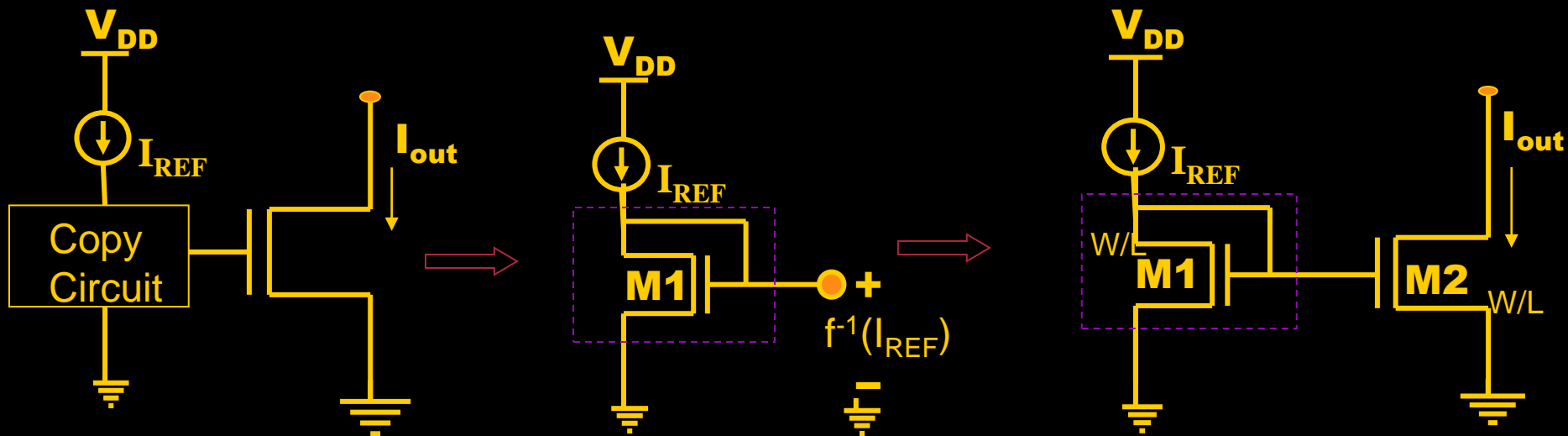
$$I_{out} = f(f^{-1}(I_{REF})) = I_{REF}$$



# How the two currents related?

Neglecting channel length modulation,


$$I_{REF} = \frac{1}{2} \mu_n C_{ox} (W/L)_1 (V_{gs} - V_t)^2$$

$$I_{out} = \frac{1}{2} \mu_n C_{ox} (W/L)_2 (V_{gs} - V_t)^2$$

$$\frac{I_{out}}{I_{REF}} = \frac{(W/L)_2}{(W/L)_1}$$




Or,  $I_{out} = \frac{(W/L)_2}{(W/L)_1} I_{REF}$

 If  $L_1 = L_2$ ,  $I_{out} = (W_2/W_1) I_{REF}$




**Current Mirror**

# Current Mirror using NMOS

   

**Current Sink**

# Current Mirror using PMOS

 

# Signal Processing

$$I_{D0} = g_{m0} \cdot V_{in} ;$$

$$I_{D1} = I_{D0} ;$$


$$\begin{aligned} I_{D2} &= I_{D1} (W/L)_2 / (W/L)_1 ; \\ &= g_{m0} \cdot V_{in} (W/L)_2 / (W/L)_1 ; \end{aligned}$$

$$I_{RL} = I_{D2} ;$$

$$V_{out} = R_L I_{RL} ;$$

Voltage Gain,
 
$$V_{out} / V_{in} = g_{m0} \cdot R_L (W/L)_2 / (W/L)_1$$



# Design Example 1:

Design a current sink using  $V_{DD} = 5V$ ,  $V_{SS} = 0V$  to sink a current of  $10\mu A$ . Estimate the minimum voltage across the current sink and the output resistance. Data given:  $L=5\mu m$ ,  $V_{GS} = 1.2V$ ,  $V_{tn} = 0.83V$ ,  $\lambda = 0.06/V$ ,  $K_n = 50\mu A/V^2$ .

$$I_{REF} = (V_{DD} - V_{GS} - V_{SS})/R$$

$$10\mu A = (5.0 - 1.2 - 0.0) / R$$


$$\therefore R = \underline{380K\Omega}.$$

$$\text{But, } I_{REF} = \frac{1}{2} K_n (W/L)_1 (V_{gs} - V_{tn})^2$$

$$10\mu A = \frac{1}{2} 50 (W/5\mu m) (1.2 - 0.83)^2$$

$$\therefore W = W1 = W2 = 14.61 \cong \underline{15\mu m}$$
 
$$\therefore I_{out} = \underline{10\mu A}$$



# Example Contd.....


The requirement for M2 to stay in the saturation region is,  
 $V_{DS2} \geq V_{GS2} - V_{tn} = \Delta V = 1.2 - 0.83 = \underline{0.37V}$  = excess gate voltage or overdrive voltage.

To keep M2 in saturation, the drain of M2 should be approx.,  
 $V_{D2} \geq V_{SS} + 0.37V = \underline{0.37V}$ .

Output resistance,  $r_o = 1 / (\lambda I_{out}) = 1 / (0.06 \times 10\mu A) = \underline{1.67M \Omega}$
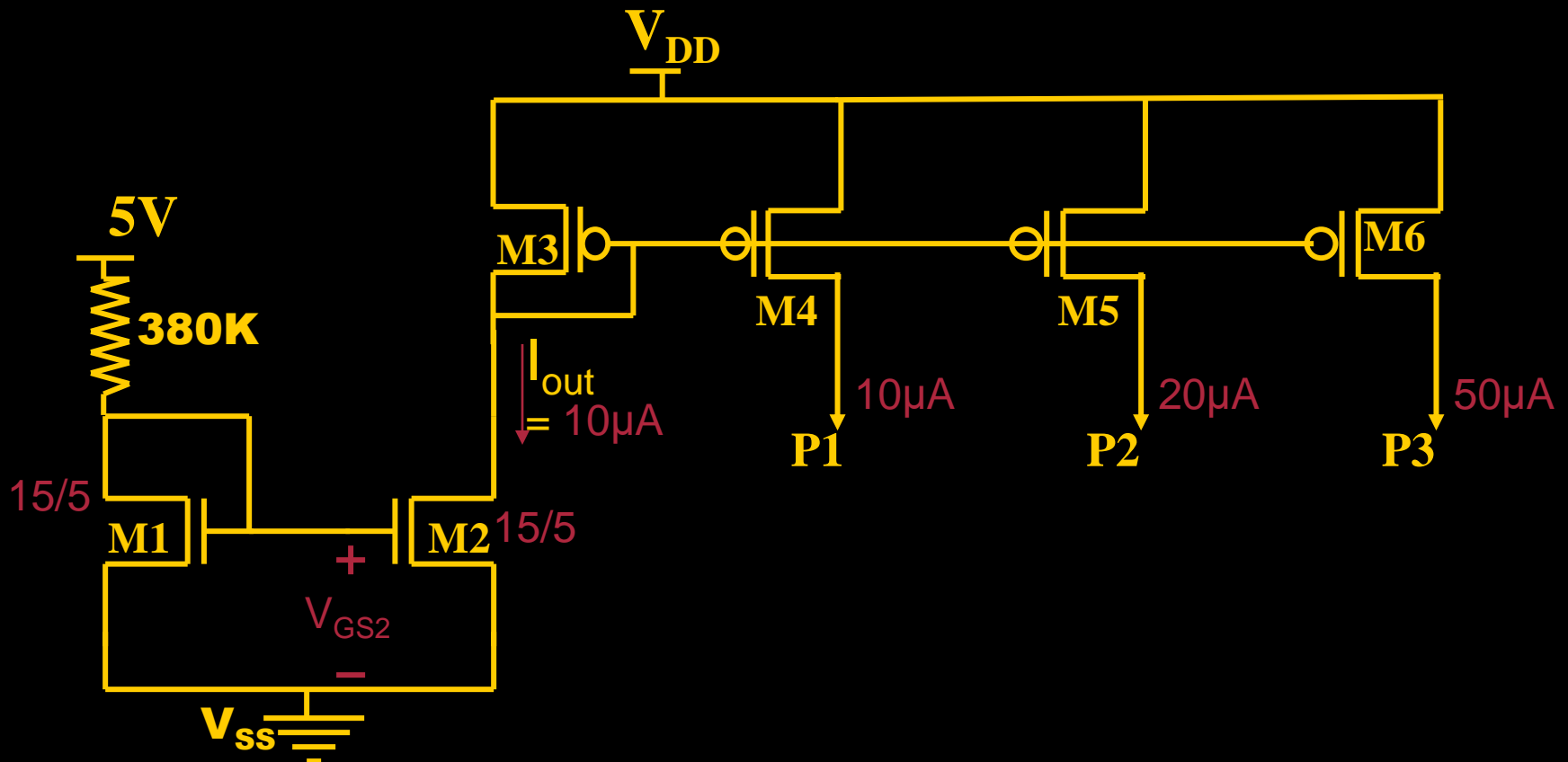
# Design Example 2:

Using the  $10\mu\text{A}$  NMOS reference current sink of the previous example, design 3 current sources (PMOS) with values of  $10\mu\text{A}$ ,  $20\mu\text{A}$ ,  $50\mu\text{A}$ . Data given:  $K_p = 17\mu\text{A}/\text{V}^2$ ,  $V_{tp} = 0.91\text{V}$





## Example Contd.....

$$I_{REF} = \frac{1}{2} K_p (W/L)_3 (V_{gs} - V_{tp})^2$$

$$10\mu A = \frac{1}{2} 17 (W_3/5\mu m)(1.2-0.91)^2$$

$$\Rightarrow \underline{W_3 \approx 70\mu m}$$

∴ The sizes of MOSFETs M4, M5 and M6 for supplying 10μA, 20μA, and 50μA can be obtained by using the relationship,  $I_{out} = (W_2/W_1)I_{REF}$  gives,

$$W_4 = \underline{70\mu m}$$

$$W_5 = \underline{140\mu m}$$


$$W_6 = \underline{350\mu m}$$

# Simple Current Mirror - Drawbacks

- So far we have neglected the channel length modulation.
- But for short-channel devices this results in significant error in copying currents.
- This is the major drawback of simple current mirrors.
 
# Simple Current Mirror - Drawbacks

If we consider channel length modulation,



$$I_{REF} = \frac{1}{2} \mu_n C_{ox} (W/L)_1 (V_{gs} - V_t)^2 (1 + \lambda V_{ds1})$$

$$I_{out} = \frac{1}{2} \mu_n C_{ox} (W/L)_2 (V_{gs} - V_t)^2 (1 + \lambda V_{ds2})$$


$$\text{Or, } \frac{I_{out}}{I_{REF}} = \frac{(W/L)_2 (1 + \lambda V_{ds2})}{(W/L)_1 (1 + \lambda V_{ds1})}$$

Here,  $V_{ds1} = V_{gs1} = V_{gs2}$

But  $V_{ds1}$  is not equal to  $V_{ds2}$
 
# Cascode Current Mirror

- Used to suppress the effect of channel length modulation.



- $V_b$  is chosen such that  $V_Y = V_X$ , then  $I_{out}$  closely tracks  $I_{REF}$ .
- The cascode device “shields” the bottom transistor from variations in  $V_P$ .

# How to generate $V_b$ ?


Objective is to make,

$$V_Y = V_X;$$

i.e.,  $V_b - V_{gs3} = V_X;$

Or,  $V_b = V_{gs3} + V_X;$



 
This implies that, if a gate-to-source voltage is added to  $V_X$ , then the required  $V_b$  can be obtained.


   
# Final Circuit

$$\frac{I_{out}}{I_{REF}} = \frac{(W/L)_2 (1 + \lambda V_{ds2})}{(W/L)_1 (1 + \lambda V_{ds1})} = \frac{(W/L)_2}{(W/L)_1}$$

Note: Body effect (of M0 and M1) also does not have any effect on this ratio.




# Cascode Current Mirror

- **Advantages:**
  - ✓ Insensitive to channel-length modulation.
  - ✓ Increase in output resistance.
- **Drawback:**
  - ✓ Minimum voltage at point P increases or swing decreases with the cascode stages.
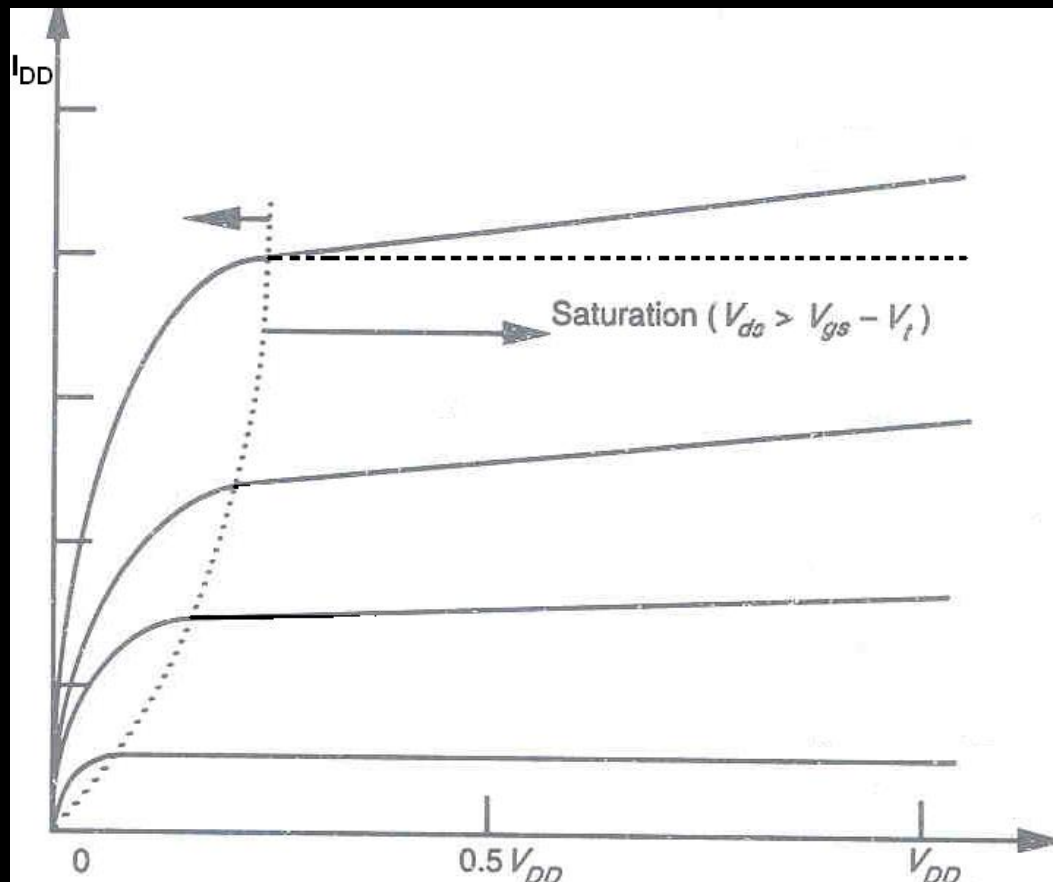
# Cascode Current Mirror



**Note:** As the number of cascode stages increase the current becomes more stable and output resistance increases.





# Minimum Voltage Across Current Mirror:

Simple Current Mirror:

  

$$\Delta V = V_{GS} - V_{th}$$

If  $V_{GS} = 1.2$ ;  $V_{th} = .83$




Then,  $\Delta V = .37v$

# Minimum Voltage Across Current Mirror:

## Cascode Current Mirror:

$$\Delta V = V_{GS} - V_{th}$$


$$V_{GS} = \Delta V + V_{th}$$

   



$$V_{GS} = 1.2; V_{th} = .83; \Delta V = .37V$$

If the voltage on the gate of M4 can be reduced to  $2\Delta V + V_{THN}$ , then the voltage on the drain of M2 becomes  $\Delta V = 0.37\text{ V}$ , and the minimum voltage across the current source is reduced to  $2\Delta V = 0.74\text{ V}$ . The circuit shown in Fig. 20.6a illustrates this idea [4]. A battery (M6) is used to drop the potential at the gate of M4 down to  $2\Delta V + V_{THN}$ . This reduces the voltage on the drain of M4 to  $2\Delta V$  before M2 and M4 enter the triode region. Implementation of this current source is shown in Fig. 20.6b. The MOSFET M3 is re-sized to generate  $3\Delta V + 2V_{THN}$ , that is,  $V_{GS3} = 2\Delta V + V_{THN} = 1.57\text{V}$ , on its gate while M6 is used to drop  $\Delta V + V_{THN}$  so that the gate voltage of M4 becomes  $2\Delta V + V_{THN}$ . To accomplish this, the width of M3 is made one-fourth the size of the other MOSFETs. Note that a MOSFET with its gate and drain tied together being fed by a constant current (M1 and M3 in Fig. 20.6) behaves as a constant DC potential (a battery).

# Technique to Lower Minimum Voltage

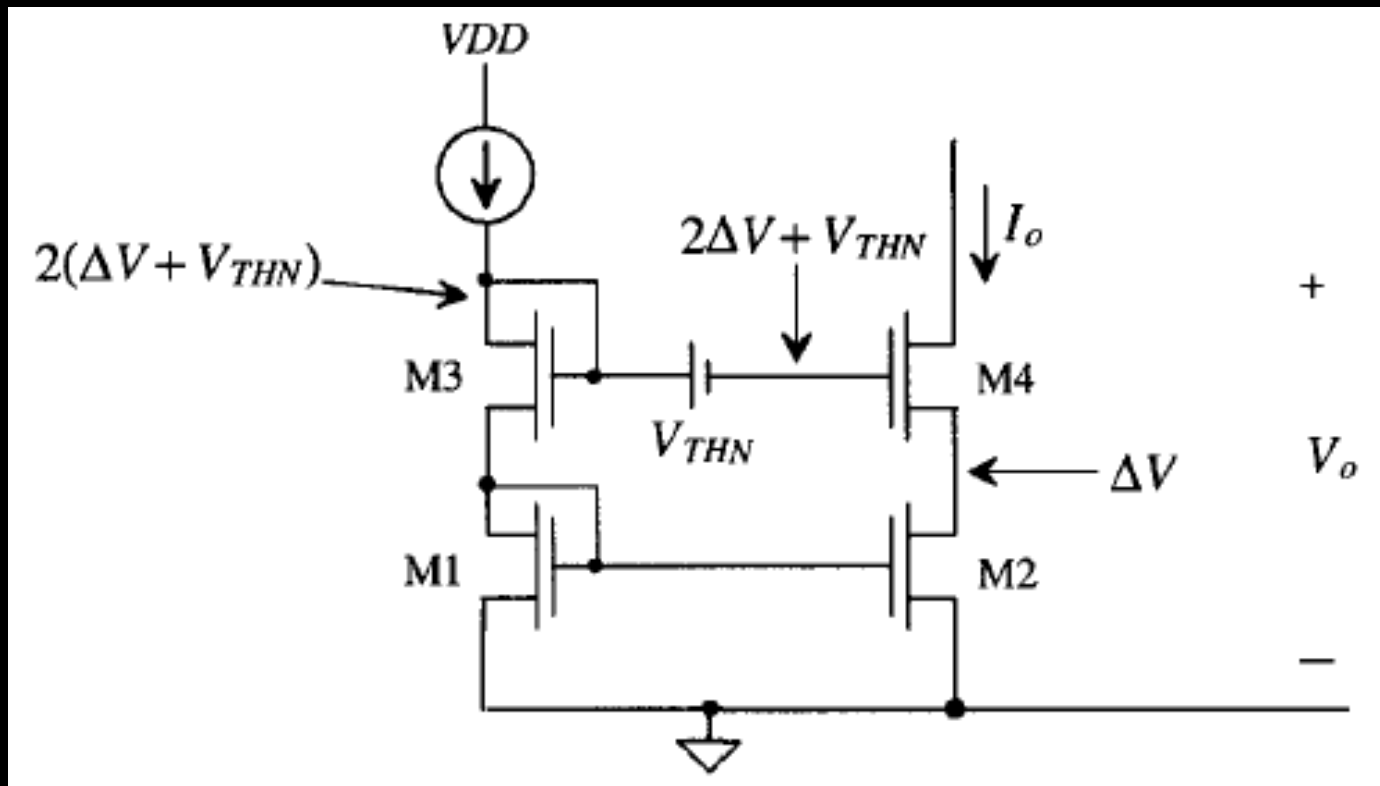
 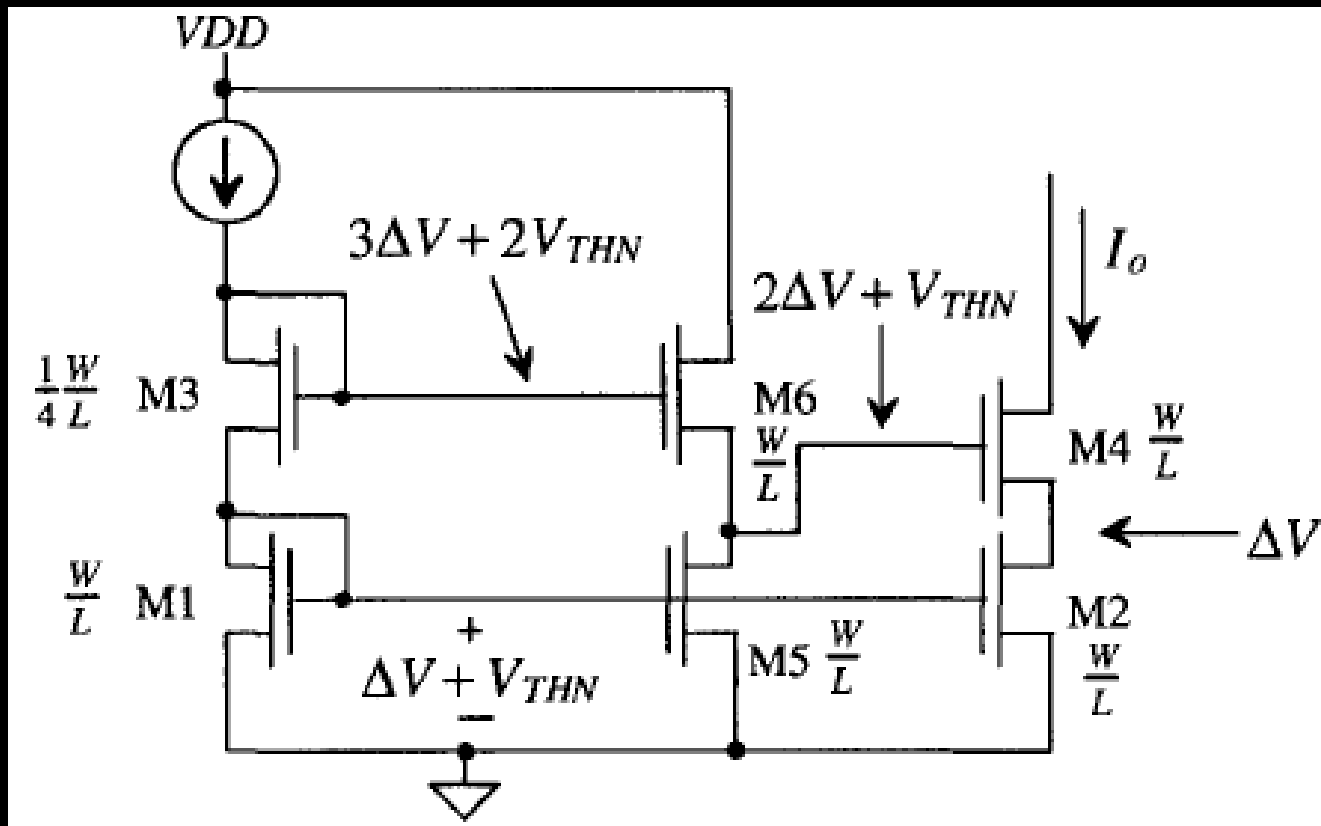
$$I_{REF} = \frac{1}{2}K_n (W/L) (V_{GS} - V_{THN})^2$$




# Output Resistance Estimation
 
## a) Simple Current Mirror:


Output Resistance,

$$R_{o(1)} = r_{o2} = 1/(\lambda I_{out})$$




# Output Resistance Estimation

## b) 2 - Stage Cascode Current Mirror:

 


Cascode Current Mirror

 


Arrangement to measure Output resistance

# Output Resistance Estimation

## b) 2 - Stage Cascode Current Mirror:

 

 Arrangement to measure  
Output resistance



Small signal equivalent ckt.



# Output Resistance Estimation

## b) 2 - Stage Cascode Current Mirror:

Here,  $v_{sb4} = i_x r_{o2}$ ;  $v_{gs4} = v_{bs4}$

$$\begin{aligned} v_x &= i_x r_{o2} + r_{o4} [i_x - g_{m4} v_{gs4} - g_{mb4} v_{bs4}] \\ &= i_x r_{o2} + r_{o4} [i_x + g_{m4} (i_x r_{o2}) + g_{mb4} (i_x r_{o2})] \end{aligned}$$

$$\text{Or, } R_{o(2)} = v_x / i_x = r_{o4} [1 + (g_{m4} + g_{mb4}) r_{o2}] + r_{o2}$$

Since  $g_{mb} \ll g_m$ ,

$$R_{o(2)} = r_{o4} [1 + g_{m4} r_{o2}] + r_{o2} \quad (\text{Neglecting body effect})$$

## For a triple cascode current mirror:

$$R_{o(3)} = r_{o6} [1 + g_{m6} (r_{o4} (1 + g_{m4} r_{o2} + r_{o2}))] + r_{o4} (1 + g_{m4} r_{o2}) + r_{o2}$$

$$R_{o(3)} = r_{o6} [1 + g_{m6} R_{o(2)}] + R_{o(2)}$$

In general, for n-stage cascode current mirror,

$$R_{o(n)} = r_{o(n)} [1 + g_{mn} R_{o(n-1)}] + R_{o(n-1)}$$


Where  $R_{o(n-1)}$  is the resistance looking into the drain of lower MOSFETs.

# Other Current Sources / Sinks


1. Wilson Current Mirror
2. Regulated Cascode Current Mirror

- Use negative feedback
- More stable current
- Enhanced output impedance
- Wider voltage swings

# Wilson Current Mirror

 

# Regulated Cascode Current Mirror

 

- More current stability, higher output impedance & Wider voltage swings compared to Wilson Current Mirror