


Clocking Strategies

Introduction

- **Clock - key to synchronous systems**
- Clocks help the design of FSM where outputs depend on both input and previous states.
- Clock signals provide reference points in time - define what is previous state, current state and next state:

Introduction


 
- **Clock - key to synchronous systems**
- Clocks help the design of FSM where outputs depend on both input and previous states.
- Clock signals provide reference points in time - define what is previous state, current state and next state:



Latch vs Flip-Flop



- Latch

stores data when
clock is low

  


- Flip-Flop

stores data when
clock rises

 
 


Clock for timing synchronization

 
- Clocks serve to slow down signals that are too fast
- Flip-flops / latches act as barriers
- With a latch, a signal can't propagate through until the clock is high
- With a Flip-flop, the signal only propagates through on the rising edge
- All real flip-flops consist of two latch like elements (master and slave latch)



Latch Timing Parameters

  

Flip-flop Timing Parameters


 


Clocking Strategies

- Different clocking methods:
 - Pulse mode clocking
 - Edge triggered clocking
 - Two phase clocking
 - Single phase clocking



Pulse Mode Clocking

  - Two requirements:
- All loops of logic are broken by a single latch
- The clock is a narrow pulse
- It must be shorter than the shortest path through the logic




Edge Trigger Flip-flop

  - Used in many ASIC designs (Gate Arrays and Std Cells)
- Using a single clock, but replaces latches with flip-flops



Two phase clocking


 
- Use different edges for latching the data and changing the output



There are 4 different time periods, all under user control:

- ◆ $\phi 1$ high
- ◆ $\phi 1$ falling to $\phi 2$ rising
- ◆ $\phi 2$ high
- ◆ $\phi 2$ falling to $\phi 1$ rising

Single-phase Clocking

  


Clock Distribution

- In a large CMOS chip, clock distribution is a serious problem
 - $V_{dd}=5V$
 - $C_{reg}=2000pF$ (20K register bits @ 0.1pF)
 - $T_{clk}=10ns$
 - $T_{rise/fall}=1ns$
 - $I_{peak}=Cdv/dt=(2000p \times 5)/1n=10A$
 - $Pd=CV_{dd}^2f=2000p \times 25 \times 100M=5W$
- Methods for reducing the values of I_{peak} and Pd
 - Reduce C
 - Interleaving the rise/fall time

Clock Distribution

- Clocking is a floorplanning problem because clock delay varies with position on the chip
- Ways to improve clock distribution
 - Physical design
 - * Make clock delays more even
 - * At least more predictable
 - Circuit design
 - * Minimizing delays using several stages of drivers
- Common physical clocking networks
 - H tree
 - Balanced tree

Clocking Distribution – *H Tree*

 

Clocking Distribution – *Reducing Power*

- Technique used to reduce the high dynamic power dissipation
 - Use a low capacitance clock routing line such as metal3.
 - This layer of metal can be, dedicated to clock distribution only