 


ADIABATIC TECHNIQUES




INTRODUCTION

- Definition of 'Adiabatic' in thermodynamics:
 - Of, relating to, or being a reversible thermodynamic process that occurs without gain or loss of heat and without a change in entropy.

ADIABATIC CIRCUIT PRINCIPLES

- Adiabatic or energy-recovery circuits use reversible logic to conserve energy.
- They achieve low energy dissipation by restricting current so that it flows across a device with very low voltage drop and by recycling (reusing) the energy stored on the device's capacitors.
- This approach differs dramatically from CMOS circuits, which dissipate energy during switching.
- Avoids dissipating most of the circuit node energy when switching, by transferring charges in a nearly adiabatic (literally, “without causing heat”) fashion.
 - i.e., asymptotically thermodynamically reversible

ADIABATIC CHARGING – POWER DISSIPATION

 

Charging a load capacitance
through a switch

- $Q = CV$
- $I = Q/T = CV/T$
- $E = I^2 RT$ (Resistor)
 $= (CV/T)^2 RT$
 $= (2RC/T)(1/2 CV^2)$
- Better than CMOS by a factor of $(2RC/T)$

Where T is the time it takes
charge or discharge

ADIABATIC CHARGING – POWER DISSIPATION

- Reversible logic uses the fact that a single clock cycle is much longer than $2RC$, and thus attempts to spread the charging of the gate over the whole cycle and hence reduces the energy dissipated.

ADIABATIC LOGIC

- Adiabatic Logic is the term given to low-power electronic circuits that implement reversible logic.
- The term comes from the fact that an adiabatic process is one in which the total heat or energy in the system remains constant.

ADIABATIC LOGIC

- In general, in order to restore the charge, the following rules should be followed by the MOS devices in an adiabatic circuit:
 - A device can be turned on only while the source-drain voltage is zero
 - Source-drain voltage can be changed only while the device is off
 - Any voltage change must be done gradually

ADIABATIC LOGIC

- There are two basic types of adiabatic circuits;
 - Fully adiabatic
 - Quasi adiabatic

FULLY ADIABATIC CIRCUITS

- With fully adiabatic circuits, charge from a discharging capacitor is used to charge the capacitance of the next stage.
- While these circuits allow the designer to obtain asymptotically zero energy (losing energy only due to the leakage currents through non-ideal switches), that benefit comes at the cost of substantial design complexity.
- Ex: SCRL(split level charge recovery logic),
RERL(reversible energy recovery logic)

QUASI-ADIABATIC CIRCUITS

- Quasi-adiabatic circuits possess a simpler architecture (e.g., adiabatic charging and discharging) and power clock system, which makes them much more practical for today's electronic systems.
- These circuits also feature minimum energy loss that is typically proportional to the capacitance driven and the square of the voltage.
- Ex: Pass transistor Adiabatic Logic (PAL) circuit which operates with a two-phase sinusoidal power clock.

COMPARISON – CONVENTIONAL V/S ADIABATIC


❑ Conventional CMOS

- Changing value of a bit requires converting bit signal into heat
- 2 States : True, False
- Speed is very high at the expense of power consumption.

❑ Adiabatic CMOS

- Returns value (energy) of the bit back to the source
- 3 States: True, False, Off
- Very low power dissipation is achieved at expense of speed.

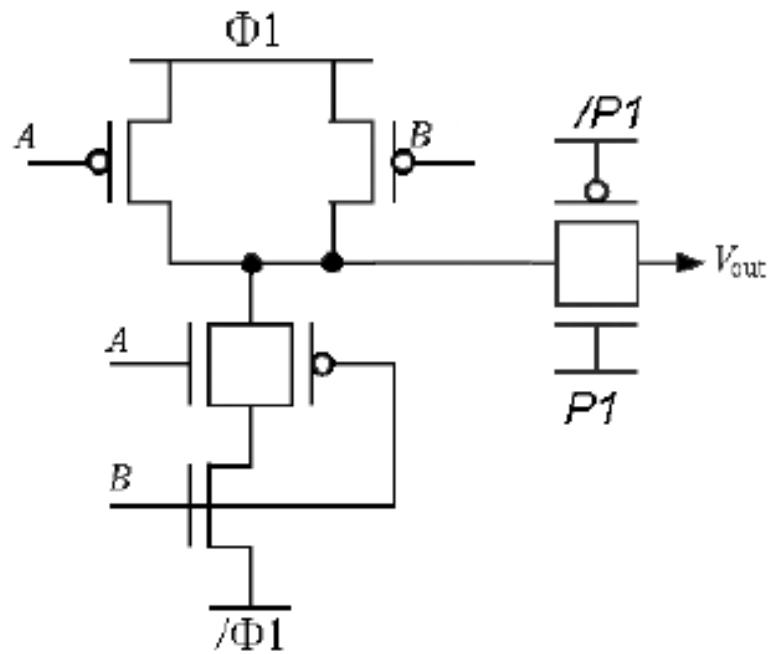SPLIT-LEVEL CHARGE RECOVERY LOGIC (SCRL) - SCRL NAND GATE



- This circuit is very similar to a conventional NAND; however, one of the main differences is that the top and bottom rails are driven by trapezoidal clocks ($\Phi 1$ and $\bar{\Phi} 1$) rather than V_{dd} and Gnd .
- In the beginning the whole circuit is set at $V_{dd}/2$ except for $P1$ which is set to Gnd and $\bar{P}1$ which is set to V_{dd} so that the transmission gate is off.
- In the next step, the transmission gate is turned on by gradually switching the value of $P1$ and $\bar{P}1$.
- Next, $\Phi 1$ and $\bar{\Phi} 1$ which were at $V_{dd}/2$ are split to V_{dd} and Gnd respectively.
- At this point, the gate computes the NAND of A and B like a non-adiabatic gate would compute.

- Once the output is used by the next gate, the transmission gate can be turned off gradually.
- Then $\Phi 1$ and $/\Phi 1$ are gradually returned to $V_{dd}/2$ and now the input can change and the next cycle can begin.
- It is important not to change the inputs until the rails are back to $V_{dd}/2$ so that the transistors are not turned on when there is a potential difference across the gate, thus satisfying the first rule.

○ Extra – PMOS

- Once $\Phi 1$ and $\bar{\Phi} 1$ are split, when A has a value of logical 1 and B of logical 0, current flows from Vdd through the P-MOS controlled by B and down through the N-MOS controlled by A.
- This presents a high voltage drop across NMOS controlled by A, which will dissipate energy.
- This problem is solved by the extra P-MOS, which sets $V_{ds} = 0$ for the NMOS controlled by A.
- In general, it must be ensured that internal nodes do not dissipate power.


- Pipelined circuit at the gate level can be achieved.
- In order to achieve gradual swings needed to operate these gates, trapezoidal clocks are used.
- Initially, the voltage is held constant for quarter of a cycle, then gradually raised or lowered, held constant again, and for the final quarter, is gradually returned to the initial value.

OTHER ADIABATIC LOGIC STYLES

- ECRL
- PFAL

- Ref : Low-Power VLSI Circuits and Systems - Ajith Pal

PRINCIPLES OF ADIABATIC POWER SUPPLY


 


- The power supply terminal swings gradually from 0 to V_{dd} , stays at V_{dd} for a while and then swings back to 0

PRINCIPLES OF ADIABATIC POWER SUPPLY

- If $x = 0$, and the initial charge on capacitance C is 0, then node y follows the power supply to V_{dd} during its upward swing.
- Similarly, while discharging, potential of node y follows the power supply terminal swinging gradually from V_{dd} to 0, so that there is little potential difference across the path (from the power supply terminal to node y) in the whole transition process.
- Hence only a small amount of energy is dissipated.

PRINCIPLE OF ADIABATIC POWER SUPPLY

  

PRINCIPLES OF ADIABATIC POWER SUPPLY

- The power supply/clock waveform $\Phi 1$ can be divided into four phases:
 1. $\Phi 1$ is in the idle phase when $\Phi 1 = 0$
 2. $\Phi 1$ is in the evaluation phase when $\Phi 1$ goes up from 0 to V_{dd} .
 3. $\Phi 1$ is in the hold phase during the time interval in which $\Phi 1$ remains high
 4. $\Phi 1$ is in the restoration phase when it goes down from V_{dd} to 0.

PRINCIPLES OF ADIABATIC POWER SUPPLY

- After evaluation: the output y_1 of the first stage must hold for a while in order to be sampled by the second stage.
- Also there should be an isolation device to isolate the input x and the output y_1 , say a transmission gate.
- Otherwise x can not change its value as long as y_1 needs to hold its value, and y_1 can not change its value as long as y_2 needs to hold its value and so on.
- Hence an input has to be held constant until the signal propagates all the way to the last stage of the logic levels.

PRINCIPLES OF ADIABATIC POWER SUPPLY

- A consequence of the isolation, the charge may not flow back to the power/clock terminal along the original charging path.
- Thus, another path has to be created to let the potential of y_l follow Φ_1 going down to 0.
- However, unlike the charging path which is controlled by the inputs, the turning on of the discharge path depends on the logic value of y_l .
- When y_l is 1, charge can flow back to power terminal through the path shown above during the restoration phase.
- If y_l is 0, this path must be open to prevent current leaking from Φ_1 to y_l , which not only will consume energy but might set a wrong logic value to node y_l .

PROBLEMS OF ADIABATIC LOGIC

- It requires 50% more area than conventional CMOS
- Simple circuit designs can be very complicated.
- Adiabatic circuits face difficulties in speed for a number of reasons:
 - Charging time is inherently much slower than CMOS
 - Adiabatic circuits are difficult to pipeline.
 - Increasing speed of adiabatic circuits increases power-clock data sensitivity
- Factors at work aiding the speed problem:
 - Scaling decreases R and C , which naturally makes T smaller
 - Multiple power-clock designs to handle pipelining

REFERENCES

- <http://chipdesignmag.com/lpd/blog/tag/asynchronous/>
- Adiabatic Logic by Benjamin Gojman, August 8, 2004
- Ultra Low Energy Computing Using Adiabatic Switching Principle by Yibin Ye and Kaushik Roy

Thank You !